

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY

Electronics and Communication Engineering

Electrical Science-1 (15B11EC111)

Tutorial Sheet: 10

Q1. [CO3] A series resonance network consisting of a resistor of $30\ \Omega$, a capacitor of $2\ \mu\text{F}$ and an inductor of $20\ \text{mH}$ is connected across a sinusoidal supply voltage which has a constant output of $9\ \text{V}$ at all frequencies. Calculate the resonant frequency, the current at resonance, the voltage across the inductor and capacitor at resonance, the quality factor and bandwidth of the circuit. Also, find the upper and lower -3 dB frequency points f_H and f_L .

Q2. [CO3] A series circuit consists of a resistor of $4\ \Omega$, an inductance of $500\ \text{mH}$ and a variable capacitance connected across a $100\ \text{V}$, $50\ \text{Hz}$ supply. Calculate the capacitance required to produce a series resonance condition and the voltage generated across both the inductor and the capacitor at the points of resonance.

Q3. [CO3] A parallel resonance network consisting of a resistor of $60\ \Omega$, a capacitor of $120\ \mu\text{F}$ and an inductor of $200\ \text{mH}$ is connected across a sinusoidal supply voltage which has a constant output of $100\ \text{V}$ at all frequencies. Calculate the resonant frequency, the quality factor and bandwidth of the circuit, the circuit current at resonance frequency.

Q4. [CO3] A constant voltage of frequency $1\ \text{MHz}$ is applied to a lossy inductor (r in series with L), in series with a variable capacitor, C as shown in Fig. 5.1. The current drawn is maximum when $C=400\ \text{pF}$, while current is reduced to $(1/\sqrt{2})$ of the above value, when $C=450\ \text{pF}$. Find the value of r and L . Calculate the quality factor of the coil and the bandwidth.

Q5. [CO3] A coil having a resistance of $15\ \Omega$ and an inductance of $0.75\ \text{H}$ is connected in series with a capacitor as shown in Fig. 5.2(a). The circuit draws maximum current when a voltage of $200\ \text{V}$ at $50\ \text{Hz}$ is applied. A second capacitor is then connected in parallel to the circuit as shown in Fig. 5.2(b). What should be its value such that the combination acts like a non-inductive resistance with same voltage $200\ \text{V}$ at $100\ \text{Hz}$ and calculate the currents drawn by the two circuits too.

