

Course Name: Electrical Science- II
Course Code: 15B11EC211

Contents


➤ Sequential switching

➤ Problems

➤ References

Sequential Switching

- Sequential switching occurs when a circuit contains two or more switches that change state at different instants [1]
- When a series of sequential switches are thrown at various times, as series of sequential charge-ups or discharges will occur with the capacitor. Of course, every time a new circuit is created with the throwing of a switch, it creates new time constants and new complete responses [1,2].

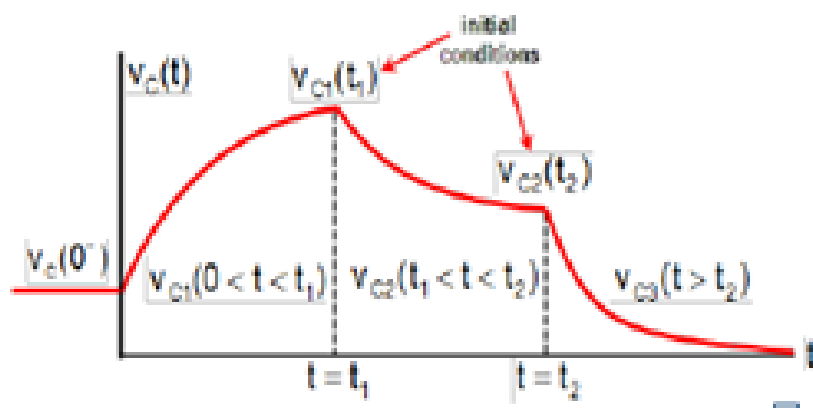

Initial steady state	$t = 0^-$
Circuit-1 with τ_1	$t = 0^+$
Circuit-2 with τ_2	$t = t_1$
Circuit-3 with τ_3	$t = t_2$
\vdots	

Sequential Switching

Mathematically what do we expect?

Circuit 1: The switch is closed at $t=0^-$ and steady state is established. The complete response of circuit-1 is

$$V_{c1}(0 < t < t_1) = V_{oc1} + [V_c(0^+) - V_{oc1}]e^{-t/\tau_1}$$

Circuit 2: When the switch is thrown at $t=t_1$, a second RC circuit is created that requires its own complete response and new time constant τ_2 . However, there are two new things that have to be accounted for.

- The discharging of the capacitor starts at $t=t_1$ and therefore, its complete response is time shifted: t is replaced by $t-t_1$.
- The capacitor's initial voltage is the final steady state value of the previous circuit -1 at time $t=t_1$.

With these modifications, the discharging behavior of the capacitor then looks like


$$V_{c2}(t_1 < t < t_2) = V_{oc2} + [V_{c1}(t_1) - V_{oc2}]e^{-\frac{(t-t_1)}{\tau_2}}$$

Circuit 3: Following the same ideas as with circuit-2's complete response, we write

$$V_{c3}(t_2 < t < \infty) = V_{c2}(t_2)e^{-\frac{(t-t_1-t_2)}{\tau_3}}$$

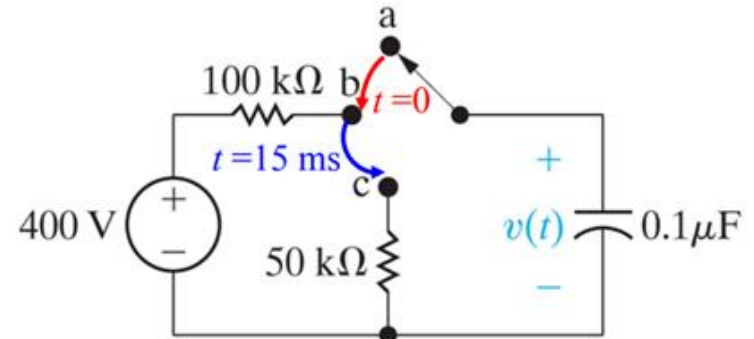Problem-1

Q. For the given network, find $v(t)$ for $t > 0$ [1]



Sol. For $t < 0$, capacitor is disconnected to rest of the circuit, Hence

$$V(0^-) = V(0^+) = 0$$

For $0 < t \leq 15$ ms, the 400 V source charges the capacitor via the 100 K Ω resistor, therefore final value of capacitor voltage is $V_f = 400$ V, $\tau = RC = 10$ ms, then capacitor voltage is given as

$$v_1(t) = V_f + [V(0^+) - V_f]e^{-t/\tau} = 400 - 400e^{-100t} \text{ V}$$

Problem-1 Continues


For $t > 15$ ms, the capacitor is disconnected from the 400 V source and is discharged via the $50\text{ K}\Omega$

Resistor, therefore,

$$V(0) = v_1(15\text{ms}) = 310.75\text{ V}$$

$V_f = 0$; $\tau = RC = 5\text{ ms}$, then capacitor voltage is given as
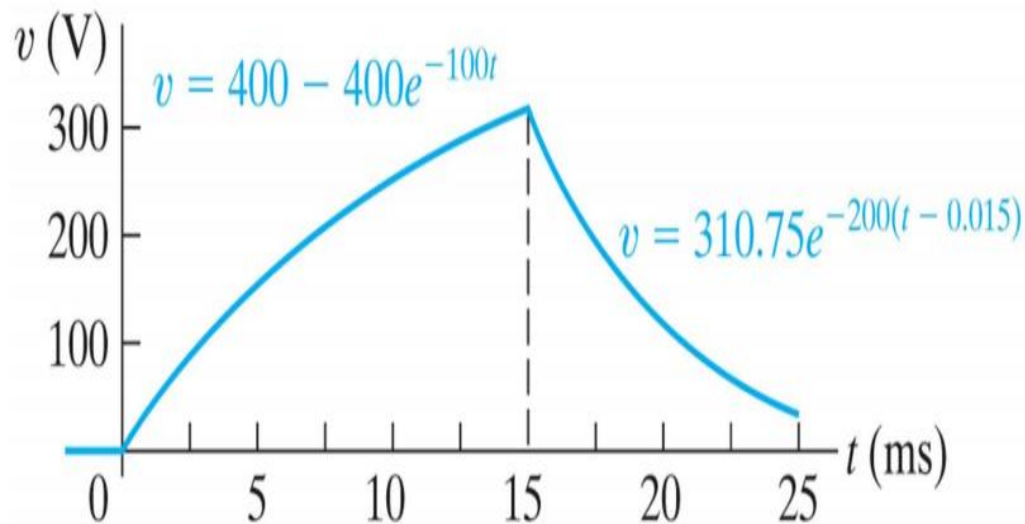
$$v_1(t) = V_f + [V(0^+) - V_f]e^{-(t-t_o)/\tau} = 310.75e^{-200(t-0.015)}\text{ V}$$




$$v(t) = \begin{cases} 0 & t < 0 \\ 400 - 400e^{-100t}\text{ V} & 0 < t \leq 15\text{ ms} \\ 310.75e^{-200(t-0.015)}\text{ V} & t > 15\text{ ms} \end{cases}$$

Practice Problem

Q. The circuit shown in Fig. is at steady state before the switch closes at time $t=0$. The switch remains closed for 1.5s and then opens. Determine the capacitor voltage for $t>0$. [1]

Ans
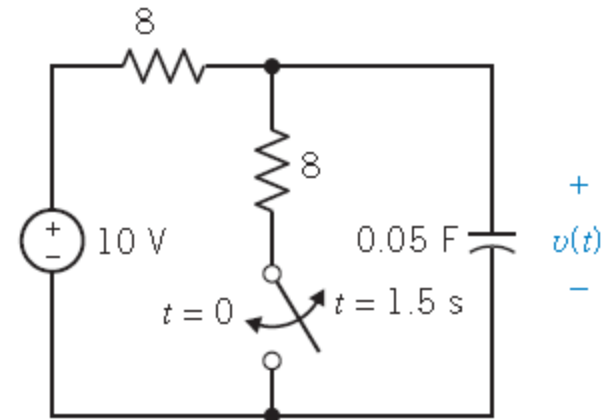
$$v(t) = \begin{cases} 10 & t < 0 \\ 5 + 5e^{-5t}V & 0 < t \leq 1.5s \\ 10 - 5e^{-2.5(t-1.5)}V & t > 1.5s \end{cases}$$



References

- [1] R.C. Dorf and J. A. Svoboda, “Introduction to Electric Circuits”, 9th ed, John Wiley & Sons, 2013.
- [2] W. H. Hayt, J. E. Kemmerly and S. M. Durbin, “ Engineering Circuit Analysis,” New York: McGraw-Hill,2006