

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY
Electronics and Communication Engineering
Electrical Science-II (15B11EC211)
Tutorial Sheet: 3

Q1[CO1] Find the differential equation for the voltage v for the circuit of Figure 1

Answer: $\frac{d^2v}{dt^2} + 1001 \frac{dv}{dt} + 1001 \times 10^3 v = \frac{dv_s}{dt} + 1000v_s$

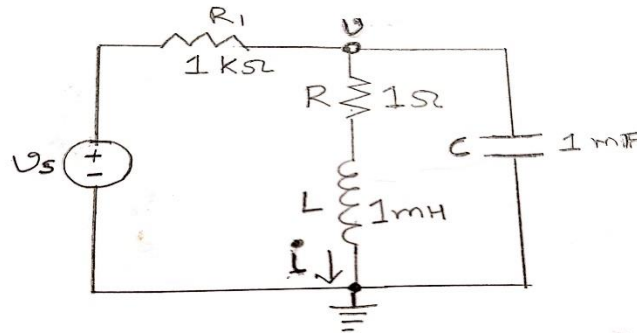


Figure 1

Q2[CO1] Find the natural response $v_n(t)$ of the RLC (Fig.2) circuit, where $R = 6\Omega$, $L=7\text{ H}$, and $C= 1/42\text{ F}$. The initial conditions are $v(0) = 0$ and $i(0) = 10\text{ A}$.

Answer: $-84 (e^{-t}-e^{-6t})\text{ Volts}$

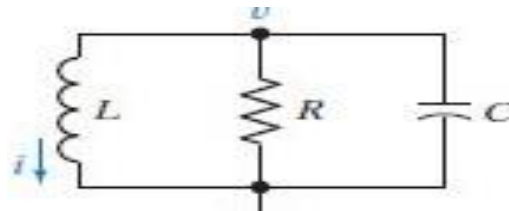


Figure 2

Q3[CO1] A parallel RLC circuit (Fig. 2) has $R=10\Omega$, $C=1\text{ mF}$, $L=0.4\text{ H}$, $v(0)=8\text{ V}$, and $i(0) = 0$. Find the natural response $v_n(t)$ for $t > 0$.

Answer: $e^{-50t} (8 - 400t)\text{ V}$

Q4[CO1] Consider the parallel RLC circuit when $R=25/3\Omega$, $L=0.1\text{H}$, $C=1\text{mF}$, $v(0)=10\text{V}$, and $i(0)=-0.6\text{A}$. Find the natural response $v_n(t)$ for $t > 0$.

Answer: $v_n(t) = 10e^{-60t} \cos 80t\text{ V}$

Q5[CO1] Determine $i(t)$ for $t > 0$ for the circuit shown in Figure 3.

Answer: $i(t) = 0.2 + 0.246 e^{-3.62t} - 0.646 e^{-1.38t}\text{ A for } t > 0.$

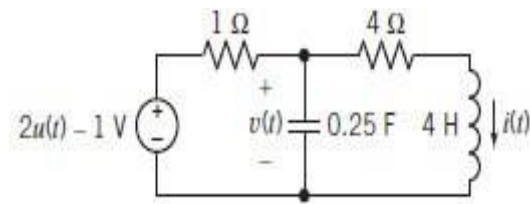


Figure 3

Q6[CO1] Find $i(t)$ for $t > 0$ for the circuit shown in Figure 4 when $R = 3 \Omega$, $L = 1 \text{ H}$, $C = 1/2 \text{ F}$, and $i_s = 2e^{-3t} \text{ A}$. Assume steady state at $t = 0^-$.

Answer: $i = 12e^{-t} - 14e^{-2t} + 2e^{-3t}$

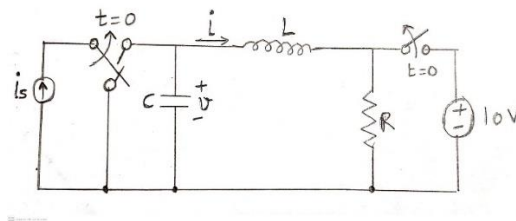


Figure 4

Q7[CO1] Find the forced response for the inductor current i_f for the parallel RLC circuit shown in Figure 5 when $i_s = 8e^{-2t} \text{ A}$. Let $R = 6 \Omega$, $L = 7 \text{ H}$, and $C = 1/42 \text{ F}$.

Answer: $i_f = -12e^{-2t} \text{ A}$

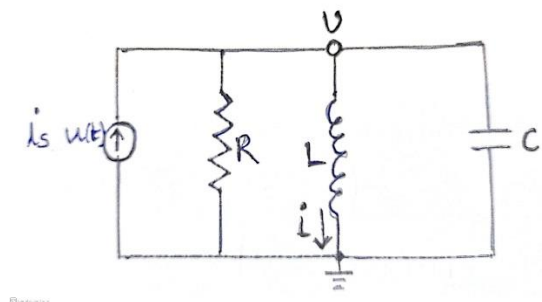


Figure5