

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY, NOIDA
Electronics and Communication Engg.
B.Tech. IInd year
Digital Systems (18B11EC213) Even Sem
Tutorial-2

1. Find out simplified SOP expression for the function given below by K-map.

i. $f(x,y,z,w)=\Sigma m(1,3,6,7,9,13,14,15)$

ii. $f(x,y,z,w)=\Sigma m(0,1,2,3,4,7,8,11,12,14,15)$

iii. $f(x,y,z,w)=\Pi M(4,6,7,9,12,14,15)$

iv. $f(x,y,z,w)=\Pi M(0,1,2,3,4,7,8,12,14)$

2. Simplify the following Boolean function in POS form using K-map.

i. $f(x,y,z,w)=\Sigma m(1,2,3,6,7,10,11)+\Sigma d(5,8,9)$

ii. $f(x,y,z,w)=\Pi M(1,2,3,5,6,7)+\Pi d(8,9)$

iii. $f(x,y,z,w)=\Sigma m(2,3,10,11)+\Sigma d(1,8,9)$

iv. $f(x,y,z,w)=\Pi M(1,2,3,8)+\Pi d(4,9)$

3. Realize 4-bit Binary to Gray Code converter using any logic gate.

4. Realize full subtractor with 2-level NAND-NAND realization.

5. Implement the following Boolean function with 8 x 1 multiplexer.

i. $f(x,y,z,w)=\Pi M(1,2,3,5,7,8,11)$

ii. $f(x,y,z,w)=\Sigma m(0,2,3,5,6,7,11)$

6. Implement the following Boolean function with 4 x 1 multiplexer and external logic gates.

i. $f(x,y,z)=\Sigma m(1,2,3,5,7)$

ii. $f(x,y,z)=\Sigma m(0,2,3,7)$

iii. $f(x,y,z,w)=\Sigma m(1,2,3,5,9,10,14)$

iv. $f(x,y,z,w)=\Sigma m(1,2,4,5,9,10,14)$

7. Design 1x8 demultiplexer using two 1x4 demultiplexers.

8. Design 4x1 and 8x1 multiplexer using 2x1 multiplexer.

9. Design a magnitude comparator for comparing two numbers of three bits.

10. Find out the set of prime-implicants and essential prime-implicants from the given functions and obtain the minimal expression using K-map

i. $f(x,y,z,w)=\Sigma m(0,1,2,5,7,8,9,10,13,15)$

ii. $f(x,y,z,w)=\Sigma m(0,1,2,3,4,6,8,9,10,11)$