

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY
Electronics and Communication Engineering
Electrical Science-I (15B11EC111)
Tutorial Sheet: 1

Q1. [CO1] Using only 1K resistors, synthesize a resistor of $3/5$ K and $5/3$ K. You can use maximum 4 resistors in each case.

Q2. [CO1] Find the effective resistance between terminals A and B for the networks given in Fig. 1.1.
[Ans. (a) $12\ \Omega$; (b) $5\ \Omega$; (c) $10R/3$ (d) $3\ \Omega$ (e) $4\ \Omega$]

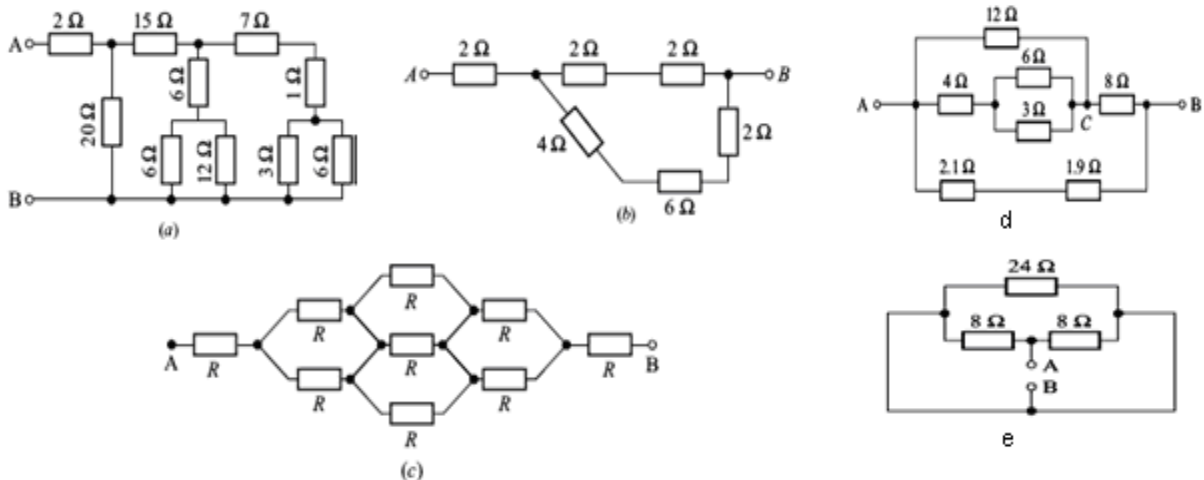


Fig. 1.1

Q3. [CO1] The resistance of two coils is 25 ohms when connected in series, and 6 ohms when connected in parallel. Determine the individual resistances of the two coils.

[Ans. $15\ \Omega$, $10\ \Omega$]

Q4. [CO1] Calculate the current drawn from a 12-V supply with internal resistance $0.5\ \Omega$ by the infinite ladder network, each resistance being 1 ohm, in Fig. 1.2.

[Ans. 3.71 A]

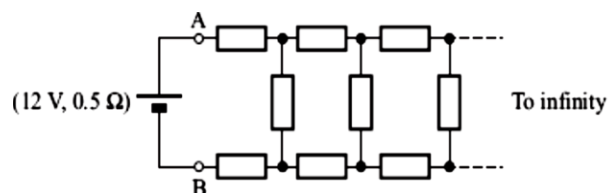


Fig. 1.2

Q5. [CO1] A 4 mF capacitor has the current waveform shown in Fig. 1.3. Assuming that $v(0)=10\text{ V}$, sketch the voltage waveform $v(t)$.

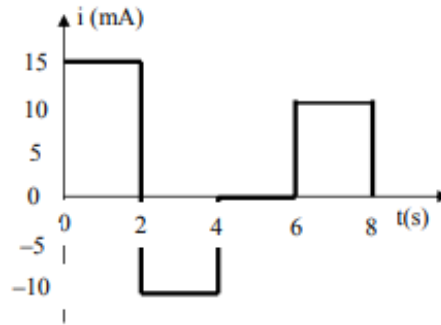


Fig. 1.3

Q6. [CO1] The current $i(t)$ in a 2H inductor connected in a telephone circuit changes according to

$$i(t) = \begin{cases} 0 & t \leq 0 \\ 4t & 0 < t \leq 2 \\ -4t + 16 & 2 < t \leq 4 \end{cases}$$

Where unit of time is second and the unit of current is mA. Determine the power $p(t)$ absorbed by the inductor and energy $w(t)$ stored in the inductor.

$$\text{Ans. } p(t) = \begin{cases} 0 & t \leq 0 \\ 32t \mu\text{W} & 0 < t \leq 2 \\ (32t - 128) \mu\text{W} & 2 < t \leq 4 \end{cases}, \quad w(t) = \begin{cases} 0 & t \leq 0 \\ 16t^2 \mu\text{J} & 0 < t \leq 2 \\ (16t^2 - 128t) \mu\text{J} & 2 < t \leq 4 \end{cases}$$

Q7. [CO1] Consider the circuit shown in Fig. 1.4 with $v(t) = 12e^{-8t}V$ and $i(t) = 5e^{-8t}A$ for $t \geq 0$. Both $v(t)$ and $i(t)$ are zero for $t < 0$. Find the power supplied by this element and the energy supplied by the element over the first 100 ms of operation.

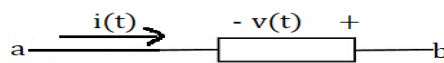


Fig. 1.4

$$\text{Ans. } p(t) = 60e^{-16t}W \text{ and } W = 2.99 J$$