

Solution
Tutorial - 3

Q1. Solution :-

The KCL node equation at the upper node is

$$\frac{V - V_s}{R_1} + i + C \frac{dV}{dt} = 0$$

To determine equation in terms of V , we need a second equation in terms of current i . Equation for current through inductor is

$$Ri + L \frac{di}{dt} = V.$$

Using the operator $s = \frac{d}{dt}$, two equations are

$$\frac{V}{R_1} + CsV + i = \frac{V_s}{R_1}$$

$$\text{and } -V + Ri + Lsi = 0$$

Substituting parameter values and rearranging we have,

$$(10^{-3} + 10^{-3}s)V + i = 10^{-3}V_s$$

$$-V(10^{-3}s + 1) + i = 0$$

Using Cramer's rule, solve for V

$$V = \frac{(s+1000)V_s}{(s+1)(s+1000)+10^6} = \frac{(s+1000)V_s}{s^2+1001s+1001 \times 10^3}$$

Therefore, we have

$$[s^2 + 1001s + 1001 \times 10^3]V = (s+1000)V_s$$

The differential equation is

$$\text{Ans} = \left[\frac{d^2V}{dt^2} + 1001 \frac{dV}{dt} + 1001 \times 10^3 V = \frac{dV_s}{dt} + 1000V_s \right]$$

Signature _____

Q2

Solution:- Given


$$R = 6 \Omega, L = 7 H \text{ \& } C = 1/42 F$$

Initial condⁿ

$$V(0) = 0$$

$$i(0) = 10 A$$

$$V_n(t) = ?$$

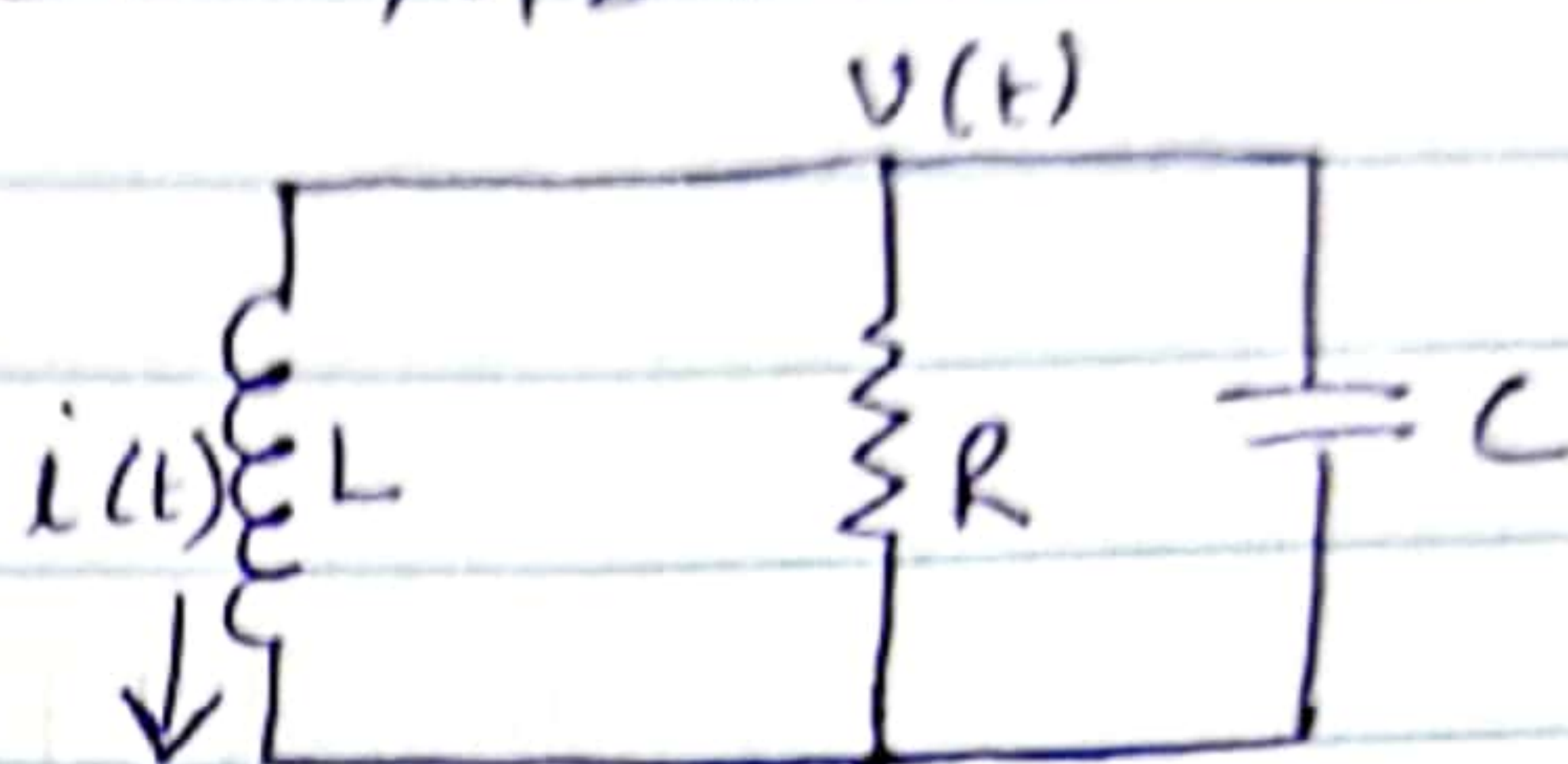

$$\frac{dV(0)}{dt} = - \left[\frac{V(0) + Ri(0)}{Rc} \right]$$

$$= - \left[\frac{0 + 6 \times 10}{6 \times \frac{1}{42}} \right] = -420 V/s$$

For source free parallel RLC ckt, two roots -

$$S_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 6 \times \frac{1}{42}} = \frac{42}{12} = 3.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{6 \times \frac{1}{42}}} = \sqrt{6} = 2.42$$

$$\left. \begin{array}{l} \alpha > \omega_0 \\ \text{Overdamped} \\ \text{case.} \end{array} \right\}$$

$$S_{1,2} = -3.5 \pm \sqrt{(3.5)^2 - 6} = -1, -6$$

$$S_1 = -1 \text{ \& } S_2 = -6$$

for $t > 0$

$$V_n(t) = A_1 e^{-1t} + A_2 e^{-6t}$$

Differentiating $V_n(t)$

$$\frac{dV_n(t)}{dt} = -A_1 e^{-t} - 6A_2 e^{-6t}$$

Applying initial conditions

$$V(0) = A_1 + A_2 \dots (1)$$

$$\frac{dV(0)}{dt} = -420 = -A_1 - 6A_2 \dots (2)$$

Solving eqn (1) & (2)

$$A_1 = -84 \text{ \& } A_2 = 84$$

so

$$V_n(t) = -84e^{-t} + 84e^{-6t}$$

$$\text{Ans } \boxed{V_n(t) = -84(e^{-t} - e^{-6t}) \text{ A.}}$$

Q3 Solution :-

Given $R = 10\Omega$, $C = 1\text{mF}$, $L = 0.4\text{H}$

Initial condition

$$V(0) = 8\text{V} \text{ \& } i(0) = 0$$

We know that

$$S_{1,2} = -\frac{1}{2RC} \pm \sqrt{\left(\frac{1}{2RC}\right)^2 - \left(\frac{1}{\sqrt{LC}}\right)^2}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times 10 \times 1 \times 10^{-3}} = 50$$

$$\omega_0 = \frac{1}{\sqrt{LC}} = \frac{1}{\sqrt{0.4 \times 1 \times 10^{-3}}} = 50 \text{ rad/sec.}$$

$\alpha = \omega_0 \Rightarrow$ Critically damped case.

$$S_1 = S_2 = -\alpha = -50$$

for ~~that~~ $t > 0$

$$V_n(t) = (A_1 + A_2 t)e^{-\alpha t} = (A_1 + A_2 t)e^{-50t}$$

$$V(0) = 8 = (A_1 + A_2 \times 0)e^0$$

$$A_1 = 8$$

$$\frac{dV(0)}{dt} = - \left[\frac{V(0) + R i(0)}{R_c} \right]$$

$$= - \left[\frac{8 + 10 \times 0}{10 \times 10^{-3}} \right]$$

$$\frac{dV(0)}{dt} = -800 \text{ V/s}$$

$$\frac{dV(t)}{dt} = (A_1 + A_2 t)(-50e^{-50t}) + A_2 e^{-50t}$$

$$\frac{dV(0)}{dt} = -800 = (8 + A_2 \times 0)(-50e^0) + A_2$$

$$-800 = -8 \times 50 + A_2$$

$$A_2 = -400$$

So Natural response

Ans $V_n(t) = (8 - 400t)e^{-50t} \text{ Volt}$

Q4 solution:

Given $R = 25/3 \Omega$, $L = 0.1 \text{ H}$, $C = 1 \text{ mF}$

Initial Condition

$$V(0) = 10 \text{ V} \text{ \& } i(0) = -0.6 \text{ A}$$

First, we determine α^2 & ω_0^2

$$\alpha = \frac{1}{2RC} \text{ \& } \omega_0^2 = \frac{1}{LC}$$

$$\alpha = \frac{1}{2RC} = \frac{1}{2 \times \frac{25}{3} \times 1 \times 10^{-3}} = 60$$

$$\omega_0^2 = \frac{1}{LC} = \frac{1}{0.1 \times 1 \times 10^{-3}} = 10^4$$

$\omega_0^2 > \alpha^2$, So the natural response is underdamped.

Damped resonant frequency ω_d is

$$\begin{aligned}\omega_d &= \sqrt{\omega_0^2 - \alpha^2} = \sqrt{10^4 - 3.6 \times 10^3} \\ &= 80 \text{ rad/s.}\end{aligned}$$

The ~~case~~ characteristic roots are

$$s_1 = -\alpha + j\omega_d = -60 + j80$$

$$s_2 = -\alpha - j\omega_d = -60 - j80$$

The natural response is

$$v_n(t) = B_1 e^{-60t} \cos 80t + B_2 e^{-60t} \sin 80t$$

Because $v(0) = 10$, we have

$$B_1 = v(0) = 10$$

By using equation directly to find B_2

$$\begin{aligned}B_2 &= \frac{\alpha}{\omega_d} B_1 - \frac{v(0)}{\omega_d RC} - \frac{i(0)}{\omega_d C} \\ &= \frac{60 \times 10}{80} - \frac{10}{80 \times 25/3000} - \frac{-0.6}{80 \times 10^{-3}} \\ &= 7.5 - 15.0 + 7.5 = 0\end{aligned}$$


Therefore, natural response is

Ans $V_n(t) = 10e^{-60t} \cos 80t \text{ V}$

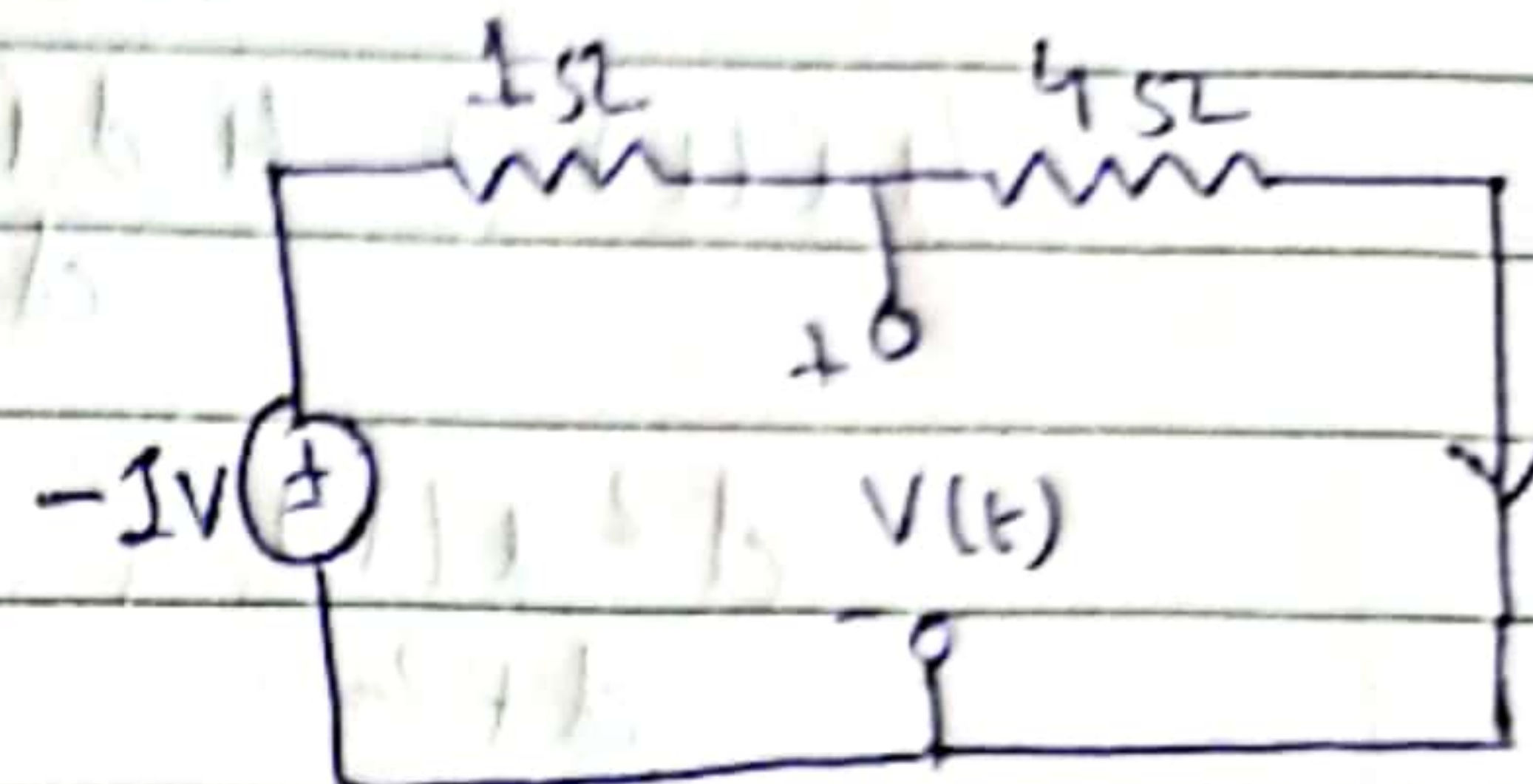Q5) Solution:-

for $t < 0$, $u(t) = 0$

circuit will be in steady state at $t = 0^-$ and hence capacitor will act as open circuit while inductor will act as short circuit.



$$i(0^-) = \frac{-1}{1+4} = -\frac{1}{5} = -0.2 \text{ A}$$

Now

$$V(0^-) + R i(0^-) + 1 = 0$$


$$V(0^-) + 1 \times \left(-\frac{1}{5}\right) + 1 = 0$$

$$V(0^-) = -\frac{4}{5} \text{ volt.}$$

for $t > 0$, $u(t) = 1$

$$V(0^+) = V(0) = V(0^-) = \frac{4}{5}$$
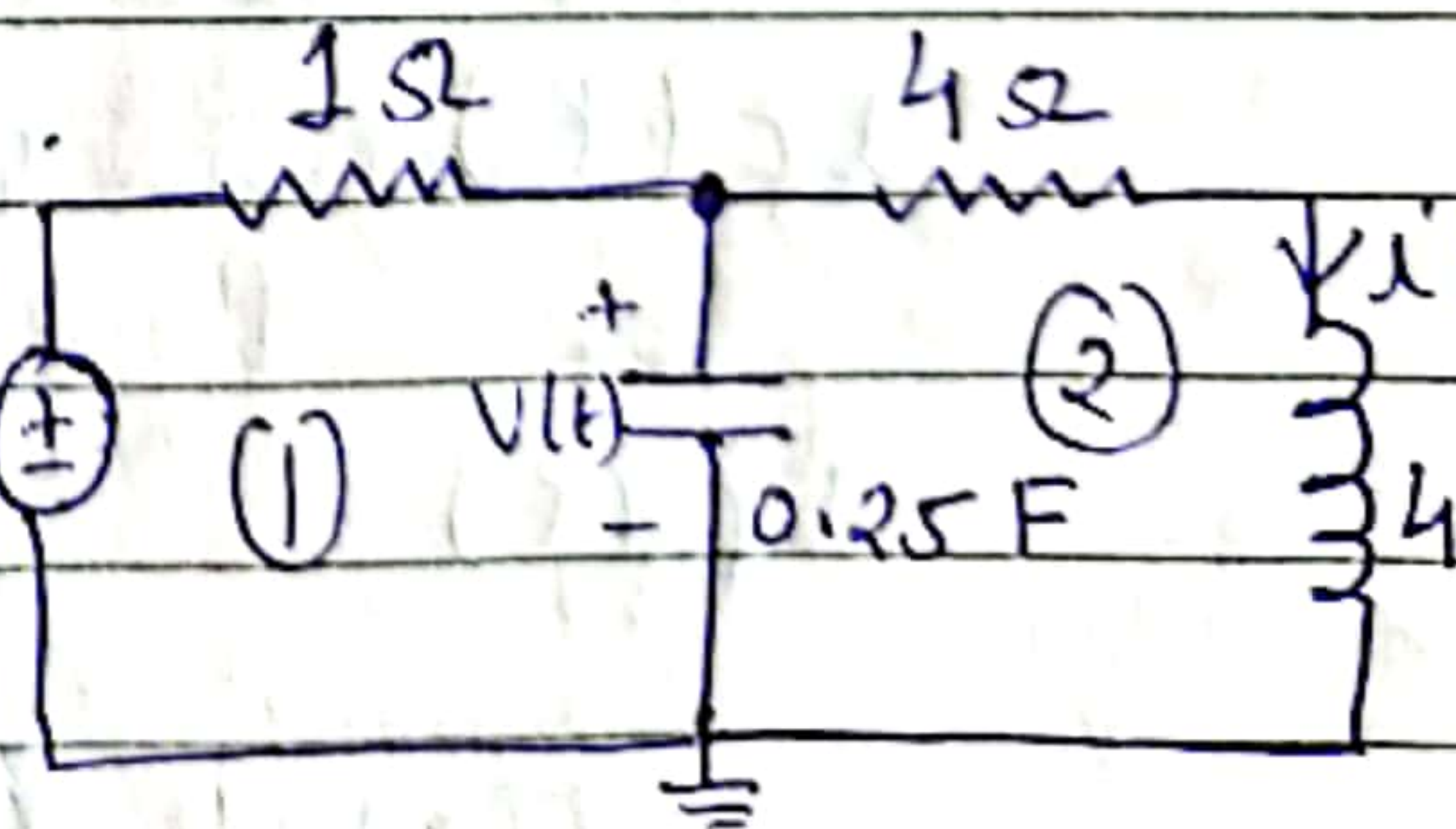
$$i(0) = i(0^-) = i(0^+) = -0.2 \text{ A}$$



Applying KVL in loop ②

$$V(t) = 4i(t) + L \frac{di(t)}{dt} \quad \text{--- (1)}$$

Applying KCL at top node

$$\frac{V(t) - 1}{1} + 0.25 \frac{dV(t)}{dt} + i(t) = 0 \quad \text{--- (2)}$$

using eq (1) & (2)

$$4i(t) + 4 \frac{di(t)}{dt} + 0.25 \frac{d}{dt} \left[4i(t) + 4 \frac{di(t)}{dt} \right] + i(t) = 0$$

$$\frac{d^2 i(t)}{dt^2} + 5 \frac{di(t)}{dt} + 5 i(t) = 1$$

$$s = \frac{d}{dt}$$

$$(s^2 + 5s + 5) i(t) = 1$$

To find roots

$$s^2 + 5s + 5 = 0$$

$$s = \frac{-b \pm \sqrt{b^2 - 4ac}}{2a}$$

$$s = -3.62, -1.38$$

Natural response

$$i_n(t) = A_1 e^{s_1 t} + A_2 e^{s_2 t}$$

$$i_n(t) = A_1 e^{-3.62t} + A_2 e^{-1.38t} \quad \text{Ampere.}$$

Forced response

$$i_f(t) = \frac{1}{s^2 + 5s + 5} \times 1e^0$$

$$i_f(t) = \frac{1}{0^2 + 0 \times 5 + 5} = \frac{1}{5} = 0.2 \text{ Ampere}$$

Total Response.

$$i(t) = i_n(t) + i_f(t)$$

$$i(t) = A_1 e^{-3.62t} + A_2 e^{-1.38t} + 0.2$$

To find A_1 & A_2 initial condition is used ie, $i(0) = -0.2 \text{ A}$.

from eqn (1)

$$V(0) = 4i(0) + 4 \frac{di(0)}{dt} \Rightarrow \frac{di(0)}{dt} = \frac{V(0) - 4i(0)}{4}$$

$$\frac{di(0)}{dt} = \frac{-\frac{4}{5} - 4 \times (-\frac{1}{5})}{4} = \frac{0}{5 \times 4} = 0 \text{ A/sec.}$$

from (2)

$$i(0) = -0.2 = A_1 + A_2 + 0.2 \Rightarrow A_1 + A_2 = -0.4 \quad (3)$$

$$\frac{di(t)}{dt} = -3.62A_1 e^{-3.62t} - 1.38A_2 e^{-1.38t}$$

$$\frac{di(0)}{dt} = -3.62A_1 - 1.38A_2$$

$$0 = -3.62A_1 - 1.38A_2 \Rightarrow \cancel{A_2} 3.62A_1 + 1.38A_2 = 0 \quad (4)$$

on Solving (3) & (4)

$$A_1 = 0.246, \quad A_2 = -0.646$$

Hence

Ans: $i(t) = 0.246 e^{-3.62t} + (-0.646) e^{-1.38t} + 0.2 A$

Q6 Solution:-

Given at $t=0^+$ the ckt is at steady state

at $t=0$, the voltage source is disconnected and the current source is connected.

$$V(0) = 10V \quad \& \quad i(0) = 0A$$

Consider the circuit after time $t=0$. The first differential eqn is obtained by using KVL around the RLC mesh

$$L \frac{di}{dt} + Ri = V$$

The second differential eqn is obtained by using KCL at the node at top of capacitor

$$C \frac{dV}{dt} + i = i_s$$

We rewrite the two first-order differential eqn

$$\frac{di}{dt} + \frac{R}{L} i - \frac{V}{L} = 0$$

and

$$\frac{dV}{dt} + \frac{i}{C} = \frac{i_s}{C}$$

substituting the values, we have

$$\frac{di}{dt} + 3i - V = 0 \quad \text{--- (1)}$$

&

$$\frac{dV}{dt} + 2i = 2i_s \quad \text{--- (2)}$$

using operator $s = d/dt$

$$(s+3)i - V = 0 \quad \text{--- (4)}$$

$$2i + sV = 2i_s \quad \text{--- (5)}$$

The characteristic eqn obtained from the determinant is

$$(s+3)s + 2 = 0$$

$$s^2 + 3s + 2 = 0$$

Thus roots are

$$s_1 = -2 \quad \& \quad s_2 = -1$$

To solve for $i(t)$ at $t > 0$, we use cramer rule to solve eq (4) & (5)

$$i = \frac{2i_s}{s^2 + 3s + 2}$$

Therefore, the differential eqn is

Therefore, differential eqn is

$$\frac{d^2 i}{dt^2} + 3 \frac{di}{dt} + 2i = 2i_s \quad \text{--- (6)}$$

The natural response is

$$i_n = A_1 e^{-t} + A_2 e^{-2t}$$

We assume the forced response is of form

$$i_f = B e^{-3t}$$

Substituting i_f in eq (6)

$$(9B e^{-3t}) + 3(-3B e^{-3t}) + 2B e^{-3t} = 2(2e^{-3t})$$

$$9B - 9B + 2B = 4 \Rightarrow B = 2$$

therefore

$$i_f = 2e^{-3t}$$

The Complete response is

$$i = A_1 e^{-t} + A_2 e^{-2t} + 2e^{-3t}$$

As $i(0) = 0$

$$0 = A_1 + A_2 + 2 \quad \text{--- (7)}$$

We need to find $\frac{di(0)}{dt}$ from eq (1)

$$\frac{di}{dt} + 3i - v = 0$$

at $t = 0$,

$$\frac{di(0)}{dt} = -3i(0) + v(0) = 10$$

The derivative of complete response at $t = 0$ is

$$\frac{di(0)}{dt} = -A_1 - 2A_2 - 6$$

$$\text{as } \frac{di(0)}{dt} = 10$$

$$-A_1 - 2A_2 = 16 \quad \text{--- (8)}$$

using (7) & (8)

$A_1 = 12$ & $A_2 = -14$, Thus complete soln.

Ans: $i = 12e^{-t} - 14e^{-2t} + 2e^{-3t} \text{ Amp}$

Q7

Solution:

The source current is applied at $t=0$
 After $t=0$, the KCL eqn at the upper node is

$$i + \frac{V}{R} + C \frac{dV}{dt} = i_s \quad \rightarrow (1)$$

We know

$$V = L \frac{di}{dt} \quad \rightarrow (2)$$

So $\frac{dV}{dt} = L \frac{d^2 i}{dt^2}$

Using eq (1) & (2)

$$i + \frac{L}{R} \frac{di}{dt} + CL \frac{d^2 i}{dt^2} = i_s$$

Rearranging by dividing by LC

$$\frac{d^2 i}{dt^2} + \frac{1}{RC} \frac{di}{dt} + \frac{1}{LC} i = \frac{i_s}{LC}$$

Substituting the values we obtain.

$$\frac{d^2 i}{dt^2} + 7 \frac{di}{dt} + 6i = 48e^{-2t} \quad \rightarrow (3)$$

To obtain forced response, we assume

$$i_f = B e^{-2t}$$

Where B is to be determined.

Substituting assumed value in eq (3)

$$4B e^{-2t} + 7(-2B e^{-2t}) + 6B e^{-2t} = 48e^{-2t}$$

$$\text{or } (4 - 14 + 6)B e^{-2t} = 48e^{-2t}$$

$$\Rightarrow B = -12$$

Ans.

$$i_f = -12e^{-2t} \text{ Amp}$$