

Solutions to Tutorial Sheet-9

$$1. \quad I_D = I_s \left[\exp\left(\frac{V_D}{V_T}\right) - 1 \right] = 200 \times 10^{-9} \left[\exp\left(\frac{0.1}{0.026}\right) - 1 \right] = \mathbf{9.1625 \mu A}$$

$$2. (a) \quad V_{DD} = 5 \text{ V}, I = 5 \text{ mA}, V_T = 0.7 \text{ V}; V_R = V_{DD} - V_T = 5 - 0.7 = 4.3 \text{ V}$$


$$\therefore R = \frac{V_R}{I} = \frac{4.3}{5 \times 10^{-3}} = \mathbf{860 \Omega}$$

$$(b) \quad V_R = V_{DD} - V_T = 6 - 0.7 = 5.3 \text{ V}; \quad \therefore R = \frac{5.3}{5 \times 10^{-3}} = 1060 \Omega$$

$$\text{Power dissipated in resistance } R = I^2 R = (5 \times 10^{-3})^2 \times 1060 = \mathbf{26.5 \text{ mW}}$$

$$\text{Power dissipated in the diode} = IV_T = 5 \times 10^{-3} \times 0.7 = \mathbf{3.5 \text{ mW}}$$

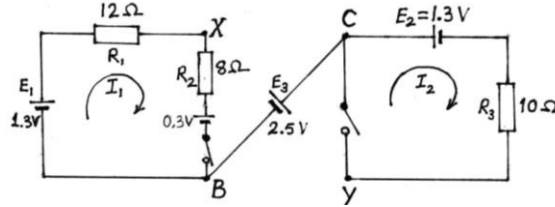3. Equivalent circuit is shown in figure.



Since diode D1 is forward biased ($0.3 \text{ V} < 1.3 \text{ V}$), it is replaced by a closed switch and a battery of 0.3 V . Diode D2 is reverse-biased, it is replaced by an open switch. Therefore, $I_2 = 0$. Now,

$$I_1 = \frac{1.3 - 0.3}{8 + 12} = 0.05 \text{ A}; \quad V_{XB} = V_{XA} + V_{AB} = I_1 R_2 + V_{AB} = 0.05 \times 8 + 0.3 = 0.4 + 0.3 = 0.7 \text{ V}$$

$$\text{Now, } V_{CY} = I_2 R_3 + E_2 = 0 \times 10 + 1.3 = 1.3 \text{ V}; \quad \therefore V_{XY} = V_{XB} + V_{BC} + V_{CY} = 0.7 - 2.5 + 1.3 = \mathbf{-0.5 \text{ V}}$$

4. Diodes are forward biased and hence each diode can be replaced by a resistance of 10Ω and a battery of 0.6 V .

$$I_D = \frac{5 - 0.6 - 0.6}{100 + 10 + 10} = \frac{5 - 1.2}{120} = \mathbf{31.667 \text{ mA}}$$

$$V_D = I_D (r_f + r_f) + V_T + V_T = 31.667 \times 10^{-3} (10 + 10) + 0.6 + 0.6 = \mathbf{1.833 \text{ V}}; \quad V_o = I_D \times 100 = \mathbf{3.167 \text{ V}}$$

5. Diode is reverse-biased, and hence it is an open-circuit. Hence,

$$\text{Net resistance} = \left[8 + \left(\frac{6 \times 3}{6 + 3} \right) \right] = 10 \Omega; \quad \therefore I = \frac{15}{10} = 1.5 \text{ A}; \quad \therefore I_1 = 1.5 \left(\frac{6}{6 + 3} \right) = \mathbf{1 \text{ A}}$$

6. The diode is now forward-biased and therefore it behaves as a short-circuit. Hence, the current through 3Ω resistor is **zero**.

$$7. \quad I = \frac{1 - 0.3}{20 + 8} = \frac{0.7}{28} = \mathbf{25 \text{ mA}}$$

8. Diode D2 is reversed biased, hence it will not conduct. Assume that the diode D1 is removed.

$$\therefore V_B = \left(\frac{100}{100 + 50} \right) 7.5 \text{ V} = 7.5 \left(\frac{2}{3} \right) \text{ V} \quad \text{and} \quad V_D = \left(\frac{300}{300 + 150} \right) 7.5 \text{ V} = 7.5 \left(\frac{2}{3} \right) \text{ V}$$

$$\text{Since } V_B \approx V_D, \text{ the diode } D_1 \text{ also does not conduct. } \therefore I_2 = \frac{7.5}{150 + 300} = \frac{7.5}{450} = \mathbf{16.66 \text{ mA}}$$

9. (a) When $V_i = 0 \text{ V}$, all diodes are likely to be forward-biased. Conduction through diode D1 brings the point A to 0.6 V . For the diodes D2, D3 and D4 to conduct, the minimum voltage required at point A is $0.6 \text{ V} + 0.6 \text{ V} + 0.6 \text{ V} = 1.8 \text{ V}$. Since $V_A = 0.6 \text{ V}$, these diodes do not conduct. So, these can be treated as open-circuit. Therefore, $V_o = \mathbf{0.6 \text{ V}}$.

$$\therefore I = \frac{10 - 0.6}{2 \times 10^3} = \mathbf{4.7 \text{ mA}}$$

(b) When $V_i = 2 \text{ V}$, the diodes D2, D3 and D4 conduct. This makes the voltage at point A as $V_A = 0.6 + 0.6 + 0.6 = 1.8 \text{ V}$. This makes the diode D1 reverse-biased and hence it cannot conduct.

$$\therefore V_o = \mathbf{1.8 \text{ V}} \quad \text{and} \quad I = \frac{10 - 1.8}{2 \times 10^3} = \frac{8.2}{2} = \mathbf{4.1 \text{ mA}}$$