 


Single Cycle Datapath

The Big Picture: Where are We?

- The Five Classic Components of a Computer




The Performance Perspective

- Performance of a machine was determined by:
 - Instruction count
 - Clock cycle time
 - Clock cycles per instruction
- Processor design (datapath and control) will determine:
 - Clock cycle time
 - Clock cycles per instruction

The MIPS Instruction Formats

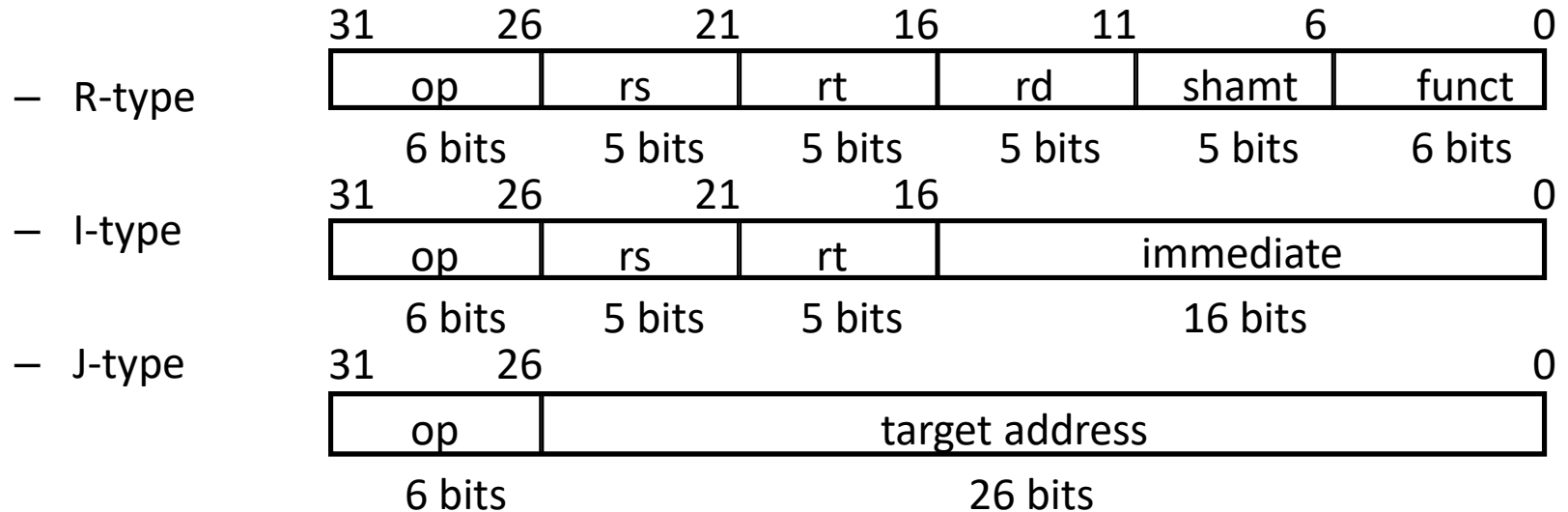- All MIPS instructions are 32 bits long. The three instruction formats:




- The different fields are:
 - op: operation of the instruction
 - rs, rt, rd: the source and destination register specifiers
 - shamt: shift amount
 - funct: selects the variant of the operation in the “op” field
 - address / immediate: address offset or immediate value
 - target address: target address of the jump instruction

The MIPS Subset


- ADD and subtract

- add rd, rs, rt
- sub rd, rs, rt

 

- OR Immediate:

- ori rt, rs, imm16

 

- LOAD and STORE


- lw rt, rs, imm16
- sw rt, rs, imm16

- BRANCH:


- beq rs, rt, imm16

- JUMP:


- j target

 

An Abstract View of the Implementation

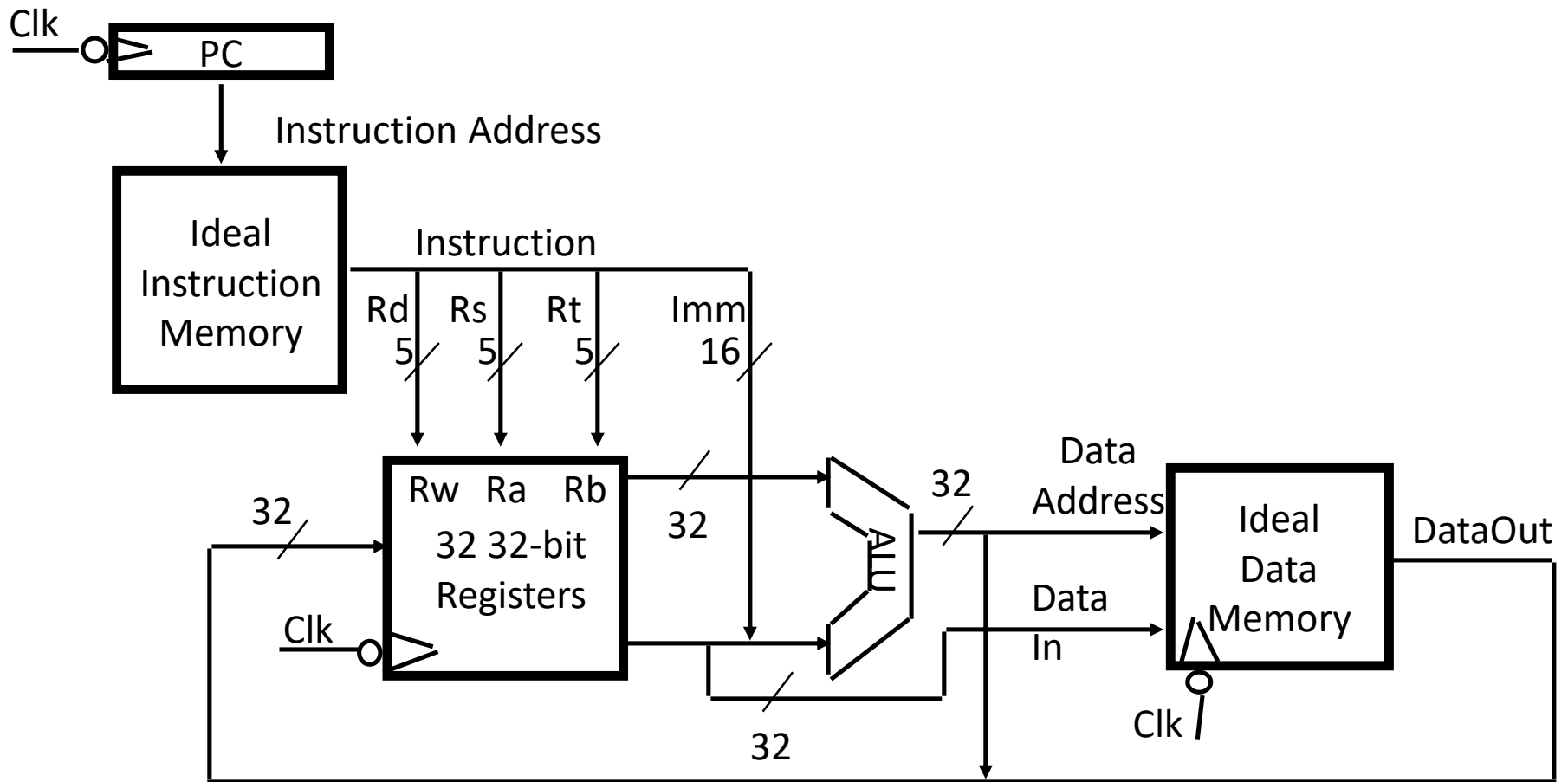


Clocking Methodology

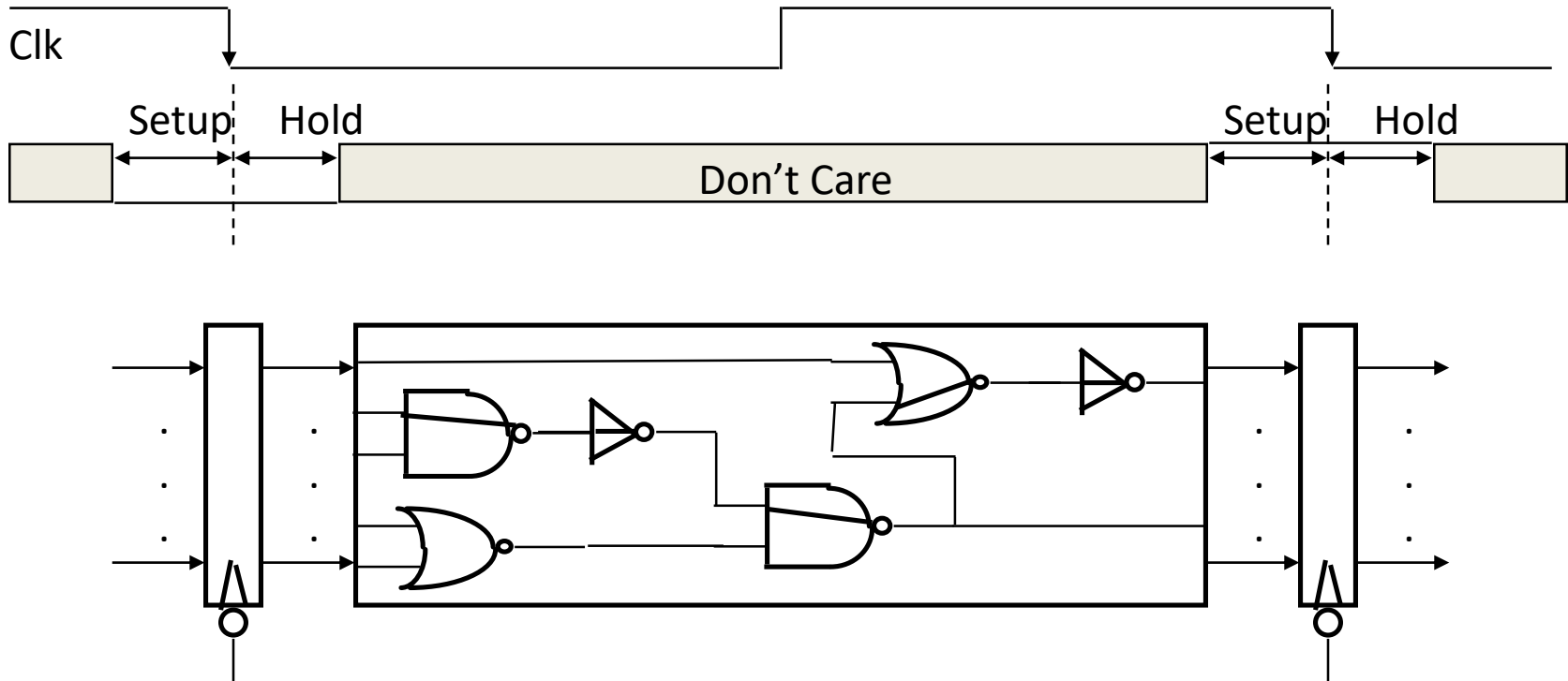

- All storage elements are clocked by the same clock edge
- Cycle Time = CLK-to-Q + Longest Delay Path + Setup + Clock Skew

An Abstract View of the Critical Path

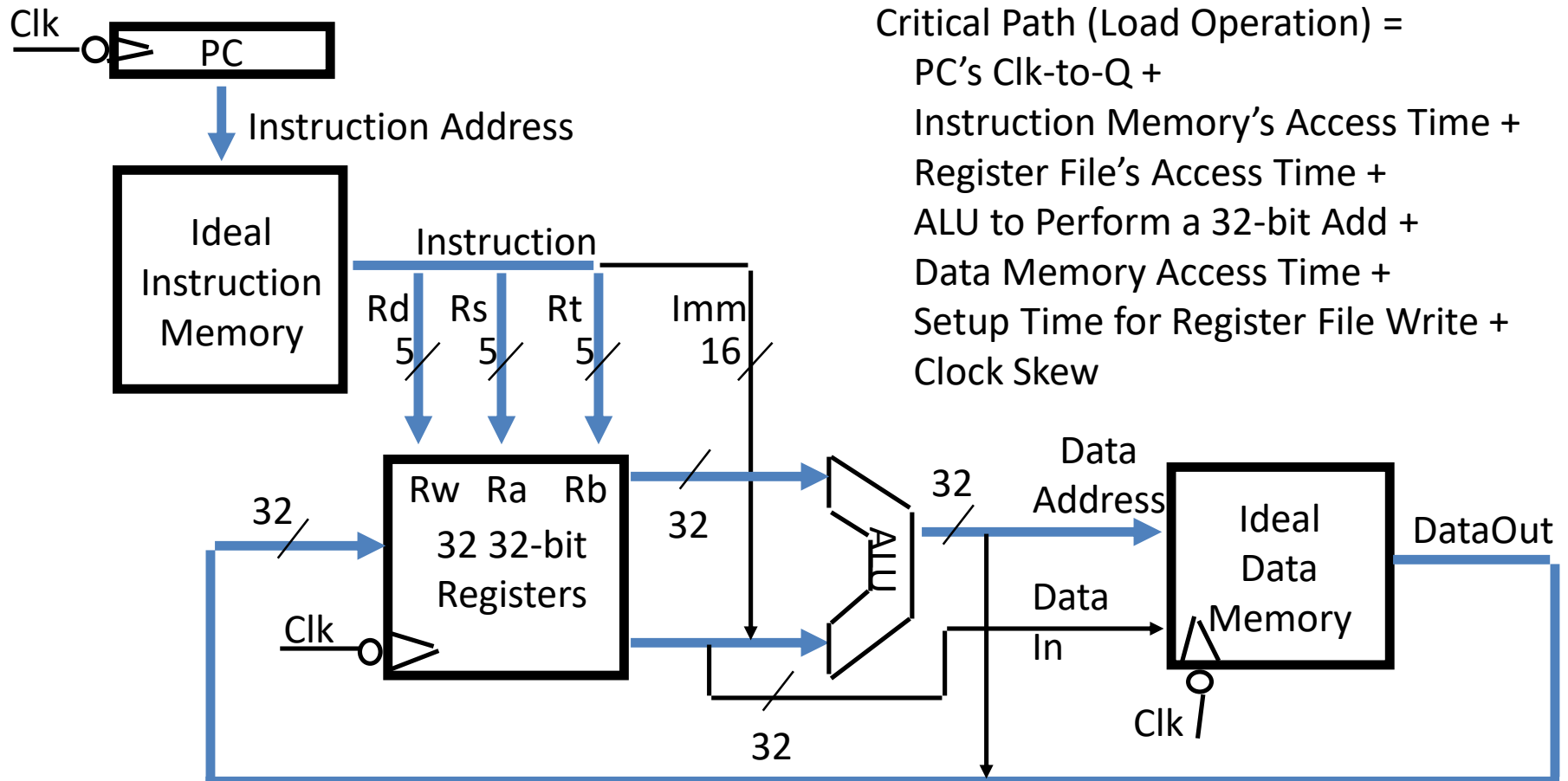- Register file and ideal memory:
 - The CLK input is a factor ONLY during write operation
 - During read operation, behave as combinational logic:
 - Address valid => Output valid after “access time.”



The Steps of Designing a Processor

- Instruction Set Architecture => Register Transfer Language
- Register Transfer Language => Datapath Design
 - Datapath components
 - Datapath interconnect
- Datapath components => Control signals
- Control signals => Control logic => Control Unit Design

RTL Example 1: The ADD Instruction

- add rd, rs, rt
 - mem[PC] Fetch the instruction from memory
 - $R[rd] \leftarrow R[rs] + R[rt]$ The ADD operation
 - $PC \leftarrow PC + 4$ Calculate the next instruction's address

RTL Example 2: The Load Instruction

- **lw rt, rs, imm16**

- mem[PC]

Fetch the instruction
from memory

- Addr <- R[rs] + SignExt(imm16)

Calculate the memory
address

- R[rt] <- Mem[Addr]


Load the data into the
register

- PC <- PC + 4


Calculate the next
instruction's address

Need of Combinational Logic Elements


- Adder

 

- MUX

 


- ALU

 


Storage Element: Register

 - Register
 - Similar to the D Flip Flop except
 - N-bit input and output
 - Write Enable input
 - Write Enable:
 - 0: Data Out will not change
 - 1: Data Out will become Data In




Storage Element: Idealized Memory

- Memory (idealized)
 - One input bus: Data In
 - One output bus: Data Out
- Memory word is selected by:
 - Write Enable = 0: Address selects the word to put on Data Out
 - Write Enable = 1: address selects the memory memory word to be written via the Data In bus
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block:
 - Address valid => Data Out valid after “access time.”

 


Storage Element: Register File

- Register File consists of 32 registers:
 - Two 32-bit output busses:
busA and busB
 - One 32-bit input bus: busW
- Register is selected by:
 - RA selects the register to put on busA
 - RB selects the register to put on busB
 - RW selects the register to be written via busW when Write Enable is 1
- Clock input (CLK)
 - The CLK input is a factor ONLY during write operation
 - During read operation, behaves as a combinational logic block: RA or RB valid => busA or busB valid after “access time.”

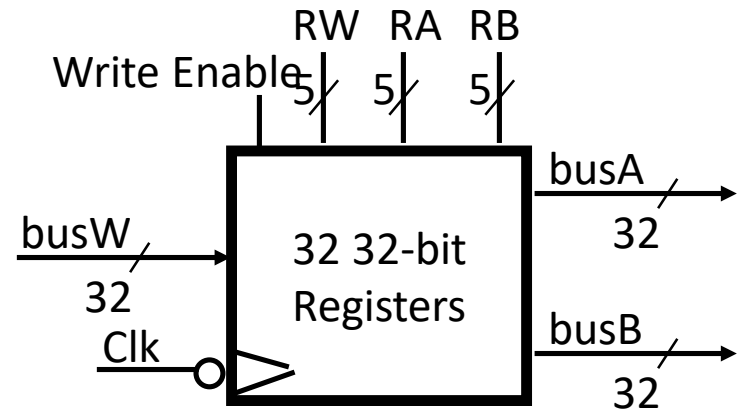

Overview of the Instruction Fetch Unit

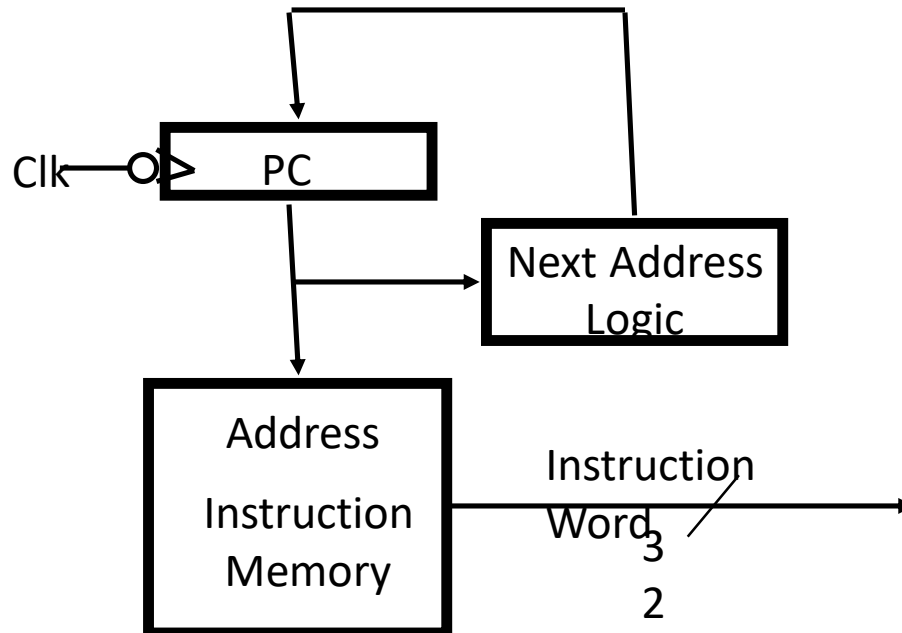- The common RTL operations
 - Fetch the Instruction: $\text{mem}[\text{PC}]$
 - Update the program counter:
 - Sequential Code: $\text{PC} \leftarrow \text{PC} + 4$
 - Branch and Jump $\text{PC} \leftarrow \text{“something else”}$




RTL: The ADD Instruction



- add rd, rs, rt
 - mem[PC] Fetch the instruction from memory
 - $R[rd] \leftarrow R[rs] + R[rt]$ The ADD operation
 - $PC \leftarrow PC + 4$ Calculate the next instruction's address

Datapath for Register-Register Operations

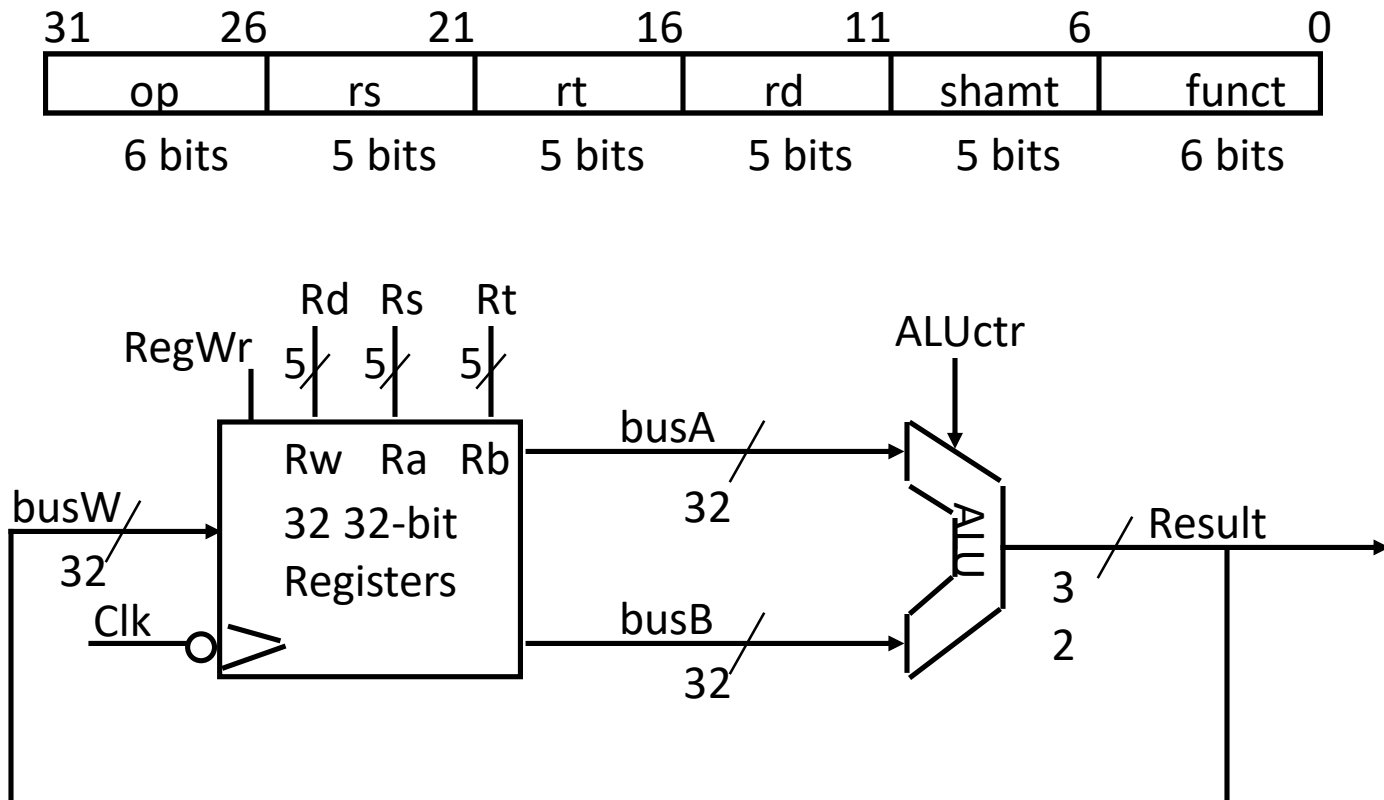
- $R[rd] \leftarrow R[rs] \text{ op } R[rt]$ Example: add rd, rs, rt
 - Ra, Rb, and Rw comes from instruction's rs, rt, and rd fields
 - ALUctr and RegWr: control logic after decoding the instruction



Register-Register Timing

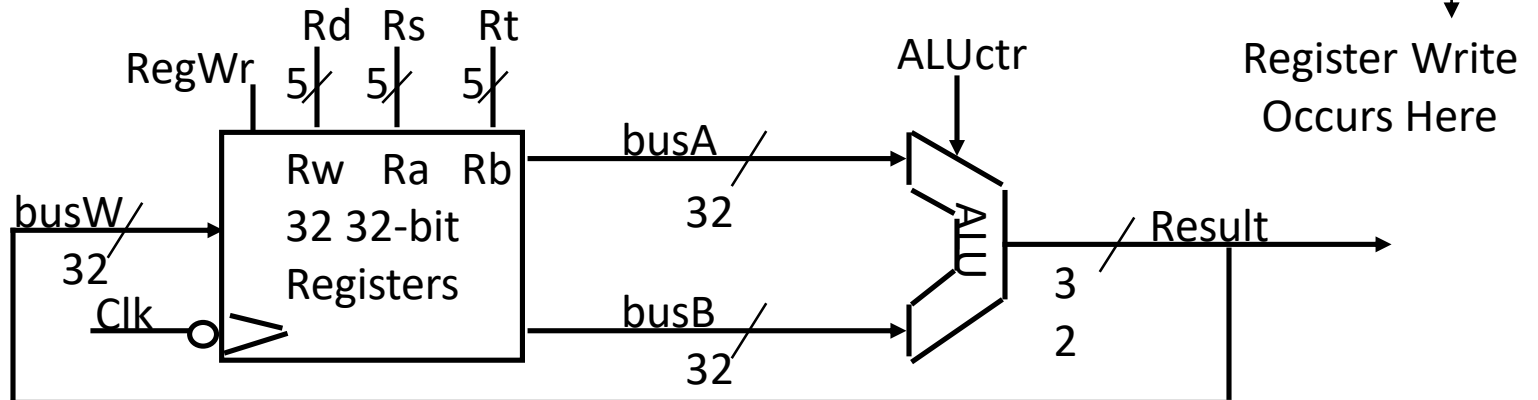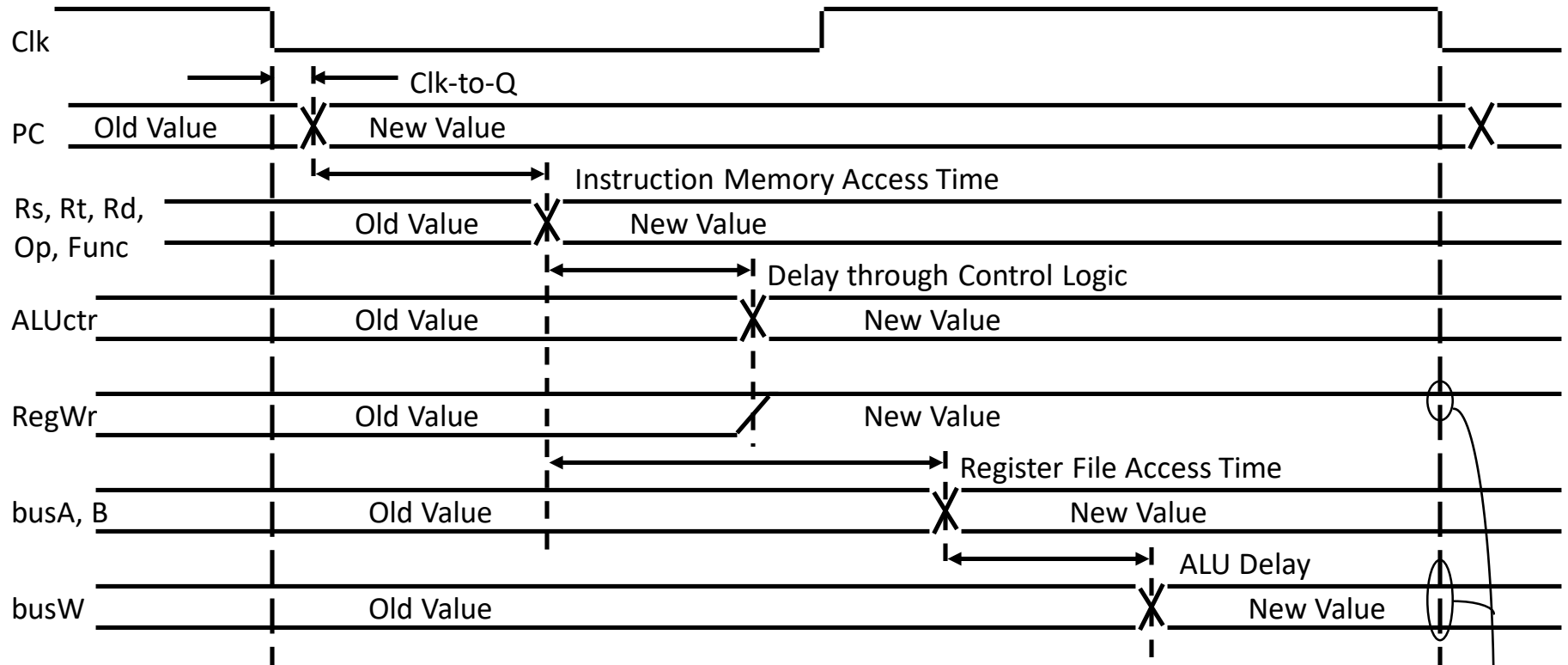


RTL: The OR Immediate Instruction

 



- ori rt, rs, imm16

 - mem[PC] Fetch the instruction from memory
- $R[rt] \leftarrow R[rs] \text{ OR ZeroExt}(\text{imm16})$ The OR operation
- $PC \leftarrow PC + 4$ Calculate the next instruction's address




Datapath for Logical Operations with Immediate

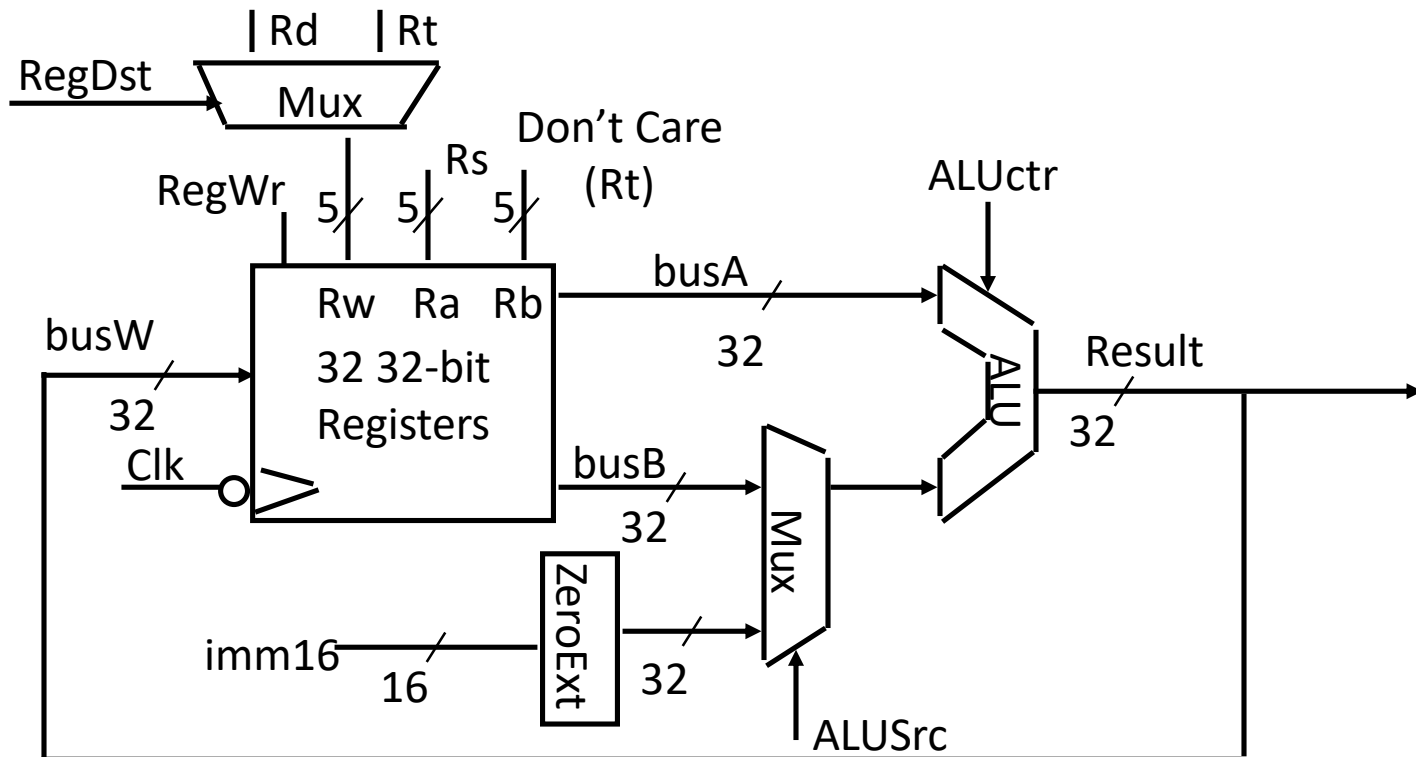 
- $R[rt] \leftarrow R[rs] \text{ op ZeroExt}[imm16]$ Example: `ori rt, rs, imm16`



RTL: The Load Instruction


 


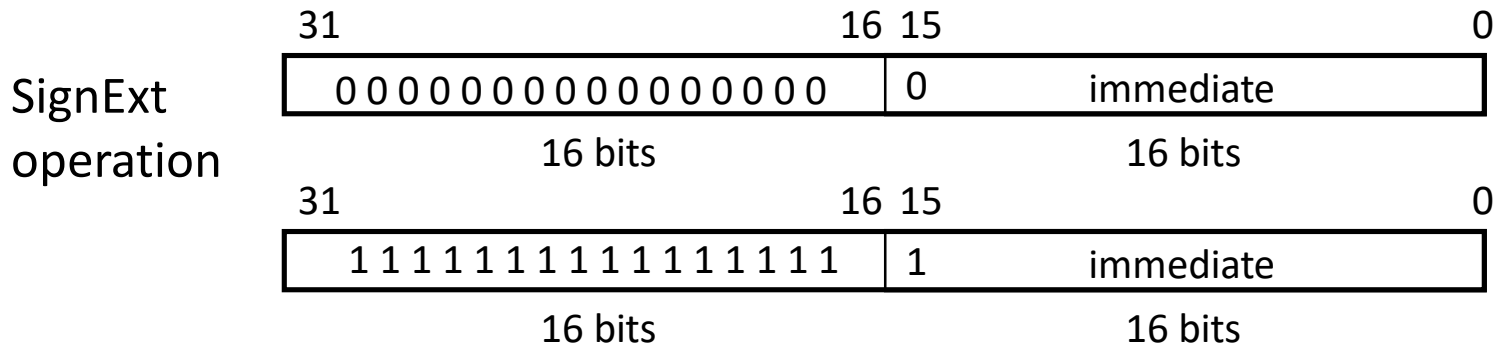- lw rt, rs, imm16 6 bits 5 bits 5 bits 16 bits
 - mem[PC] Fetch the instruction from memory
 - Addr <- R[rs] + SignExt(imm16) Calculate the memory address
 - R[rt] <- Mem[Addr] Load the data into the register
 - PC <- PC + 4 Calculate the next instruction's address




Datapath for Load Operations

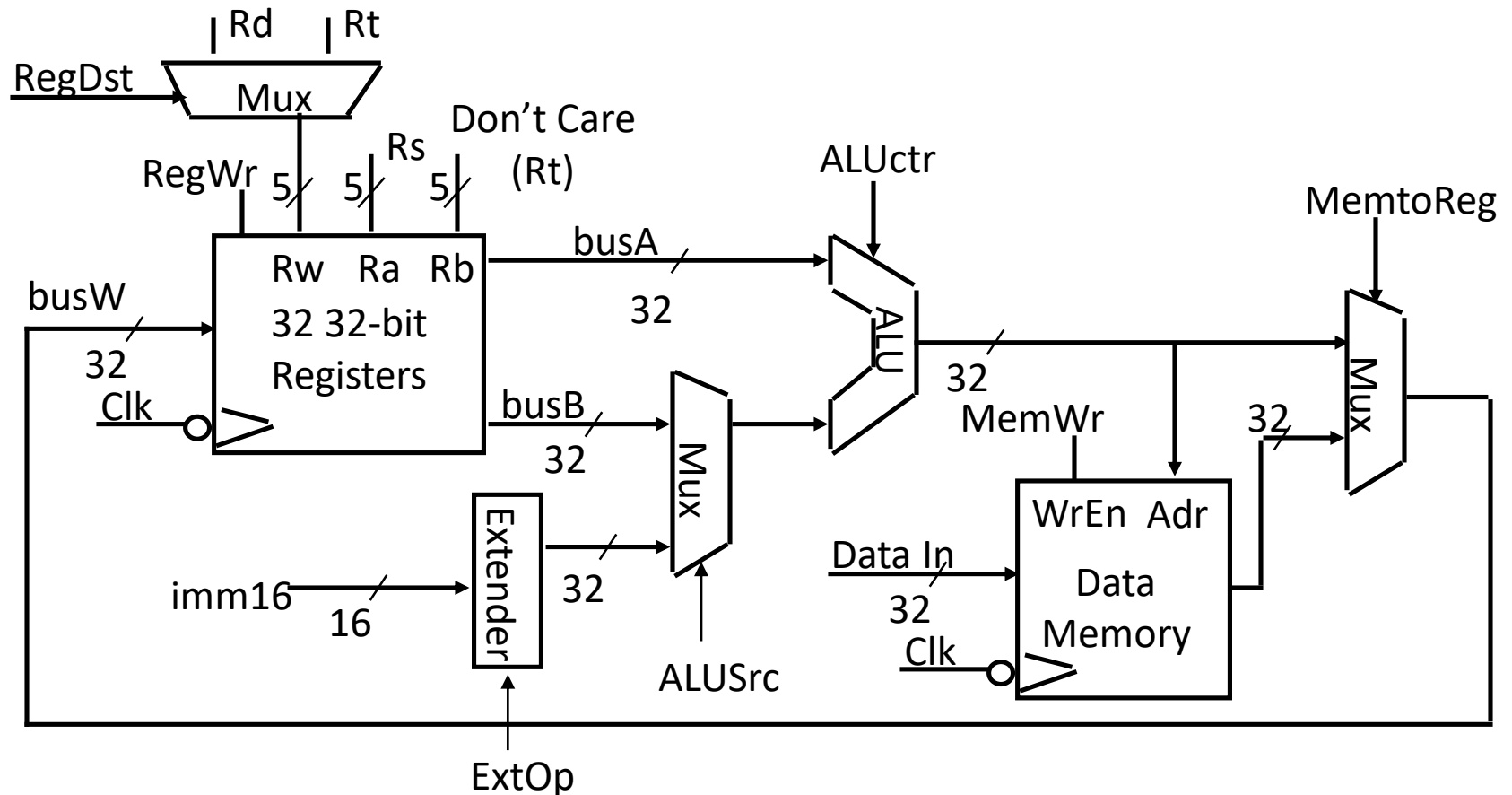 - $R[rt] \leftarrow \text{Mem}[R[rs] + \text{SignExt}[\text{imm16}]]$ Example: `lw rt, rs, imm16`





RTL: The Store Instruction

 


- `sw rt, rs, imm16`
 - `mem[PC]` Fetch the instruction from memory
 - `Addr <- R[rs] + SignExt(imm16)` Calculate the memory address
 - `Mem[Addr] <- R[rt]` Store the register into memory
 - `PC <- PC + 4` Calculate the next instruction's address

Datapath for Store Operations

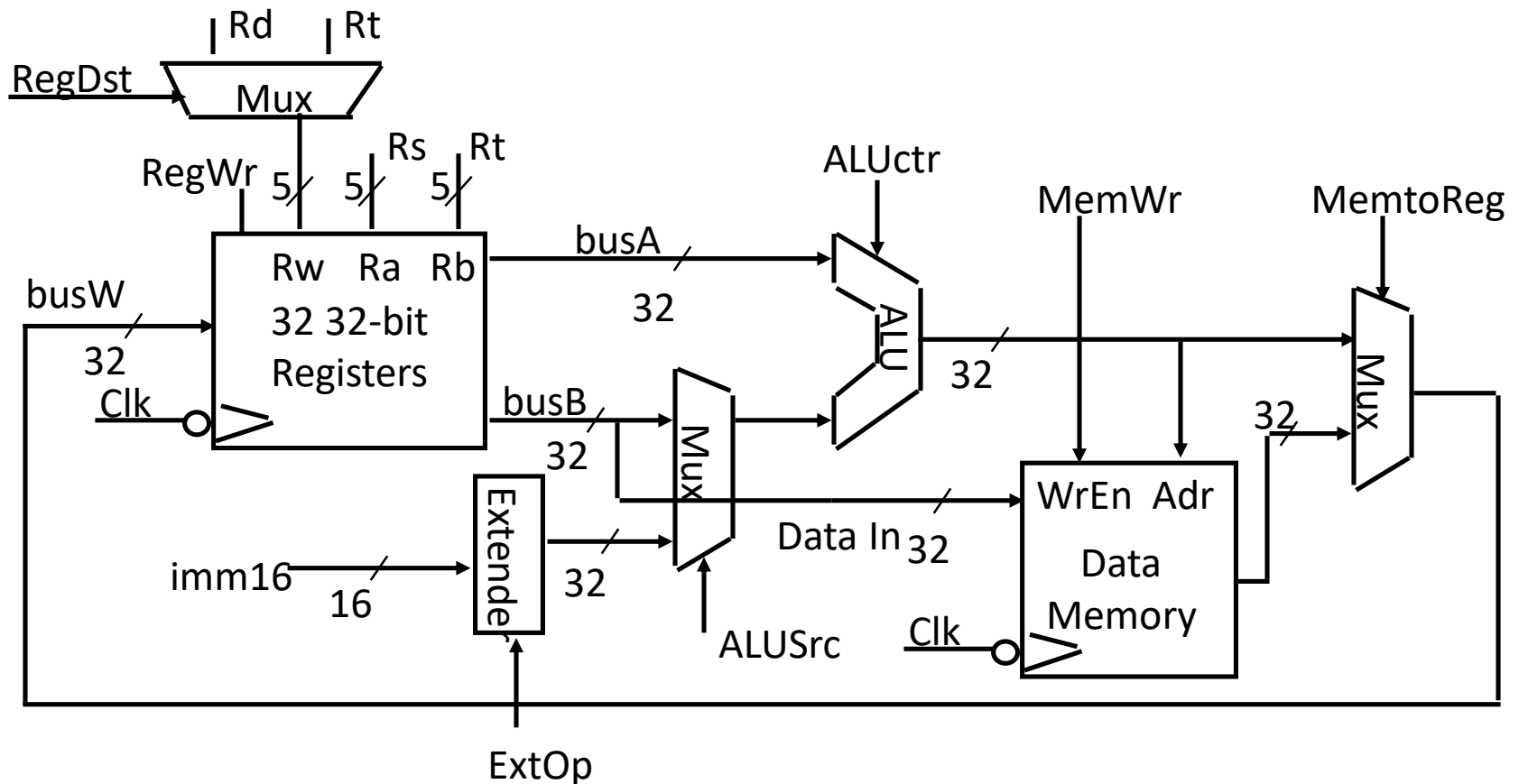 - Mem[R[rs] + SignExt[imm16] <- R[rt]] Example: sw rt, rs, imm16



RTL: The Branch Instruction

 


- beq rs, rt, imm16
 - mem[PC] Fetch the instruction from memory
 - Cond <- R[rs] - R[rt] Calculate the branch condition
 - if (COND eq 0) Calculate the next instruction's address

PC <- PC + 4 + (SignExt(imm16) x 4)
else PC <- PC + 4

Datapath for Branch Operations

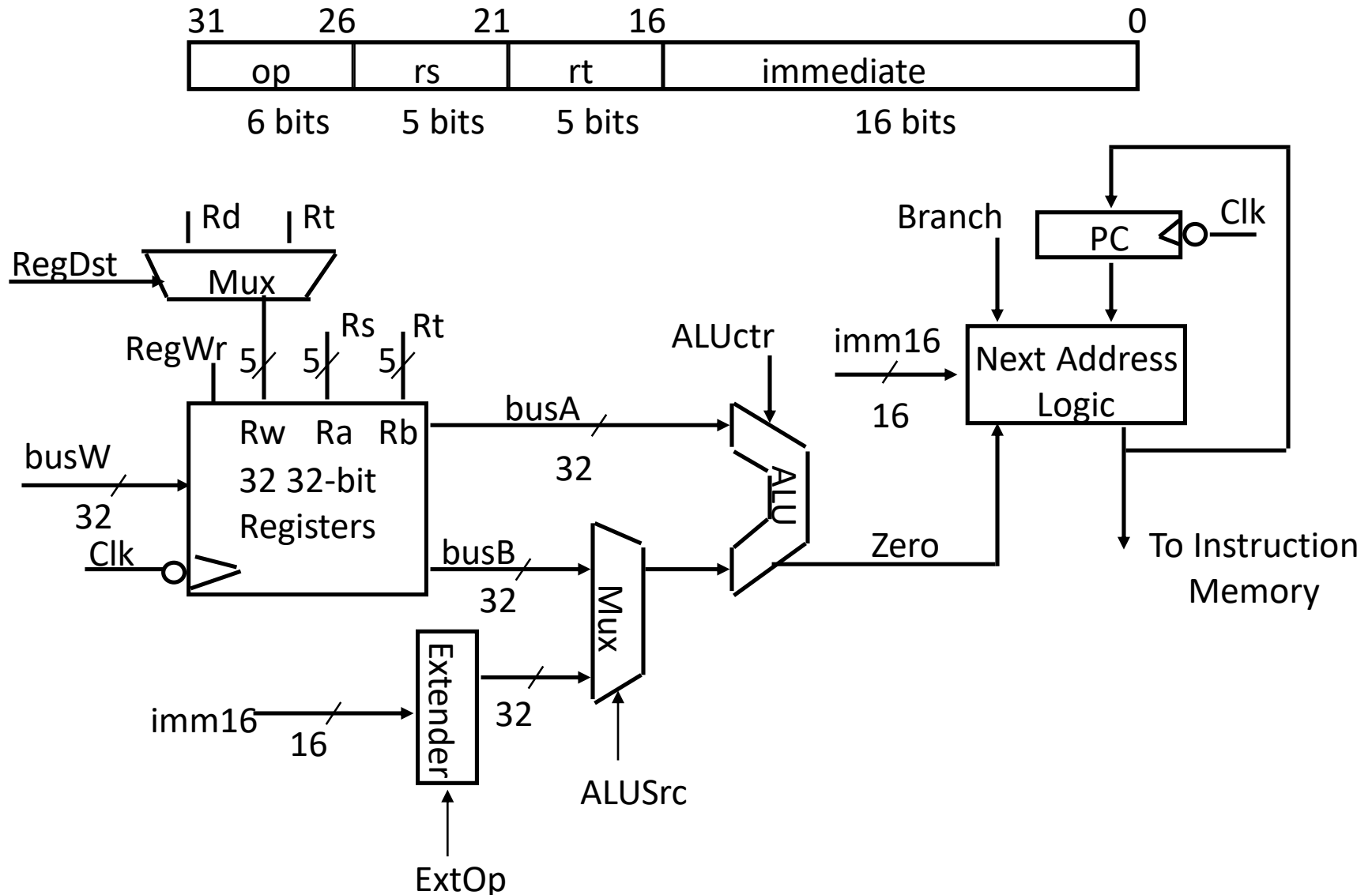- `beq rs, rt, imm16` We need to compare Rs and Rt!




Binary Arithmetics for the Next Address

- In theory, the PC is a 32-bit byte address into the instruction memory:
 - Sequential operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4$
 - Branch operation: $PC\langle 31:0 \rangle = PC\langle 31:0 \rangle + 4 + \text{SignExt}[\text{Imm16}] * 4$
- The magic number “4” always comes up because:
 - The 32-bit PC is a byte address
 - And all our instructions are 4 bytes (32 bits) long
- In other words:
 - The 2 LSBs of the 32-bit PC are always zeros
 - There is no reason to have hardware to keep the 2 LSBs
- In practice, we can simplify the hardware by using a 30-bit $PC\langle 31:2 \rangle$:
 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
 - Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
 - In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat “00”


Next Address Logic: Expensive and Fast Solution

 - Using a 30-bit PC:
 - Sequential operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1$
 - Branch operation: $PC\langle 31:2 \rangle = PC\langle 31:2 \rangle + 1 + \text{SignExt}[\text{Imm16}]$
 - In either case: Instruction Memory Address = $PC\langle 31:2 \rangle$ concat "00"




Next Address Logic: Cheap and Slow Solution

 - Why is this slow?
 - Cannot start the address add until Zero (output of ALU) is valid
- Does it matter that this is slow in the overall scheme of things?
 - Probably not here. Critical path is the load operation.




RTL: The Jump Instruction

 

- j target
 - mem[PC] Fetch the instruction from memory
 - $PC\langle 31:2 \rangle \leftarrow PC\langle 31:28 \rangle \text{ concatenate target}\langle 25:0 \rangle$
Calculate the next instruction's address


Instruction Fetch Unit

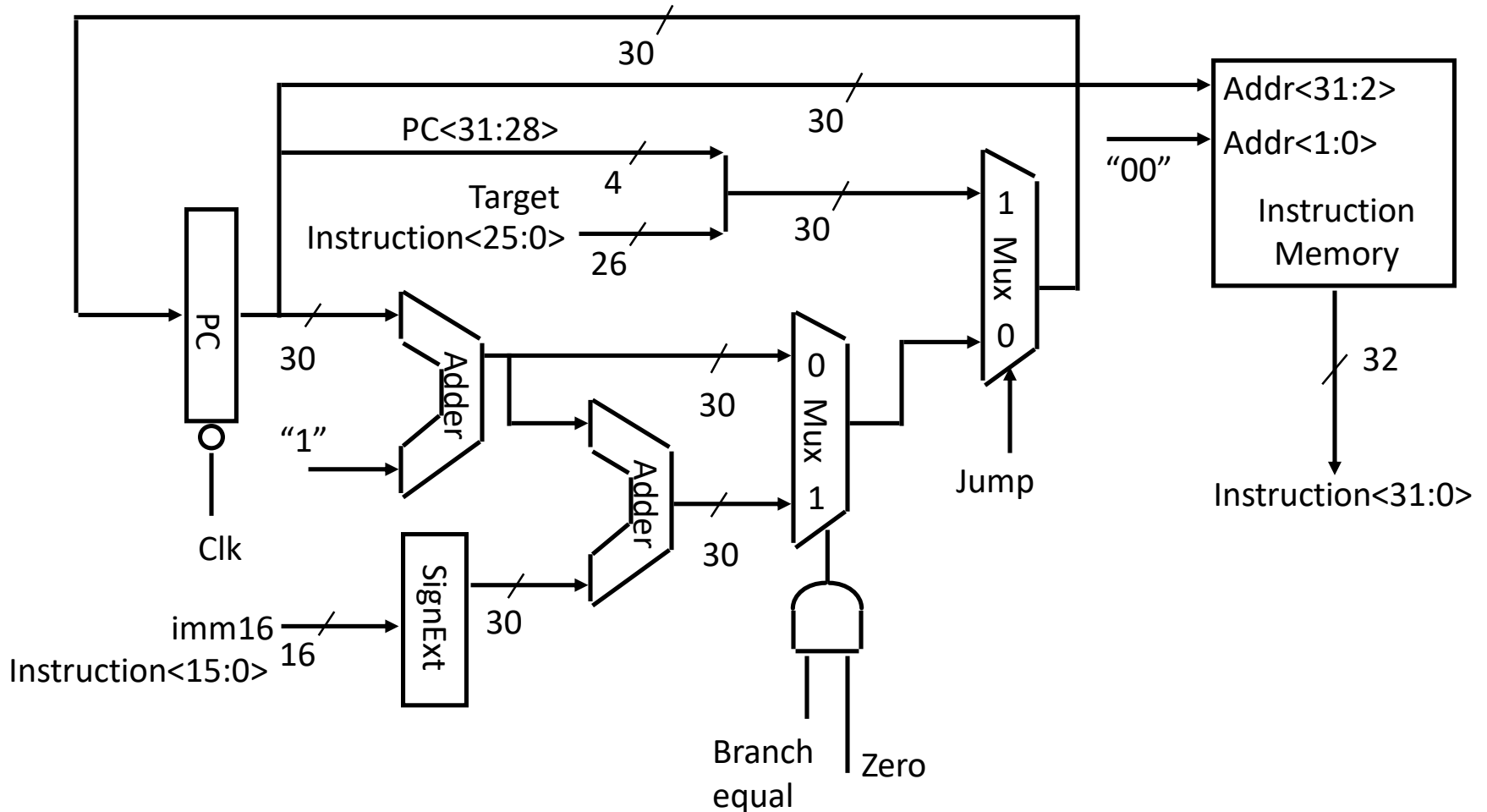- j target
 - $PC\langle 31:2 \rangle \leftarrow PC\langle 31:28 \rangle \text{ concat target}\langle 25:0 \rangle$



Putting it All Together: A Single Cycle Datapath

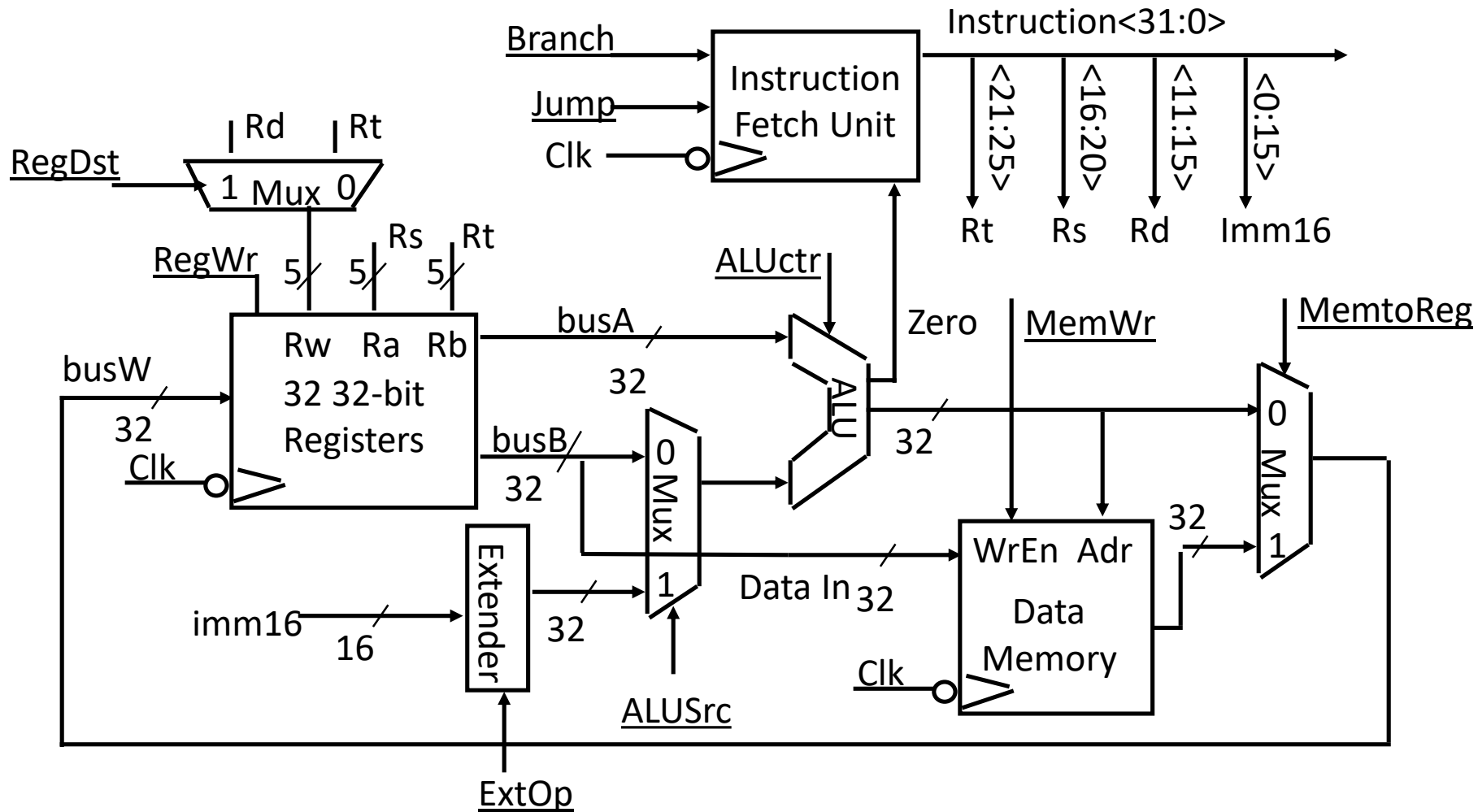- We have everything except control signals (underline)



References

- John L. Hennessy and David A Patterson, Computer Architecture: A quantitative Approach, Morgan Kaufmann / Elsevier, Sixth Edition, 23rd November 2017