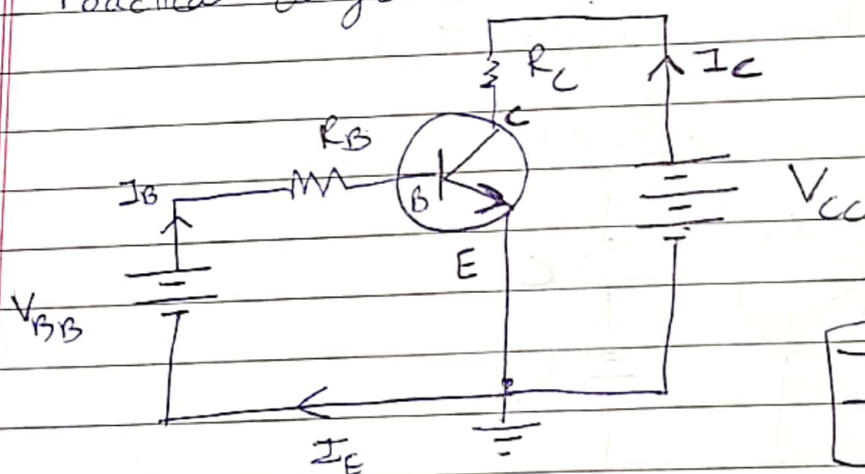


* Transistor works when EB is forward biased & CB is reverse biased

⇒ Emitter ⇒ Heavily doped & moderate size
 Base ⇒ light doped & thin
 Collector ⇒ Moderately doped & max size

Practical diagram:



Imp:

$$I_E = I_C + I_B$$

Some Imp formula:

1) $I_C = \alpha I_E$ $\Rightarrow \alpha \Rightarrow$ fraction of electron diffuse across Base region
 $I_B = (1 - \alpha) I_E$

Current gain (β): $\frac{I_c}{I_b} = \frac{\alpha}{1-\alpha}$

↓
Temperature
& voltage dependent

Hybrid Model: (H-parameter Mode)
↳ Equivalent mode of transistor


For Transistor

$h_{11} = h_i \Rightarrow$ Input Impedance

$h_{12} = h_r \Rightarrow$ Reverse Transfer

$h_{21} = h_f \Rightarrow$ forward Transfer

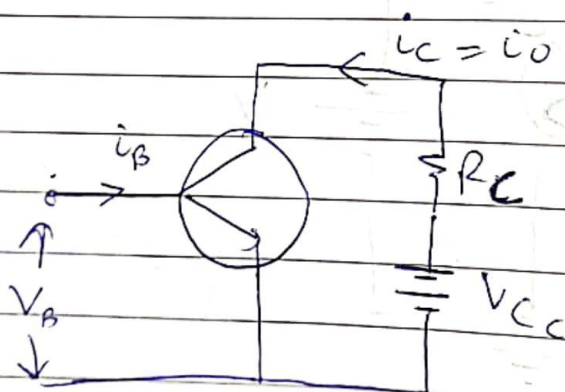
$h_{22} = h_o \Rightarrow$ Output Impedance



For Transistor

$$V_B = h_i I_B + h_r V_C$$

$$I_C = h_f I_B + h_o V_C$$

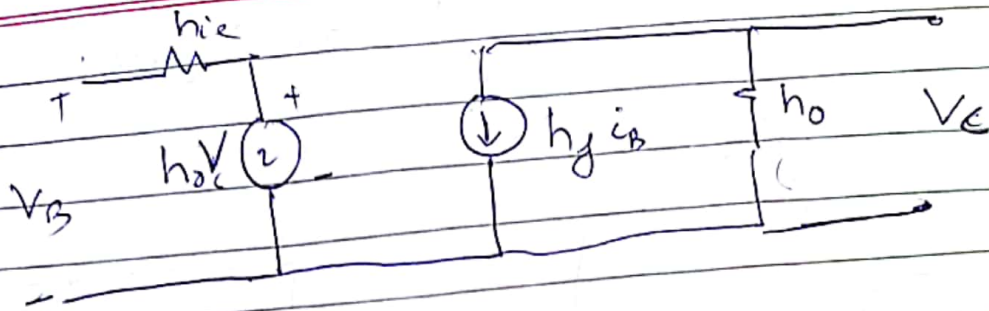


So, here

$i_1 \rightarrow i_B$
$V_1 \rightarrow V_{BE}$
$i_2 \rightarrow i_C$
$V_2 \rightarrow V_{CE}$

used -
(for higher frequency)

Hybrid - π Model

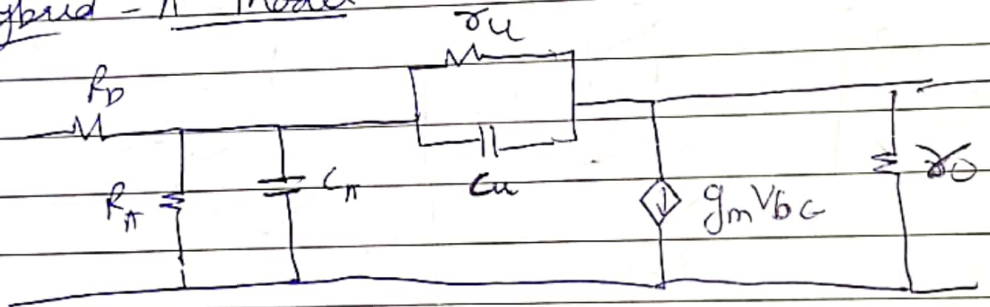Can be used for low as well as high frequency



↳ For high frequency


$$g_m (\text{trans conductance}) = \frac{I_{out}}{V_{in}} \bigg|_{V_{out}=0} = \frac{i_c}{V_{be}} \bigg|_{V_{ce}=0}$$

$$= \frac{I_C}{V_T} = \frac{I_C}{26\text{mV}} \text{ At } 300\text{K}$$


$$r_{\pi} = \frac{\beta}{g_m} = \frac{V_T}{I_B} = \frac{26\text{mV}}{I_B}$$

~~Ro~~

for Transistor at low frequency

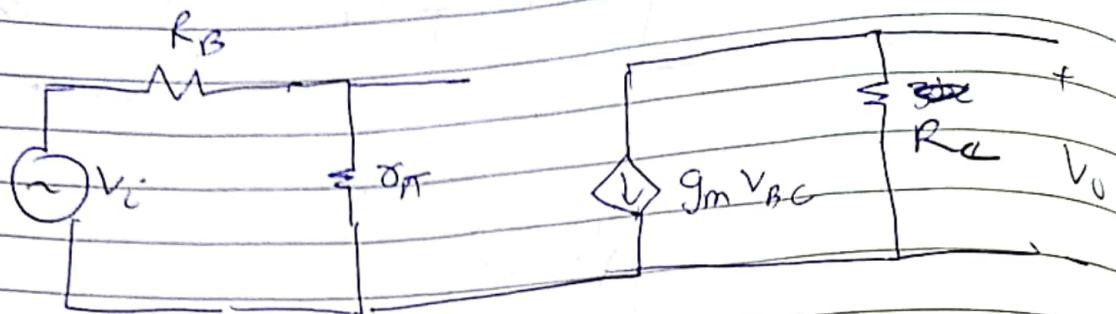

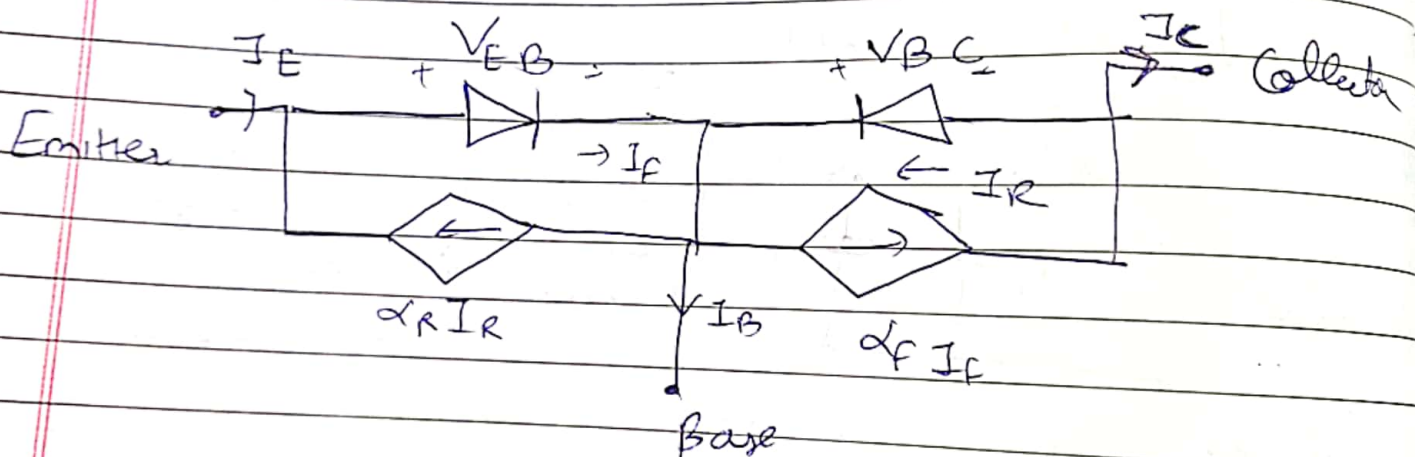Eber-Moll's model \rightarrow Not Imp for Exam Acc. to Man




$$I_E = I_F - \alpha_R I_R = I_E^0 \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) - \alpha_R I_C^0 \left(e^{\frac{V_{CB}}{V_T}} - 1 \right)$$

$$I_C = \alpha_F I_F - I_R = \alpha_F I_E^0 \left(e^{\frac{V_{BE}}{V_T}} - 1 \right) - I_C^0 \left(e^{\frac{V_{CB}}{V_T}} - 1 \right)$$

$$I_B = I_E - I_C$$

Common Emitter Configuration : Power gain
Common Base Config : Voltage gain
Common Collector Config : Current gain

Common base Configuration

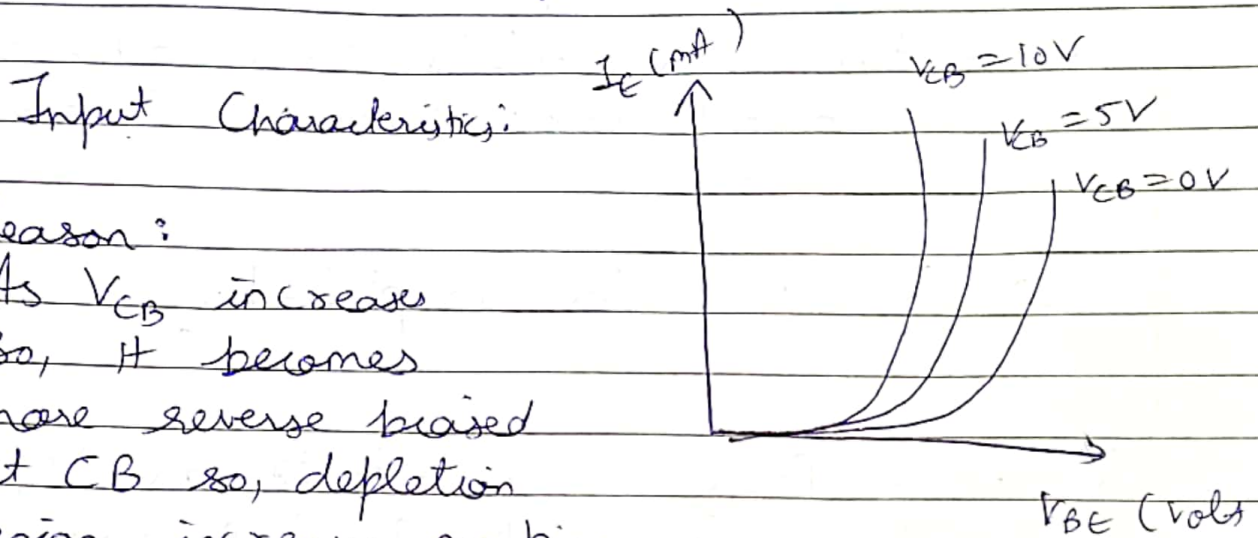


Reason:

As V_{CB} increases
so, it becomes
more reverse biased
at CB so, depletion
region increases making
the size of B more smaller
So, know less voltage is required to forward
bias emitter-base junction thus increasing I_E
& shifting the graph towards left

Output Characteristics

~~Reason:~~

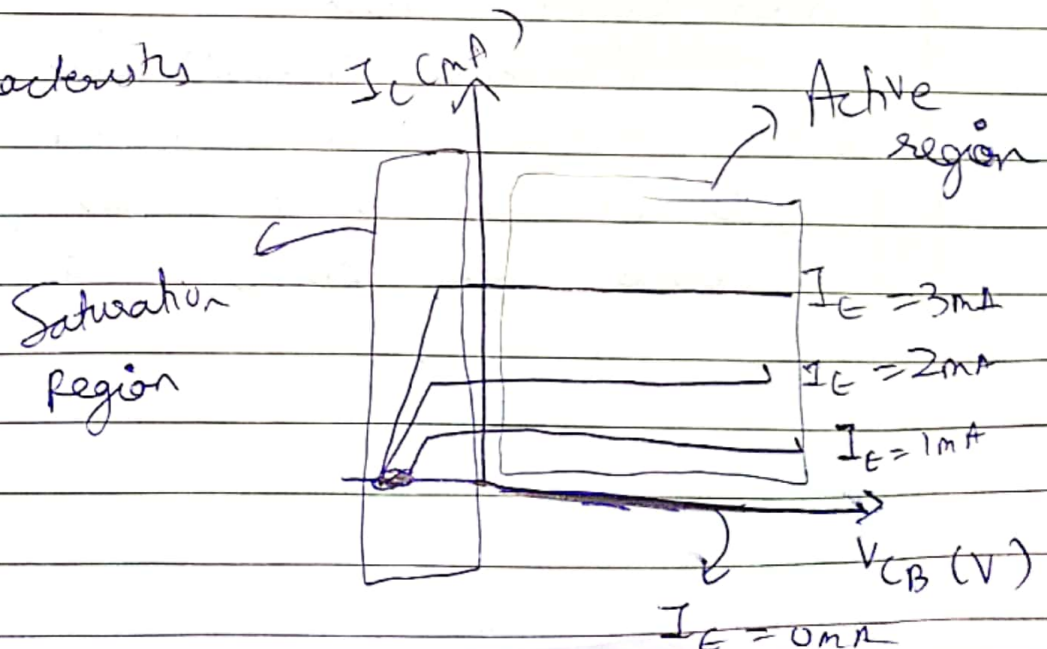

Date _____
Page _____

Active Region: here I_C remains constant even on increase in V_{CB}

So, here $I_C = \alpha I_E$

$$\alpha = \frac{I_C}{I_E}$$

So, in this region (Collector Current act like a constant current source)

↳ So, Used for Amplification.

Saturation Region: here ~~both~~ as $V_{CB} = -ve$
so, it is like both BE & CB are forward biased

In this region as the V_{CB} becomes more negative i.e. BC region becomes more forward biased

I_C (Collector Current) decreases as electrons enter into base junction (for npn) will not be able to cross base junction due to forward bias ~~to~~ nature across CB

Cut off Region

↳ When $I_E = 0 \Rightarrow I_C \approx 0$
even in increase of V_{CB} there is no I_C
when $I_E = 0$

The only current will be Reverse Saturation current (I_S) or I_{C0}
↓
flowed across Reverse bias sep
(due to minority carrier in BC)

So, For Common base

$$I_C = I_E + \overset{\text{Reverse saturation current}}{\underset{\text{i.e. found when } I_E = 0}{I_S}}$$

But as $I_E \uparrow$ So, $I_C \approx I_E$

Early Effect

↳

It's simply the thing we discussed in input characteristics
i.e. if we increase V_{CB} making BC more reverse biased
so, depletion region along Base & Collector increases
leading to decrease in size of Base, making it
more thin.

which is called Early Effect or Base-width
Modulation


& I_B current decreases

Common Emitter Configuration

Input Characteristics

Reason:

$$V_{CE} = V_{CB} + V_{BE}$$


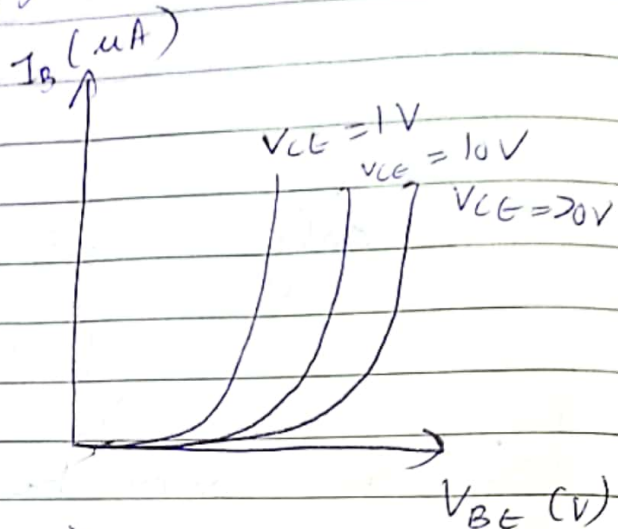


Now, if we will see for fixed value of V_{BE} if increase V_{CE} then V_{CB} will also increase

So, reverse bias along BC increase so, depletion region along BC will increase leading to smaller size of B_{ex} again. So, thereby reducing I_B hence,

With increase in V_{CE} I_B decreases for a particular value of V_{BE}

Output Characteristics

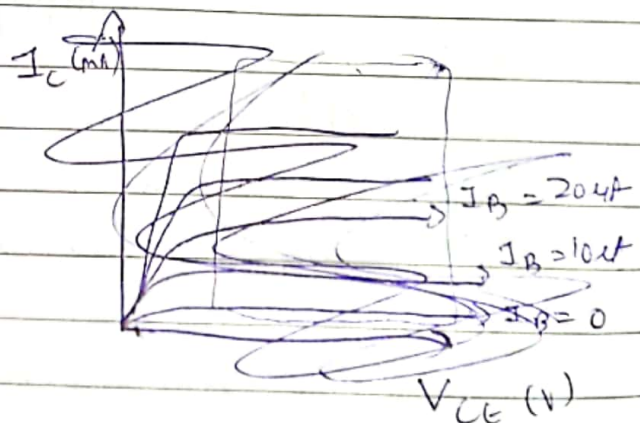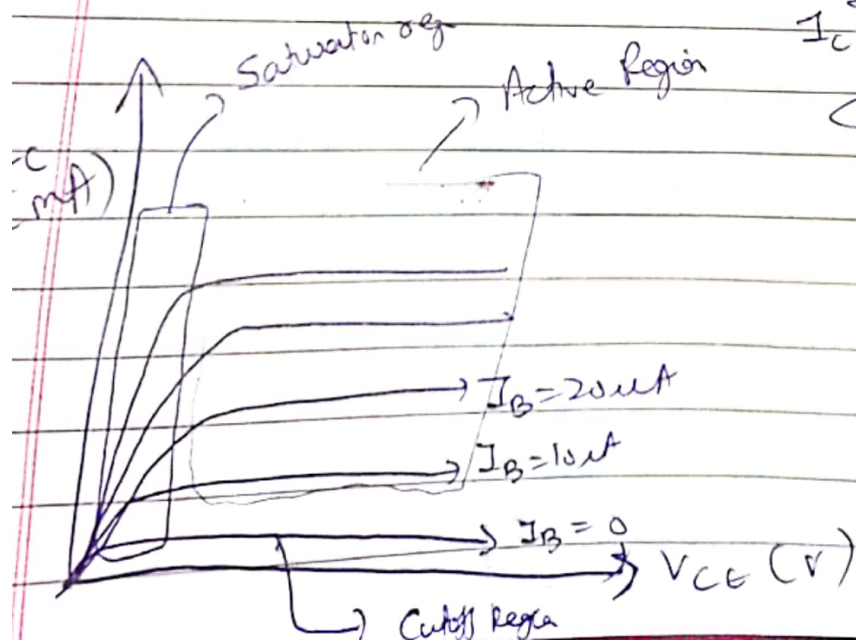

Active Region For $I_B > 0$

$$\beta_{DC} = \frac{\Delta I_C}{\Delta I_B}$$

As $I_B \uparrow$ I_C also \uparrow

I_C also with increase in V_{CC} , $I_C \uparrow$

$$V_{CC} = V_{CB} + V_{BE}$$

So, if V_{CC} increases $\Rightarrow V_{CB}$ also increases leading to increase in depletion region along BC and base region getting thin so, I_C increases

Saturation Region

Now, as the V_{CC} is close to zero Collector Base region becomes forward biased

Cut of Region

Let here for $I_B = 0$

U

$I_C \neq 0 \Rightarrow$ That is due to reverse

↓

Here unlike Common base configuration I_C value is large due to:

Saturation current I_{CO}

$$I_C = \alpha I_E + I_{CO}$$

$$I_C = \alpha (I_C + I_B) + I_{CO}$$

$$I_C = \frac{\alpha}{1-\alpha} I_B + \left(\frac{1}{1-\alpha} \right) I_{CO}$$

$$\& \beta = \frac{\alpha}{1-\alpha}$$

$$I_C = \beta I_B + \left(\frac{1}{1-\alpha} \right) I_{CO}$$

Now for cut off region $I_B = 0$

$$I_C = \left(\frac{1}{1-\alpha} \right) I_{CO}$$

$$\cong (\beta + 1) I_{CO}$$

So, there is large I_C even $I_B = 0$

So, Early effect in CE is more

Early Voltage → More significant in common Emu

↳ Same as we discussed in Input characteristics of Common Emitter

Some Imp points

Some Imp points of ~~the~~ Common Emitter circuit

* Saturation region is below ~~0.2V~~ V_{CE} . $V_{CE} = 0.2V$

So, Saturation region \Rightarrow ~~0.2V~~

$$0 < V_{CE} < 0.2V$$

(L) Remember

* Slope of output characteristics of Common Emitter Configuration is more than for Common base as

Early effect is more significant in Common Emitter

* Load line \Rightarrow Straight line joining two points

where first point is value of V_{CE} at $I_C = 0$
& second point when $V_{CE} = 0 \Rightarrow I_C$

↓
It contains every possible operating point for the circuit

Date _____
Page _____

Imp formula for BJT

$$\alpha = \frac{I_C}{I_E} = \frac{\beta}{\beta + 1}$$

$$\beta = \frac{I_C}{I_B} = \frac{\alpha}{1 - \alpha}$$

$$\beta + 1 \approx \frac{1}{1 - \alpha} = A_i \text{ (Current gain)}$$

$$I_E = I_C + I_B$$

$$I_C = \alpha I_E = \beta I_B + I_{C0}$$

$$I_E = I_B (1 + \beta)$$

$$V_{CE} = V_{CB} + V_{BE}$$

$$V_{CC} - V_{CE} = V_{CC} - I_C R_C = V_{CE} - V_{RC}$$

$$I_B = \frac{V_{BB} - V_{BE}}{R_B}$$

$$V_{RB} = V_{BB} - V_{BE}$$

$$\Rightarrow I_C = \beta I_B = \beta \left(\frac{V_{BB} - V_{BE}}{R_B} \right)$$

$$I_C = \frac{V_{CC} - V_{CE}}{R_C}$$

Base voltage $V_B = V_E + V_{BE}$