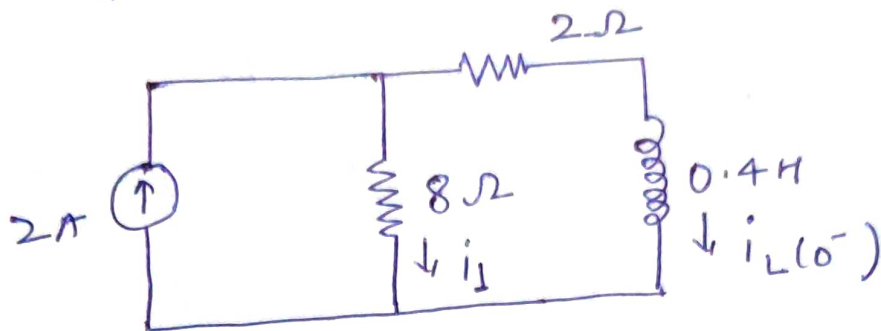


Page-1

Ans-1 For  $t < 0$ , the initial condition of current  $i_L(0^-)$ ,  $i_1(0^-)$  and  $i_2(0^-)$  is calculated from the figure:-




In steady state inductor can be represented by short circuit. So  $i_L(0^-) = 0$

by short circuit. So  $i_L(0^-) = 0$

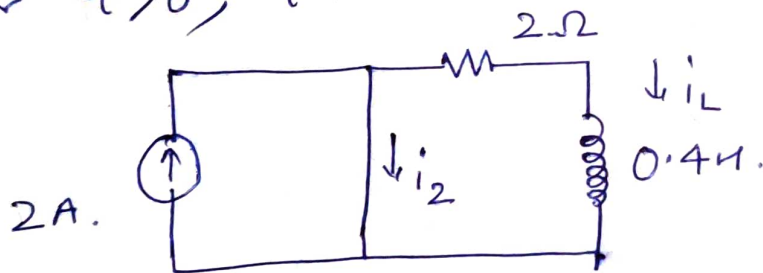0.5 MARKS  $\rightarrow i_1(0^-) = \frac{2}{10} \times 2 = \frac{2}{5} \text{ A}, i_L(0^-) = \frac{8}{10} \times 2 = \frac{8}{5} \text{ A}$

for  $t > 0$ , the circuit can be redrawn as:-



The current  $i_L$  flowing through the inductor is :-

$$i_L(\infty) = i_L(\text{final}) + [i_L(\text{initial}) - i_L(\text{final})] \exp\left(-\frac{t}{\tau}\right)$$

Time constant  $\tau = \frac{L}{R} = \frac{0.4}{2} = \frac{1}{5} \text{ sec.}$

0.5 MARKS

$$i_L(\text{final}) = i_L(\infty) = 0 \text{ A}$$

$$i_L(0^+) = i_L(0^-) = \frac{8}{5} \text{ A.}$$

$$i_L(t) = \frac{8}{5} \exp\left(-\frac{t}{\tau}\right) = \frac{8}{5} \exp(-5t).$$

$$i_L(0.15 \text{ s}) = \frac{8}{5} \exp(-0.75) = 0.754 \text{ A}$$


1 MARK

$$i_2(0.15 \text{ sec}) = 2 \text{ A} - 0.754 \text{ A} = 1.25 \text{ A}$$

1 MARK

$$i_1(0.15 \text{ sec}) = 0 \text{ A}$$

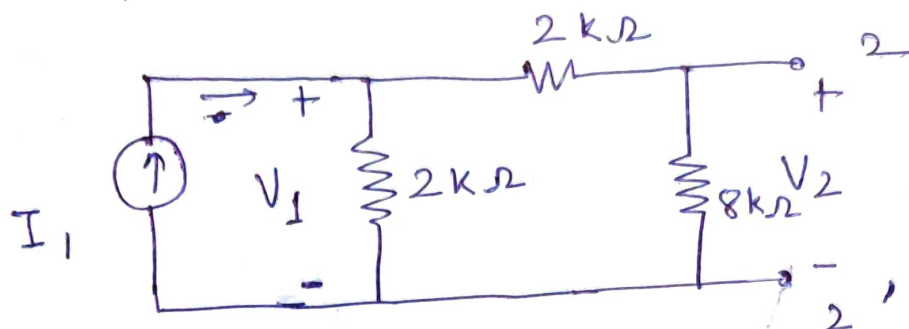Ans-2 To calculate  $Z_{11}$  and  $Z_{21}$ , we open circuit the port-2.




$$Z_{11} = \frac{V_1}{I_1} = \frac{\left[ \frac{10k}{6+12k} \times I_1 \right] \times 2k}{I_1} = \frac{5}{3} k\Omega$$

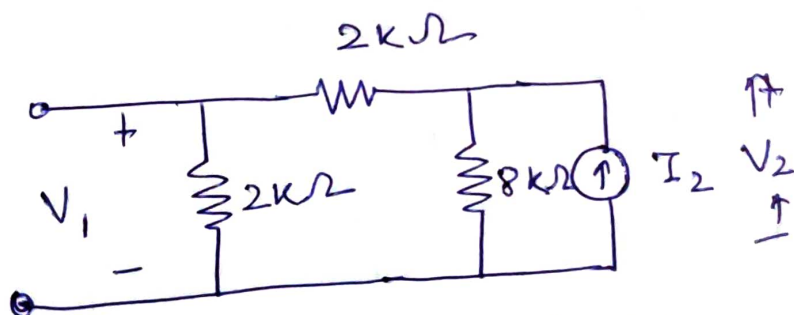1.5 MARK

$$Z_{21} = \frac{V_2}{I_1} = \frac{\left[ \frac{2k}{12k} \times I_1 \right] \times 8k}{I_1} = \frac{4}{3} k\Omega$$

To calculate  $Z_{12}$  and  $Z_{22}$ , we open circuit port-1.



$$Z_{12} = \frac{V_1}{I_2} = \frac{\left[ \frac{8k}{12k} \times 2k \right] \times I_2}{I_2} = \frac{4}{3} k\Omega$$

1.5 MARK

$$Z_{22} = \frac{V_2}{I_2} = \frac{\left[ \frac{4k}{12k} \times 8k \right] \times I_2}{I_2} = \frac{8}{3} k\Omega$$

Ans-3 In the circuit, we will first determine the equivalent input resistance  $R_{eq}$  of the shaded part as shown below


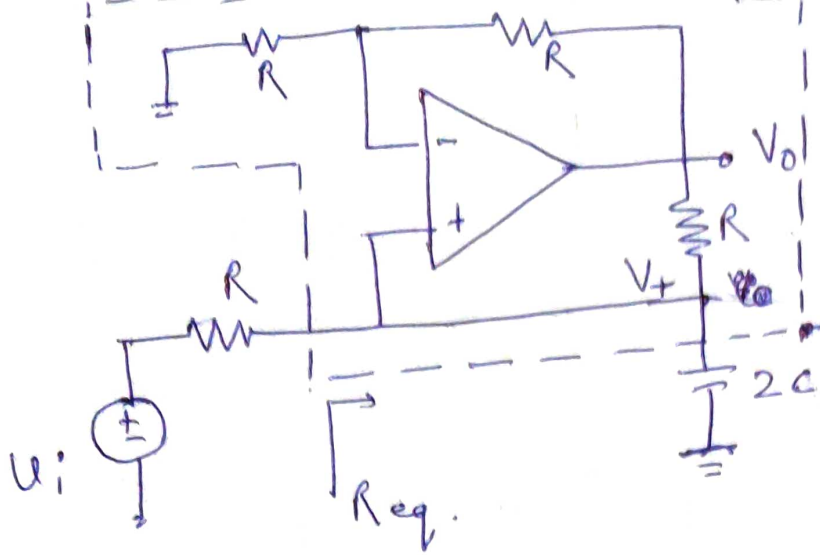


Fig. 1

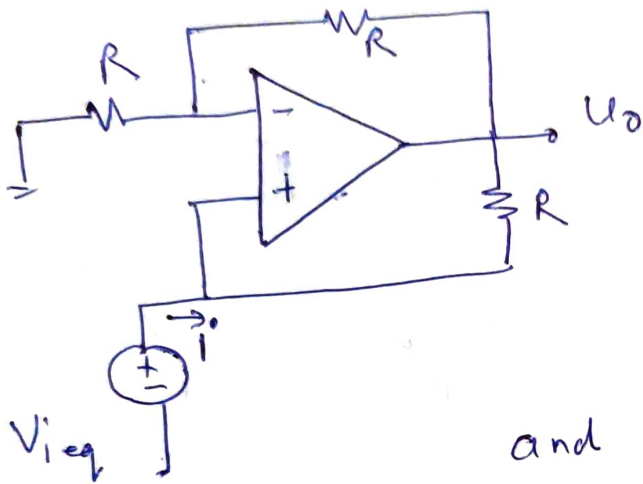

Applying KVL we get

$$U_o = U_{ieq} - iR$$

$$\text{or } U_{ieq} = U_o + iR \quad (1)$$

and we know:-

$$\frac{U_o}{U_{ieq}} = \left[ 1 + \frac{R}{R} \right] = 2.$$

$$\text{or } U_o = 2U_{ieq}. \quad (2)$$


putting (2) in (1) we have:-

$$U_{ieq} = 2U_{ieq} + iR.$$


$$R_{eq} = \frac{U_{ieq}}{i} = -R \quad (3)$$

1 MARK

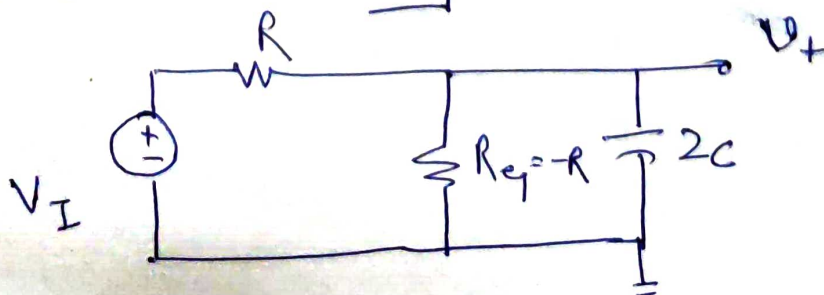Now the remaining circuit with  $R_{eq}$  is:-



By source transformation we can redraw:-

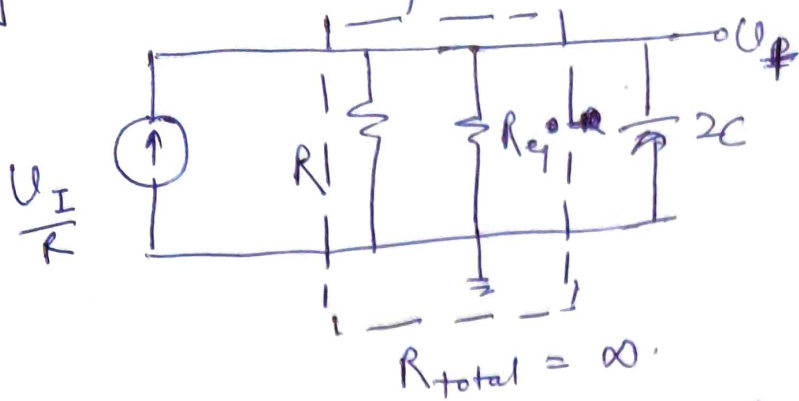

$$R_{total} = \frac{R \times R}{R - R} = \infty$$

All current  $\frac{U_I}{R}$  will flow through the capacitor so:-

$$U_+ = \frac{U_I}{R} \times \frac{1}{2sC} = \frac{U_I}{2sRC} \quad \text{--- (4) [1 MARK]}$$

Now from the circuit in fig. 1, we have:-

$$U_0 = \left[ 1 + \frac{R}{R} \right] \times U_+$$

Replacing eq-4 in above expression:-

$$U_0 = \left[ 1 + \frac{R}{R} \right] \times \frac{U_I}{2sRC}$$

$$\boxed{\frac{U_0}{U_I} = \frac{1}{sRC}} \quad \text{--- [1 MARK]}$$

Ans-4 a) Hall constant  $R_H = \frac{V_H d}{I_H B_z}$

$$R_H = \frac{6 \times 10^{-3} \times 0.4}{7.5 \times 10^{-3} \times 5 \times 10^{-5}}$$

$$R_H = 6.4 \times 10^3 \text{ cm}^3 \text{ coulomb}^{-1} \quad \text{--- [1 MARK]}$$

$R_H$  is positive, so semiconductor is of P-type

b) Hole concentration  $P_0$  is given by:-



$$P_0 = \frac{L}{q \cdot R_H} = \frac{L}{1.6 \times 10^{-19} \times 6.4 \times 10^3}$$

$$P_0 = \frac{L}{10.24 \times 10^{-16}} = 9.76 \times 10^{14} \text{ cm}^{-3} \quad \boxed{1 \text{ MARK}}$$

c) Hall mobility  $\mu_H$  is given as :-

$$\mu_H = \frac{l}{w} \left( \frac{V_H}{V_x B_z} \right) = \frac{2 \times 6 \times 10^{-3}}{0.4 \times 1.5 \times 5 \times 10^{-5}}$$

$$\mu_H = 400 \text{ cm}^2 \text{ V}^{-1} \text{ sec}^{-1} \quad \boxed{1 \text{ MARK}}$$

Ans-5 We will assume that all the dopants are ionized, then:

$$n_0 - p_0 = N_D - N_A = (6-2) \times 10^{15} = 4 \times 10^{15}$$

a) This is much higher than  $n_i$ , i.e.

$$(N_D - N_A)^2 \gg 4n_i^2$$

$$\text{so } n_0 = \frac{1}{2} \left[ (N_D - N_A) + (N_D - N_A) \right]$$

$$n_0 = N_D - N_A = 4 \times 10^{15}$$

$$\text{and } p_0 = \frac{n_i^2}{n_0} = 5.625 \times 10^4 \text{ cm}^{-3} \quad \boxed{1 \text{ MARK}}$$

$$b) E_F = E_i + kT \ln \frac{4 \times 10^{15}}{1.5 \times 10^{10}}$$

$$E_F - E_i = 0.324 \text{ eV.}$$

$$\text{so } E_C - E_F = 0.56 - 0.324 = 0.236 \text{ eV}$$

$$\boxed{1 \text{ MARK}}$$

Ans-6. a) The excess charges concentration  $\Delta n$  and  $\Delta p$  is :-

$$\Delta p = \Delta n = q_L T_p$$

$$= 2 \times 10^{19} \times 1 \times 10^{-6} = 2 \times 10^{-13} \text{ pairs/cm}^3$$

1 mark

b) Sample is doped with  $N_0 = 6 \times 10^{14} \text{ cm}^{-3}$ , and assuming they all are ionized.

$$n_0 = 6 \times 10^{14} \text{ cm}^{-3}$$

$$p_0 = \frac{n_i^2}{n_0} = \frac{2.25 \times 10^{20}}{6 \times 10^{14}} = 3.75 \times 10^5 \text{ cm}^{-3}$$

so

$$n = n_0 + \Delta n = 6 \times 10^{14} + 2 \times 10^{13} = 6.2 \times 10^{14} \text{ cm}^{-3}$$

$$p = p_0 + \Delta p = 2 \times 10^{13} \text{ cm}^{-3}$$

$$\sigma = q(n\mu_n + p\mu_p)$$

$$= 1.6 \times 10^{-19} \left( 1350 \times 6.2 \times 10^{14} + 480 \times 2 \times 10^{13} \right)$$

$$\sigma = 0.1354 \text{ S/cm.}$$

$$\rho = \frac{1}{\sigma} = 7.38 \Omega\text{-cm}$$

2 mark

Ans-7.

Built-in potential  $\phi_{bi} = \frac{kT}{q} \ln \left( \frac{N_A N_D}{n_i^2} \right)$

$$= 26 \times 10^{-3} \ln \left( \frac{2 \times 10^{30}}{2.25 \times 10^{20}} \right)$$

$$\phi_{bi} = 0.592 \text{ V.}$$

In equilibrium conditions the fermi level of P and N side after its quasi fermi level condition will get aligned. For P-side semiconductor the position of fermi level is :-

$$E_F - E_i = -KT \ln\left(\frac{N_A}{n_i}\right) = -KT \ln\left(\frac{10^{15}}{1.5 \times 10^{10}}\right)$$

$$E_F - E_i = -0.026 \times 11.10$$

$$= -0.28 \text{ eV}$$

So  $E_V - E_{FP} = -0.56 \text{ eV} + 0.28 \text{ eV}$

$$E_V - E_{FP} = -0.28 \text{ eV}$$


Similarly for N-side :-

$$E_{Fn} - E_i = KT \ln\left(\frac{2 \times 10^{15}}{1.5 \times 10^{10}}\right)$$


$$E_{Fn} - E_i = 0.30 \text{ eV}$$

So  $E_C - E_{Fn} = 0.56 - 0.30 = 0.26 \text{ eV}$

For reverse bias of 3V :-

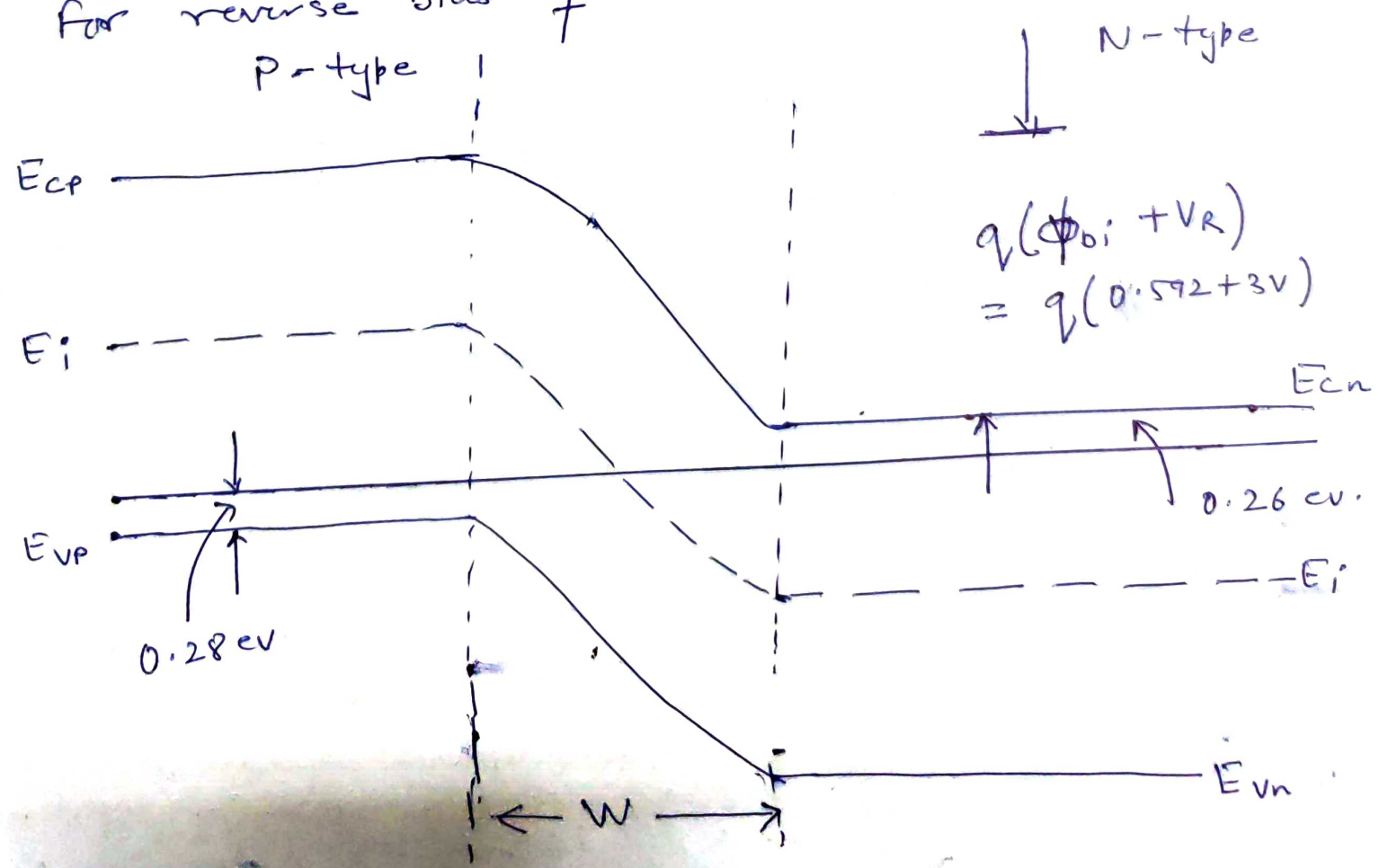

b) For forward bias of 0.7V

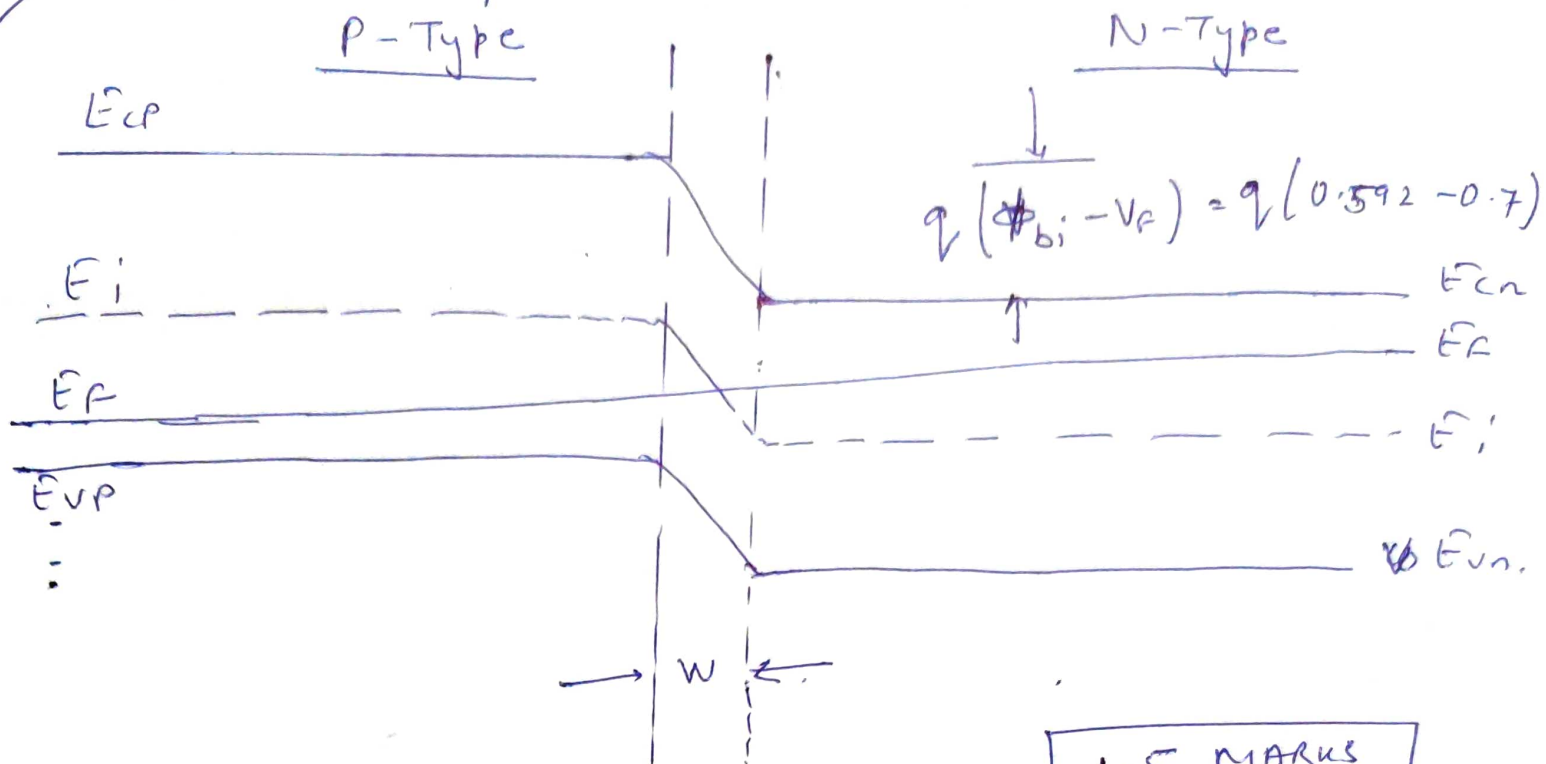

1.5 MARKS  
for BOTH

Ans-8 a)  $V_{max} = \sqrt{2} \times V_{rms} = \sqrt{2} \times 120 = 169.7$

$$I_{max} = \frac{V_{max} - 1.4}{R_L} = 168.3 \text{ mA}$$

$$I_{DC} = \frac{2 I_{max}}{\pi} = 107.14 \text{ mA}, V_{dc} = I_{dc} \times R_L = 107.14 \text{ V}$$

1 MARK

b)  $PIV = V_{max} = 169.7 \text{ V}$  — 1 MARK

c)  $I_{max} = 168.3 \text{ mA}$  — 1 MARK

d)  ~~$P_{area} = V_o \times I_{o,max} = 0.7 \times 168.3 = 117.81 \text{ mW}$~~

$$\text{Input AC power} = V_{rms} \times I_{rms} = 120 \times \left( \frac{168.3}{\sqrt{2}} \right) \text{ mW}$$

$$\begin{aligned} \text{output DC power} &= V_{oc} \times I_{oc} \\ &= 107.14 \text{ mA} \times 107.14 \text{ V} \\ &= 11478.98 \text{ mW} \end{aligned}$$

Power dissipated in 4 diodes is:-

$$120 \times \frac{168.3}{\sqrt{2}} - 11478.98 \text{ mW} = 2801.75 \text{ mW}$$


Power dissipated in each diode = 700.44 mW  
or (power rating of diode)

1 MARK



Ans 8-b

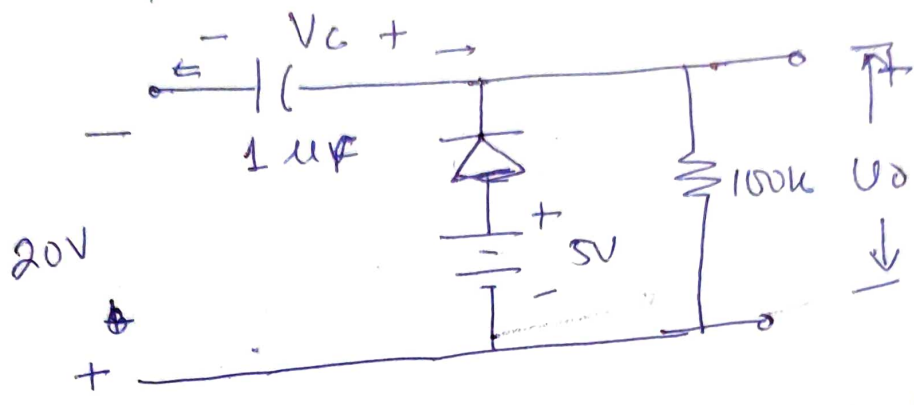
In between time interval 0 to  $T_1$ , the capacitor is not charged. We will wait for time for capacitor charging. In between time interval  ~~$T_0$  to~~  $T_1$  to  $T_2$ , the Voltage  $V_{in}$  is  $-20V$ , as shown below :-



The diode will conduct and capacitor will charge to  $V_C = 5V + 20V = 25V$ , And o/p voltage is  $+5V$ . During time interval  $T_2$  to  $T_3$ , the diode is switched off as it is reverse biased, so o/p voltage  $U_o = 25V + 10V = 35V$ .

$$U_o = \begin{cases} \text{Not charged} & 0 < t < T_1 \\ 5V & T_1 < t < T_2 \\ 35V & T_2 < t < T_3 \end{cases}$$

2 MARKS

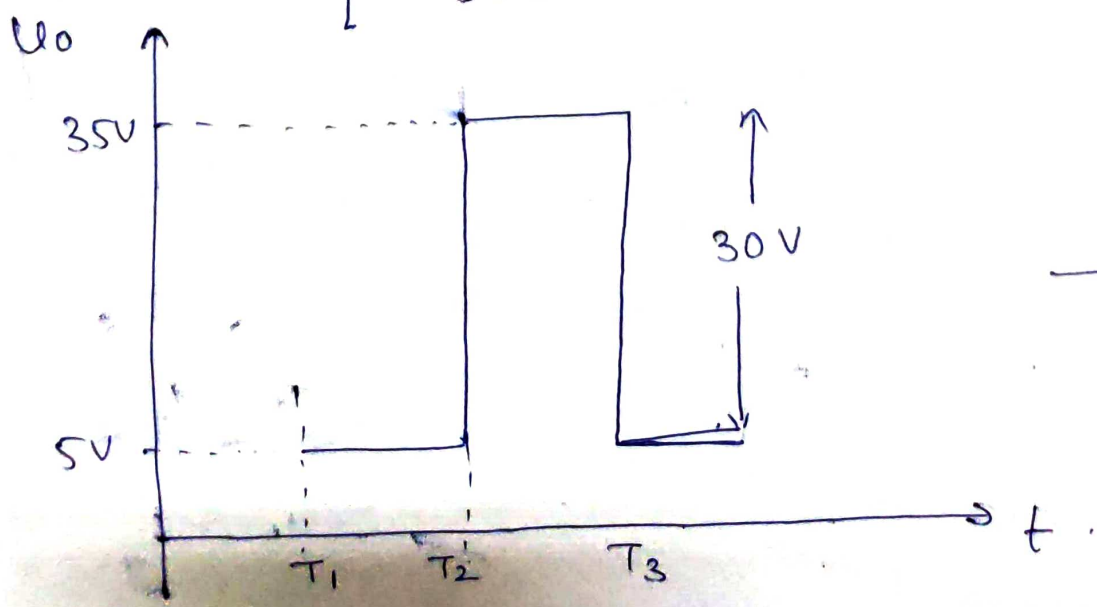

1 MARK

Ans-9a) Assuming  $D_1$  is off as  $V_I = 0, I_{d1} = 0A$


$$I_{R1} = I_{R2} = I_{d2} = \frac{5 - (-5)}{R_1 + R_2} = \frac{10}{10K + 5K}$$

$$= \frac{10}{15K} = 0.666 \text{ mA} \quad \text{--- [1 MARK]}$$

So  $V_0 = 5 - 0.62 \text{ mA} \times 5K\Omega$

$$V_0 = 1.9 \text{ V.}$$

--- [1 MARK]

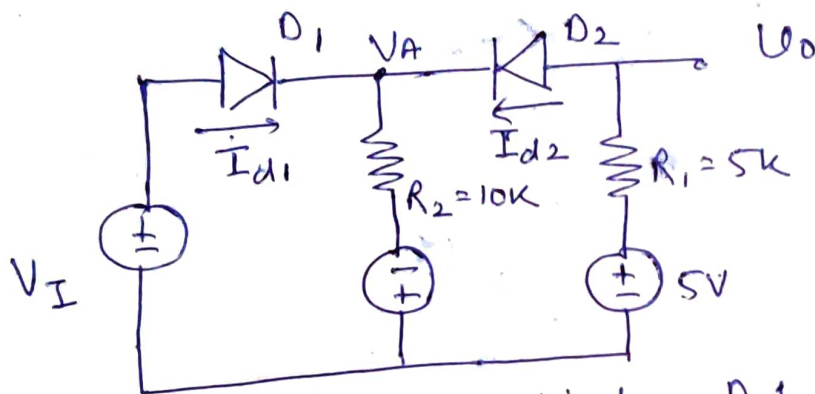

The node Voltage

$V_A$  is  $V_0 - 0$

$$V_A = 1.9 \text{ V}$$

Therefore diode  $D_1$  is reverse biased, thus assumption that  $D_1$  is off is verified.

b) If  $V_I = 4V$ , Assuming  $D_1$  and  $D_2$  are ON. The output voltage  $V_0 = V_I = 4V$ . --- [1 MARK]

$$I_{R1} = I_{R2} = \frac{5 - 4}{5K} = 0.2 \text{ mA}$$

$$I_{R2} = \frac{4 - (-5)}{10K} = \frac{9}{10K} = 0.9 \text{ mA}$$

$$I_{D1} = I_{R2} - I_{R1} = 0.9 \text{ mA} - 0.2 \text{ mA} = 0.7 \text{ mA}$$

[1 MARK]

Ans-10 a) The Ebers-Moll model of BJT, describe the behaviour of BJT by a set of governing Ebers-Moll equations. The equation of PNP BJT are:-

1 MARKS ←

$$I_E = I_{ES} \left[ \exp\left(\frac{qV_{EB}}{kT}\right) - 1 \right] - \alpha_I I_{CS} \left[ \exp\left(\frac{qV_{CB}}{kT}\right) - 1 \right] \quad \text{--- (1)}$$

$$I_C = -\alpha_N I_{ES} \left[ \exp\left(\frac{qV_{EB}}{kT}\right) - 1 \right] + I_{CS} \left[ \exp\left(\frac{qV_{CB}}{kT}\right) - 1 \right] \quad \text{--- (2)}$$


If we eliminate  $\exp\left(\frac{qV_{EB}}{kT}\right) - 1$  from eq<sup>n</sup> (1) & eq<sup>n</sup> (2) then we obtain:

$$I_E = I_{EO} \left[ \exp\left(\frac{qV_{EB}}{kT}\right) - 1 \right] - \alpha_I I_C \quad \text{--- (3)}$$

and if we eliminate  $\exp\left(\frac{qV_{EB}}{kT}\right) - 1$  from eq<sup>n</sup> (1) & (2) then:-

$$I_C = I_{CO} \left[ \exp\left(\frac{qV_{CB}}{kT}\right) - 1 \right] - \alpha_N I_E \quad \text{--- (4)}$$

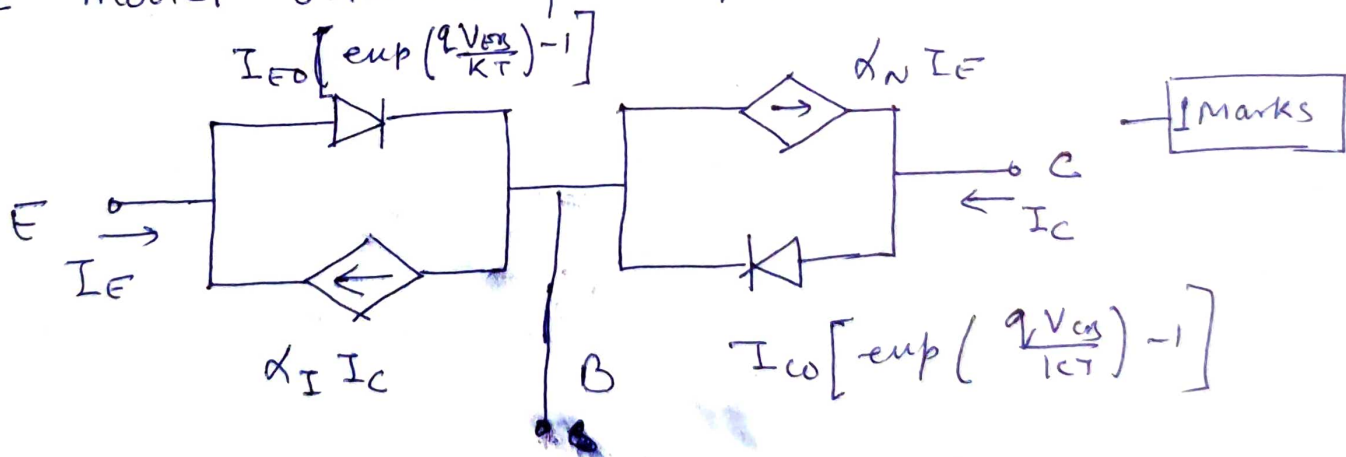The model obtained from eq<sup>n</sup> (3) and eq<sup>n</sup> (4) is as:-



where  $I_{EO}$  is reverse saturation current in B-E junction when B-C junction is open circuit. And  $I_{CO}$  is reverse saturation current in B-C junction when B-E junction is open circuit.

b) In normal active mode of <sup>BJT</sup> operation the B-C junction is reverse biased. The depletion region



Spreads into the base, Let  $W_{B0}$  is the width of base, when B-C junction is not reverse bias. Since depletion region  $W$  is function of applied Voltage by:-



$$W = \sqrt{\frac{2\epsilon_s}{qN_E} (V_{bi} + V_{BC})}$$

it increases

when B-C is reverse biased,  $W$  increases, so effective Base width  $W_B = W_{B0} - W$ , start decreasing

This decrease or narrowing of base width is called base width modulation. This phenomena in transistor was first studied by J. M. Early, and is all called Early Effect. — 1 MARKS

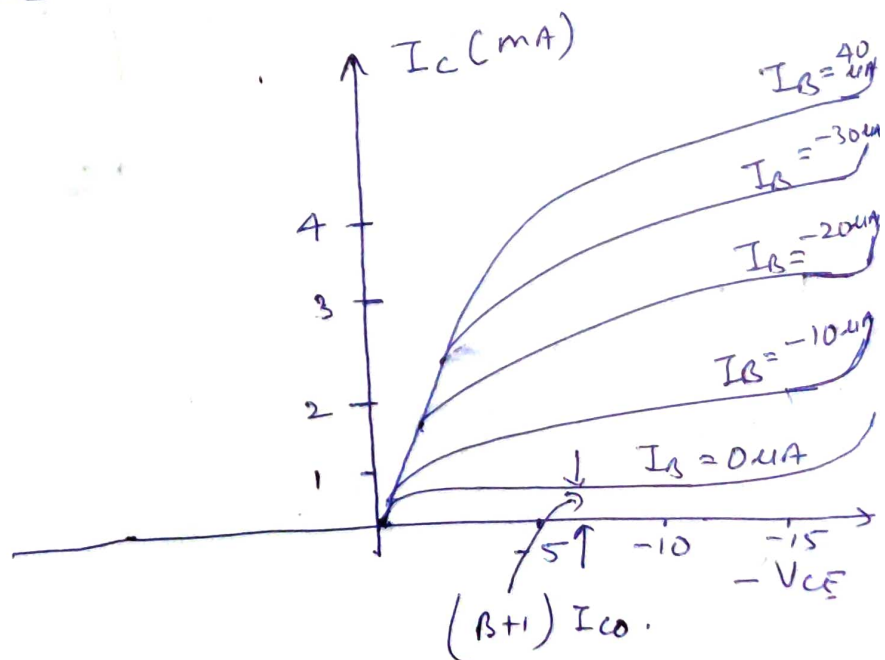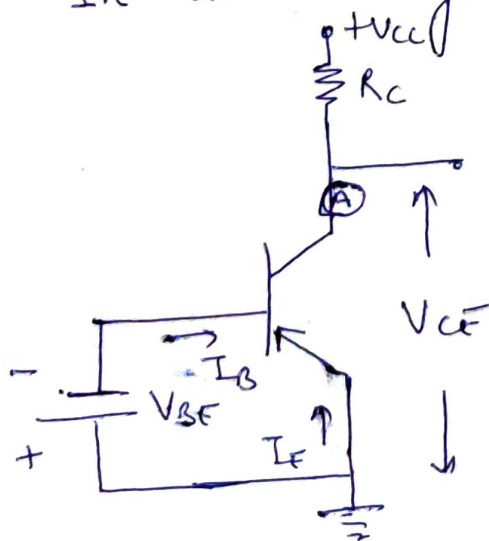Ans-C The o/p characteristics of a PNP ~~trans~~ transistor is plotted between  $I_C$  Versus  $V_{CE}$  or  $I_C$  Versus  $-V_{CE}$ , with base current constant. In active region  $I_C$  is independent of  $V_{CE}$ .



— 1 MARKS