

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY

Electronics and Communication Engineering

Electrical Science-1 (15B11EC111)

Tutorial Sheet: 9

Q1. [CO2] Find the Thevenin's equivalent circuit as seen from terminals a and b for the circuit shown in Fig. 1.

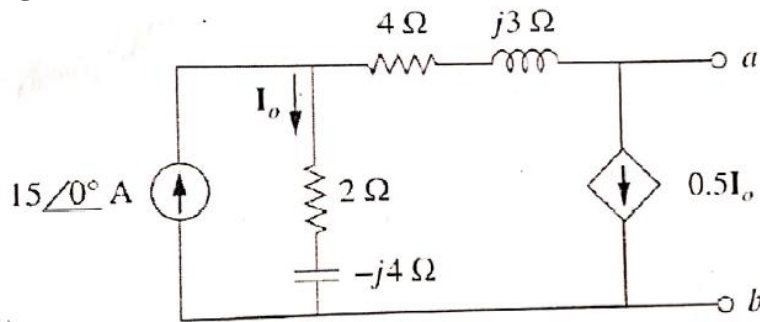


Fig. 1

Q2. [CO2] Obtain current I_o in the circuit of Fig. 2 using Norton's theorem.

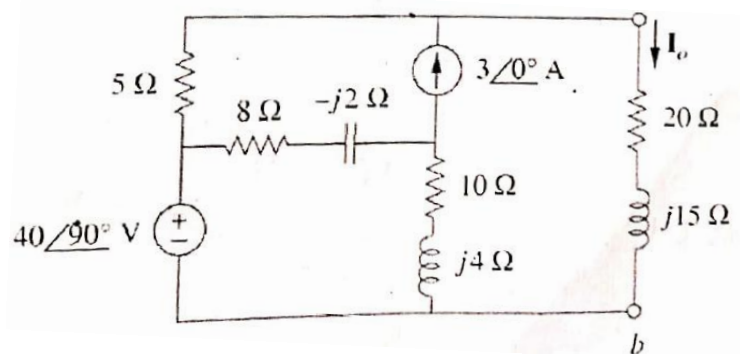


Fig. 2

Q3. [CO2] Calculate the power factor seen by the source and the average power supplied by the source in the circuit of Fig. 3.

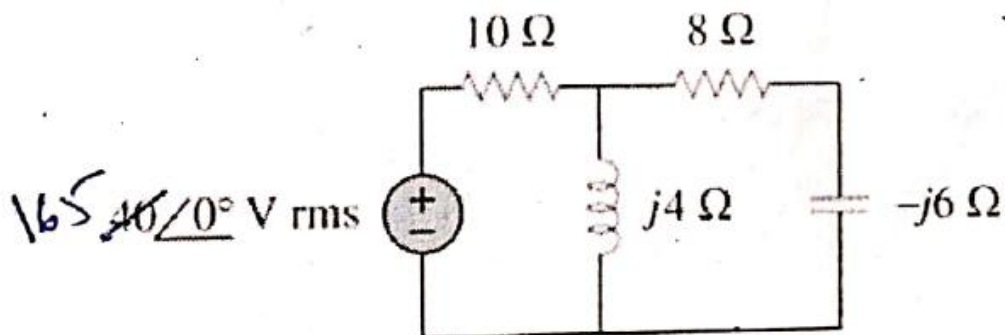


Fig. 3

Q4. [CO2] Find the value of the load impedance in the circuit of Fig. 4, for which it would absorb the maximum average power .

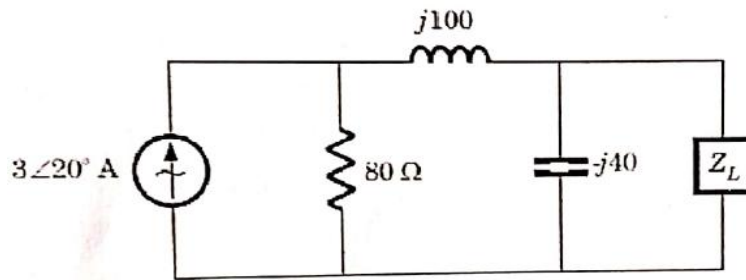


Fig. 4

Q5. [CO2] In the circuit of Fig. 5, find the maximum power absorbed by Z_L .

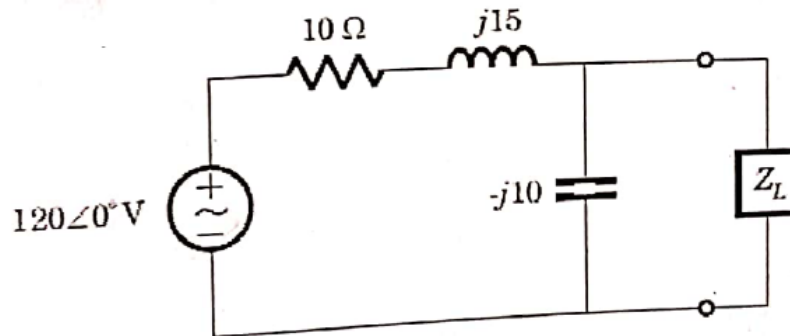


Fig. 5