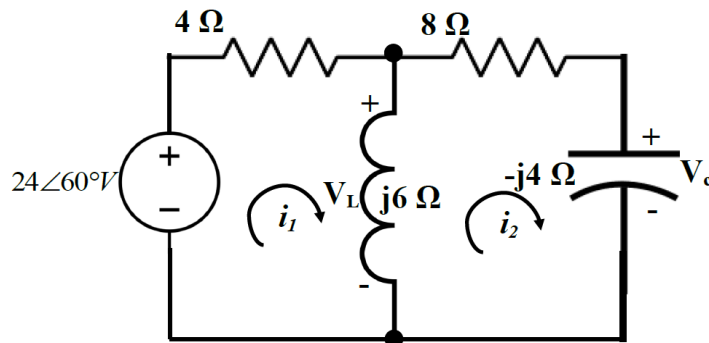


**JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY**  
**Electronics and Communication Engineering**  
**Electrical Science-1 (15B11EC111)**  
**Tutorial Sheet: 8**


---

**Q.1 [CO2]** Find  $i_1$ ,  $i_2$ ,  $V_L$  and  $V_c$  for the circuit shown in fig. 1 using mesh analysis:




**Fig.1**

**Q. 2 [CO2]** Determine mesh equation for the circuit shown in fig. 2: Given  $\omega = 103 \text{ rad/s}$

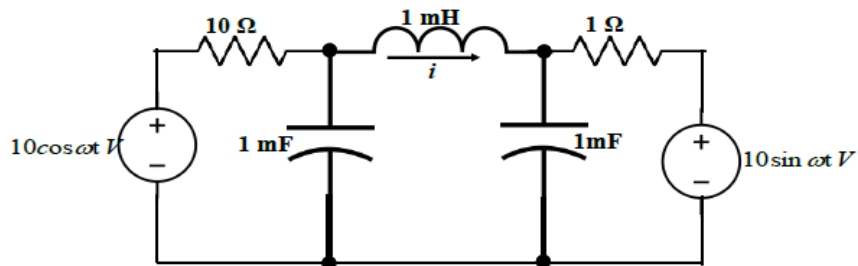


**Fig.2**

**Q. 3 [CO2]** Determine B and L for the circuit shown in fig. 3, when  $i(t) = B \cos(3t - 51.87^\circ) \text{ A}$ .

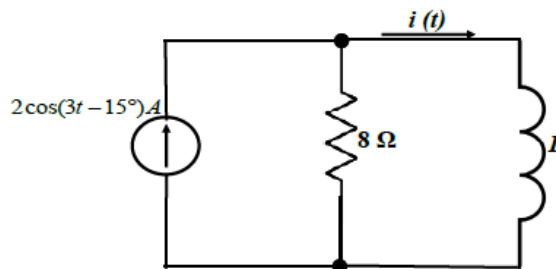


**Fig. 3**

**Q. 4. [CO2]** Determine  $i$  in the circuit shown in fig. 4:

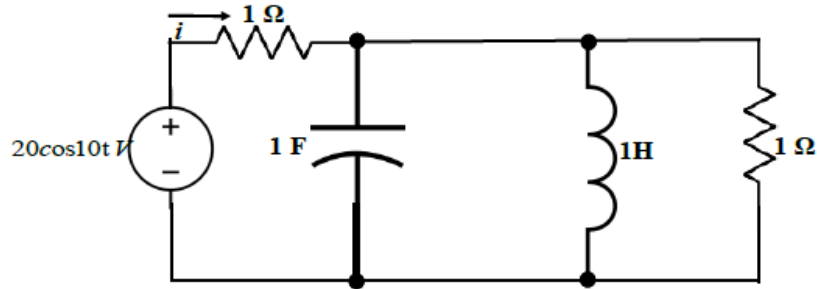


**Fig.4**

**Q. 5. [CO2]** Determine  $V_x$  in the circuit shown in fig. 5 using any method of your choice.

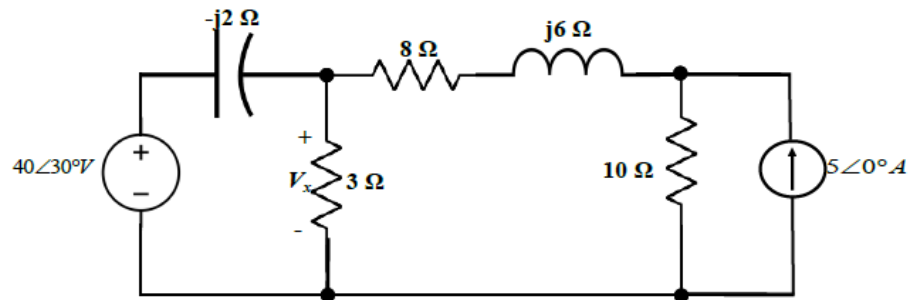

**Fig. 5**

**Q. 6. [CO2]** Use the superposition theorem to obtain  $v_x$  in the circuit shown in **fig. 6** Let  $v_s = 50\sin 2t$  V and  $i_s = 12 \cos (6t+10^\circ)$  A.

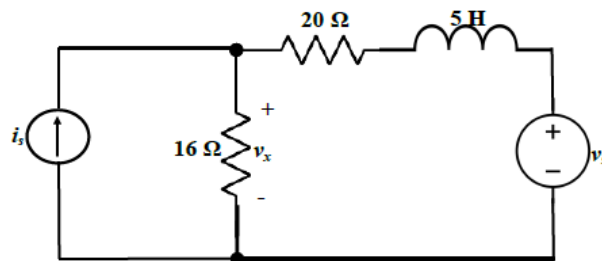

**Fig. 6**