



Digital Systems

18B11EC213

Module 1: Boolean Function Minimization Techniques and Combinational Circuits-8

Dr. Saurabh Chaturvedi

Logic Gates

- Logic Gates

NOT Gate (Inverter)

AND Gate

OR Gate

NAND Gate

NOR Gate


EX-OR (Exclusive-OR) Gate

EX-NOR (Exclusive-NOR) Gate

- Drawing Logic Circuits
- Analysing Logic Circuits
- Universal Gates


Cont..

❖ NOT Gate (Inverter)

 


A	A'
0	1
1	0

Application of the inverter: complement

 

Cont..


❖ AND Gate

 

A	B	A . B
0	0	0
0	1	0
1	0	0
1	1	1

Cont..


❖ OR Gate

 


A	B	$A + B$
0	0	0
0	1	1
1	0	1
1	1	1

Cont..

❖ NAND Gate

 

A	B	$(A.B)'$
0	0	1
0	1	1
1	0	1
1	1	0

 


Cont..

❖ NOR Gate




A	B	$(A+B)'$
0	0	1
0	1	0
1	0	0
1	1	0

 

Cont..

❖ XOR Gate

 


$$A \oplus B = A'.B + A.B'$$

A	B	$A \oplus B$
0	0	0
0	1	1
1	0	1
1	1	0

Cont..

❖ XNOR Gate

 

$$(A \oplus B)' = A.B + A'.B'$$

A	B	$(A \oplus B)'$
0	0	1
0	1	0
1	0	0
1	1	1


Drawing Logic Circuits

- When a Boolean expression is provided, we can easily draw the logic circuit.

Example-1:

$$F1(x, y, z) = x.y.z'$$

Note the use of a 3-input AND gate.

 


Cont..

 Example-2:


$$F2(x, y, z) = x + y'.z$$

We can assume that the variables and their complements are available.



Example-3:


$$F3 = xy' + x'z$$

 

Analysing Logic Circuits

- When a logic circuit is given, we can analyse the circuit to obtain the logic expression.

 Example: What is the Boolean (logic) expression of F4?



$$F4 = (A'B'+C)' = (A+B).C'$$


Universal Gates: NAND and NOR

- AND/OR/NOT gates are sufficient for building any Boolean (logic) functions.
- We call the set {AND, OR, NOT} a **complete set** of logic.

Cont..

❑ NAND Gate

 
- NAND gate is **self-sufficient**, i.e., it can implement any logic circuit with it.
- Therefore, {NAND} is also a **complete set** of logic.
- It can be used to implement AND/OR/NOT.
- ❖ Implementing an inverter (NOT gate) using NAND gate:



$$(x.x)' = x' \quad \text{Idempotency}$$


Cont..

 ❖ Implementing AND gate using NAND gates:



$$\begin{aligned} ((xy)'(xy)')' &= ((xy)')' && \text{Idempotency} \\ &= (xy) && \text{Involution} \end{aligned}$$

❖ Implementing OR gate using NAND gates:

 


$$\begin{aligned} ((xx)'(yy)')' &= (x'y')' && \text{Idempotency} \\ &= (x')'+(y')' && \text{DeMorgan} \\ &= x+y && \text{Involution} \end{aligned}$$

Cont..

□ NOR Gate

 
- NOR gate is also **self-sufficient**.
- Therefore, {NOR} is also a **complete set** of logic.
- It can be used to implement AND/OR/NOT.
- ❖ Implementing an inverter (NOT gate) using NOR gate:



$$(x+x)' = x' \quad \text{Idempotency}$$


Cont..

❖ Implementing AND gate using NOR gates:

 

$$\begin{aligned} ((x+x)' + (y+y)')' &= (x' + y')' && \text{Idempotency} \\ &= (x')' \cdot (y')' && \text{DeMorgan} \\ &= x.y && \text{Involution} \end{aligned}$$

❖ Implementing OR gate using NOR gates:

 

$$\begin{aligned} ((x+y)' + (x+y)')' &= ((x+y)')' && \text{Idempotency} \\ &= (x+y) && \text{Involution} \end{aligned}$$

Implementation Using NAND Gates

- It is possible to implement any Boolean expression using NAND gates.

Procedure:

Step-1: Obtain the sum-of-products (SOP) Boolean expression.

Let the Boolean function is $F_3(x, y, z) = xy' + x'z$

Step-2: Use the DeMorgan's theorem to obtain the expression using two-level NAND gates.


$$\text{Given } F_3 = xy' + x'z$$

$$= ((xy' + x'z)')' \quad \text{Involution}$$

$$\Rightarrow F_3 = ((xy')' \cdot (x'z)')' \quad \text{DeMorgan}$$

Cont..

$$F3 = ((xy')'.(x'z)')' = xy' + x'z$$

 

Implementation Using NOR Gates

- It is possible to implement any Boolean expression using NOR gates.

Procedure:

Step-1: Obtain the product-of-sums (POS) Boolean expression.

Let the Boolean function is $F6 = (x+y')(x'+z)$

Step-2: Use the DeMorgan's theorem to obtain the expression using two-level NOR gates.


$$\text{Given } F6 = (x+y')(x'+z)$$

$$= (((x+y')(x'+z)))' \quad \text{Involution}$$

$$\Rightarrow F6 = ((x+y')' + (x'+z)')' \quad \text{DeMorgan}$$


Cont..
 
$$F6 = ((x+y')' + (x'+z)')' = (x+y') \cdot (x'+z)$$



Implementation of SOP Expressions

 - Sum-of-Products (SOP) expressions can be implemented using:
 - ❖ Two-level AND-OR logic circuits
 - ❖ Two-level NAND logic circuits
- ❖ AND-OR logic circuit





Cont..

❖ NAND-NAND circuit (by circuit transformation)

a) Add double bubbles

  
b) Change OR-with-inverted-inputs to NAND and bubbles at inputs to their complements



Implementation of POS Expressions

- Product-of-Sums (POS) expressions can be implemented using:
 - ❖ Two-level OR-AND logic circuits
 - ❖ Two-level NOR logic circuits
- ❖ OR-AND logic circuit


Let $G = (A+B).(C+D).E$

 

Cont..

❖ NOR-NOR circuit (by circuit transformation):

 - a) Add double bubbles
- b) Change AND-with-inverted-inputs to NOR and bubbles at inputs to their complements



References

- M. M. Mano, *Digital Logic and Computer Design*, 5th ed., Pearson Prentice Hall, 2013.
- R. P. Jain, *Modern Digital Electronics*, 4th ed., Tata McGraw-Hill Education, 2009.