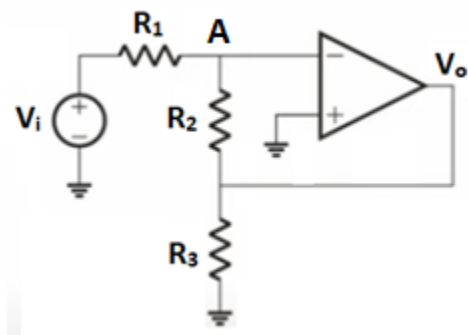


JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY
Electronics and Communication Engineering
Electrical Science-II (15B11EC211)
Solution of Tutorial Sheet: 6

Solution: 01



For Ideal case of Op-Amp, voltage gain (A_v) = $V_o/V_{id} = \infty$


Therefore, $V_{id} = 0$ i.e. $V_+ - V_- = 0$ or $V_+ = V_-$ (Virtual short concept)

Apply KCL at node A position in the inverting terminal

$$(0 - V_i)/R_1 + (0 - V_o)/R_2 = 0$$

$$A_v = V_o/V_i = -R_2/R_1$$

Solution-02

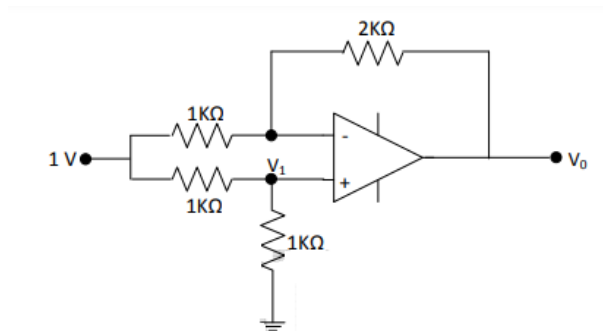

Apply superposition in the given Op-Amp

The output voltage (V_{01}) due to inverting input $= (-R_f/R)V_i = (-2k/1K) \times 1 = -2$ Volt

and for $V_1 = 1k \times 1/1k+1k = 0.5$ (Potential divider)


The output voltage (V_{02}) due to non inverting input $= (1+R_f/R)V_1 = (1+2/1) \times 0.5 = 1.5$ Volt

The total output (V_0) $= V_{01} + V_{02} = -2 + 1.5 = -0.5$ Volt

Solution:03

For ideal case of Op-Amp, voltage gain (A_v) $= V_o/V_{id} = \infty$

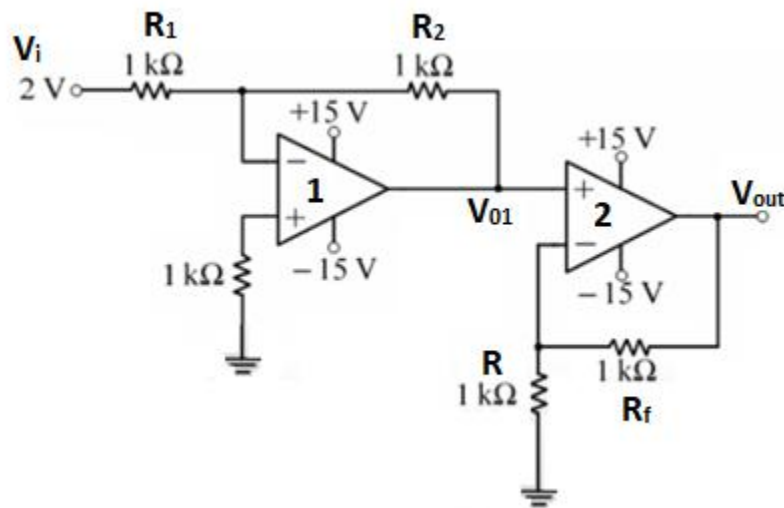Therefore, $V_{id} = 0$ i.e. $V_+ - V_- = 0$ or $V_+ = V_-$.



For OP-AMP -1: It is a inverting Op-Amp.

Therefore,

Apply KCL at inverting terminal

$$(0-V_i)/R_1 + (0-V_{01})/R_2 = 0$$

$$V_{01} = (-R_2/R_1)V_i = -(1k/1k) \times 2 = -2 \text{ Volt} \quad \text{.....(i)}$$

For OP-AMP -2: It is a non inverting Op-Amp.

Therefore,


For non-inverting amplifier, apply KCL again at inverting terminal for V_{out}

$$(V_{01}-0)/R+(V_{01}-V_{out})/R_f = 0$$

$$V_{out} = (1+R_f/R) V_{01}$$

$$V_{out} = (1+1/1) \times (-2) = -4 \text{ Volt}$$

Solution:04

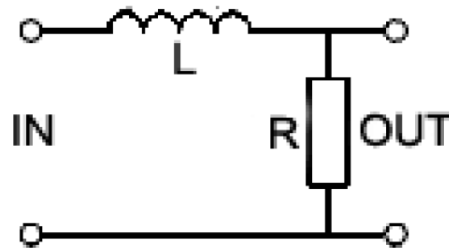

$$H(\omega) = \frac{V_o}{V_i} = \frac{R}{R + j\omega L} = \frac{1}{1 + j\omega L/R}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

At the corner frequency, $|H(\omega_c)| = 1/\sqrt{2}$, i.e.

$$\frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{\omega_c L}{R}\right)^2}} \longrightarrow 1 = \frac{\omega_c L}{R}$$

or $\omega_c = R/L$

Hence, $\omega_c = R/L = 2\pi f_c$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{10 \times 10^3}{2 \times 10^{-3}} = \underline{\underline{796 \text{ kHz}}}$$

Solution:05

$$H(\omega) = \frac{R \parallel \frac{1}{j\omega C}}{j\omega L + R \parallel \frac{1}{j\omega C}}$$

$$H(\omega) = \frac{\frac{R/j\omega C}{R + 1/j\omega C}}{j\omega L + \frac{R/j\omega C}{R + 1/j\omega C}}$$

$$H(\omega) = \frac{R}{R + j\omega L - \omega^2 RLC}$$

$$H(\omega) = \frac{0.25}{0.25 + j\omega - 0.25\omega^2}$$

$H(0) = 1$ and $H(\infty) = 0$ showing that this circuit is a lowpass filter.

Solution:06

$$H(\omega) = \frac{V_o}{V_i} = \frac{j\omega L}{R + j\omega L}$$

$H(0) = 0$ and $H(\infty) = 1$ showing that this circuit is a highpass filter.

$$H(\omega_c) = \frac{1}{\sqrt{2}} = \frac{1}{\sqrt{1 + \left(\frac{R}{\omega_c L}\right)^2}} \longrightarrow 1 = \frac{R}{\omega_c L}$$

or $\omega_c = R/L$

Hence, $\omega_c = R/L = 2\pi f_c$

$$f_c = \frac{1}{2\pi} \cdot \frac{R}{L} = \frac{1}{2\pi} \cdot \frac{200}{0.1} = \underline{\underline{318.3 \text{ Hz}}}$$

Solution: 07

$$\omega_1 = 2\pi f_1 = 20\pi \times 10^3$$

$$\omega_2 = 2\pi f_2 = 22\pi \times 10^3$$

$$B = \omega_2 - \omega_1 = 2\pi \times 10^3$$

$$\omega_0 = \frac{\omega_2 + \omega_1}{2} = 21\pi \times 10^3$$

$$Q = \frac{\omega_0}{B} = \frac{21\pi}{2\pi} = 10.5$$

$$\omega_0 = \frac{1}{\sqrt{LC}} \rightarrow L = \frac{1}{\omega_0^2 C}$$

$$L = \frac{1}{(21\pi \times 10^3)(80 \times 10^{-12})} = 2.872 \text{ H}$$

$$B = \frac{R}{L} \rightarrow R = BL$$

$$R = (2\pi \times 10^3)(2.872) = 18.045 \text{ k}\Omega$$

Solution: o8

$$\mathbf{H}'(\omega) = \frac{j\omega RC}{1 + j\omega RC} = \frac{j\omega}{j\omega + 1/RC}$$

This has a unity passband gain, i.e. $H(\infty) = 1$.

$$\frac{1}{RC} = \omega_c = 50$$

$$\mathbf{H}^{\wedge}(\omega) = 10 \mathbf{H}'(\omega) = \frac{j10\omega}{50 + j\omega}$$

$$\mathbf{H}(\omega) = \underline{\underline{\frac{j10\omega}{50 + j\omega}}}$$

Solution: o9

(a)

$$\mathbf{V}_+ = \frac{1/j\omega C}{R + 1/j\omega C} \mathbf{V}_i, \quad \mathbf{V}_- = \mathbf{V}_o$$

Since $\mathbf{V}_+ = \mathbf{V}_-$,

$$\frac{1}{1 + j\omega RC} \mathbf{V}_i = \mathbf{V}_o$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{1}{1 + j\omega RC}$$

(b)

$$\mathbf{V}_+ = \frac{R}{R + 1/j\omega C} \mathbf{V}_i, \quad \mathbf{V}_- = \mathbf{V}_o$$

Since $\mathbf{V}_+ = \mathbf{V}_-$,

$$\frac{j\omega RC}{1 + j\omega RC} \mathbf{V}_i = \mathbf{V}_o$$

$$\mathbf{H}(\omega) = \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{j\omega RC}{1 + j\omega RC}$$

Solution: 10

$$Z_f = R_f \parallel \frac{1}{j\omega C_f} = \frac{R_f}{1 + j\omega R_f C_f}$$

$$Z_i = R_i + \frac{1}{j\omega C_i} = \frac{1 + j\omega R_i C_i}{j\omega C_i}$$

Hence,

$$\begin{aligned} \mathbf{H}(\omega) &= \frac{\mathbf{V}_o}{\mathbf{V}_i} = \frac{-Z_f}{Z_i} \\ &= \frac{-j\omega R_f C_i}{(1 + j\omega R_f C_f)(1 + j\omega R_i C_i)} \end{aligned}$$

This is a bandpass filter.

$\mathbf{H}(\omega)$ is similar to the product of the transfer function of a lowpass filter and a highpass filter.