

**JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY**  
**Electronics and Communication Engineering**  
**Electrical Science-I (15B11EC111)**  
**Tutorial Sheet: 4**

---

**Q.1[CO1]** For the circuit shown in Fig.1 determine the unknown current using KCL.

[ANS:  $I_5 = 2$  Amp,  $I_3 = 1.5$  Amp]

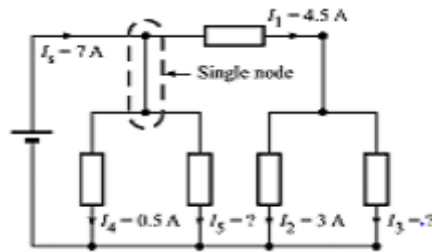


Fig. 1

**Q.2 [CO1]** Determine the node voltage at nodes B and C in the network shown in Fig.2.

[ANS:  $V_B = V_C = 114$  Volt]

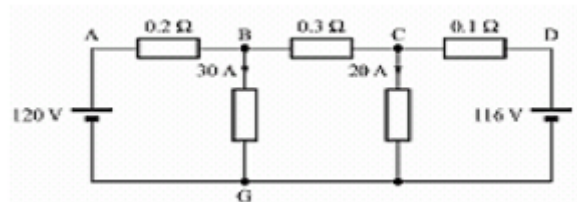


Fig. 2

**Q.3 [CO1]** Using loop current analysis, find the loop current shown in Fig. 3.

[ANS:  $I_1 = -0.25$  Amp,  $I_2 = -4.75$  Amp,  $I_3 = -4.0$  Amp]

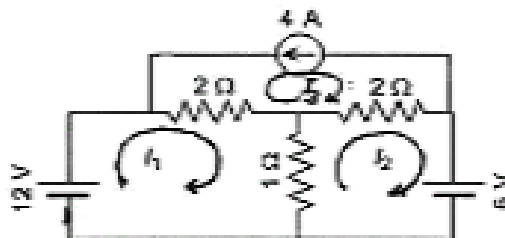


Fig. 3

**Q. 4 [CO1]** Determine the node voltage  $V_a$  for the circuit of Fig. 4.

[ANS:  $V_a = 7$  Volt]

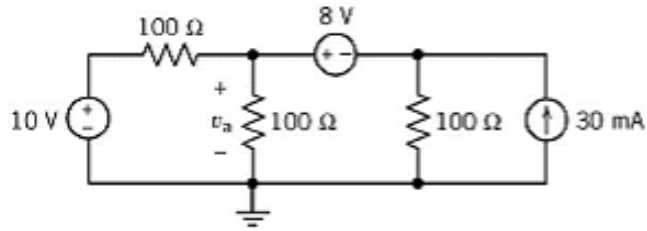


Fig.4

**Q. 5 [CO1]** The circled number in Fig. 5 is node number. The node voltage of this circuit are  $V_1 = 10$  V,  $V_2 = 14$  V and  $V_3 = 12$  V:

- Determine the value of current  $i_b$ .
- Determine the value of  $r$ , the gain of the CCVS.

[ANS: (a)  $i_b = -2$  Amp, (b) 4V/A]

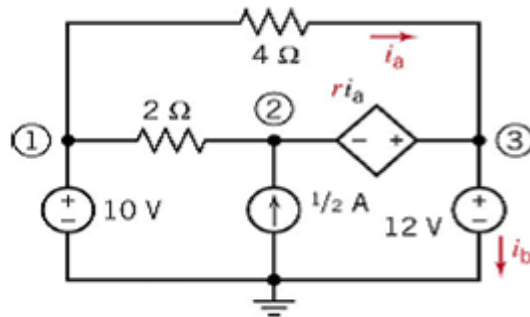


Fig. 5

**Q. 6 [CO1]** Determine the value of the voltage measure by the voltmeter in Fig. 6.

[ANS: 8 V]

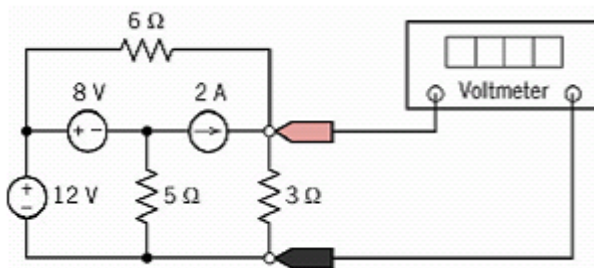


Fig. 6