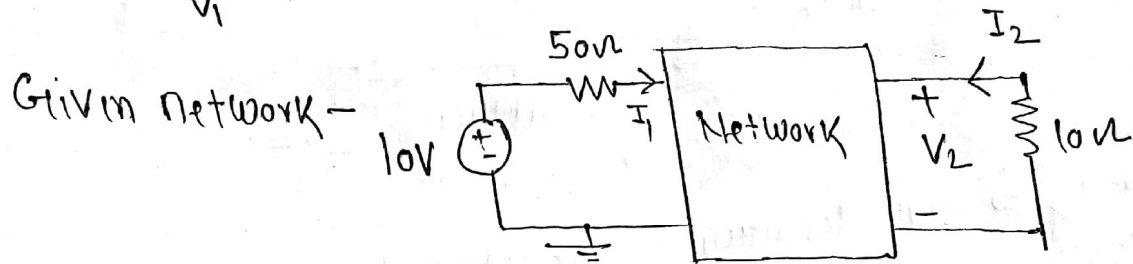


Solⁿ: 01

Tut-4 Solution

Given y matrix $\rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.2 & 0.4 \\ 0.3 & 0.6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$

Find $\frac{V_2}{V_1}$?



Voltage (V_2) from network -

$$V_2 = -I_2 \times 10 \quad \text{--- (i)}$$

From the y -matrix -

$$I_1 = 0.2 V_1 + 0.4 V_2 \quad \text{--- (ii)}$$

$$I_2 = 0.3 V_1 + 0.6 V_2 \quad \text{--- (iii)}$$

Substitute the value I_2 from (i) into (iii)




$$-\frac{V_2}{10} = 0.3 V_1 + 0.6 V_2$$

$$-V_2 = 3 V_1 + 6 V_2$$

$$-7 V_2 = 3 V_1$$

$$\boxed{\frac{V_2}{V_1} = -\frac{3}{7} \text{ Volt}}$$

Soln: 02

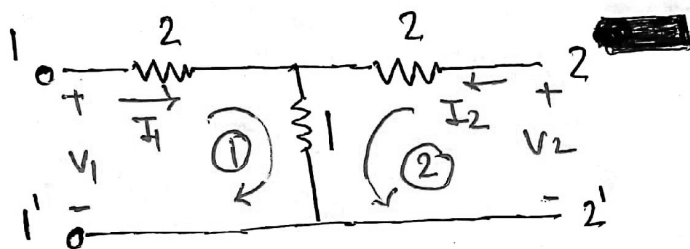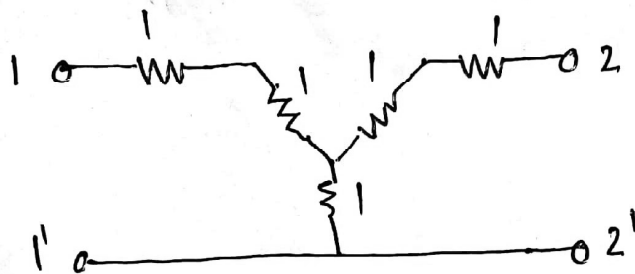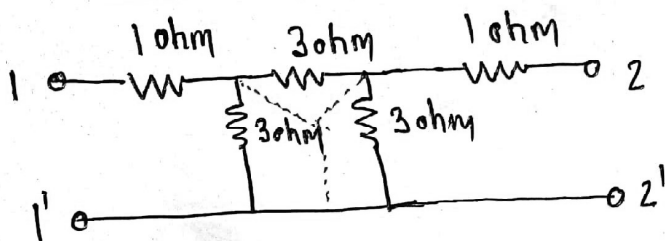

Apply KVL in mesh ①

$$V_1 = 2I_1 + 1(I_1 + I_2)$$

$$V_1 = 3I_1 + I_2 \quad \text{--- (i)}$$

Apply KVL in mesh ②

$$V_2 = 2I_2 + 1(I_2 + I_1)$$

$$V_2 = I_1 + 3I_2 \quad \text{--- (ii)}$$

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 1 & 3 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

compare from standard z-matrix

Note:

$\Delta \rightarrow Y$



$$R_A = \frac{R_1 \times R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 \times R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_1 \times R_3}{R_1 + R_2 + R_3}$$

Note:



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0} \quad Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0} \quad Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0}$$


$$Z_{11} = 3 \text{ ohm}, \quad Z_{12} = 1 \text{ ohm}$$

$$Z_{21} = 1 \text{ ohm}, \quad Z_{22} = 3 \text{ ohm}$$

Soln: 03

Given parameters values $\rightarrow Z_{11} = 4 \text{ ohm}, Z_{12} = 6 \text{ ohm}, Z_{21} = 8 \text{ ohm}, Z_{22} = 10 \text{ ohm}$

Given Network -

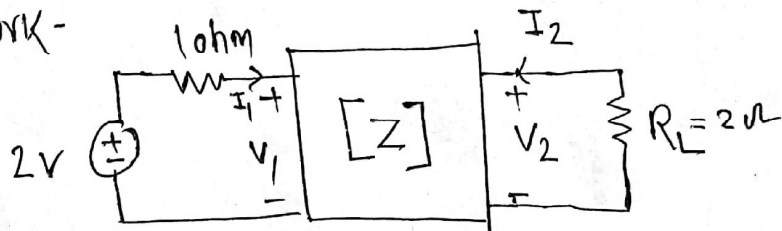

for Z parameters -

$$V_1 = I_1 Z_{11} + I_2 Z_{12} \quad \text{--- (i)}$$

$$V_2 = I_1 Z_{21} + I_2 Z_{22} \quad \text{--- (ii)}$$

From Network - $V_2 = -I_2 R_L \quad \text{--- (iii)}$

$$V_1 = 2 - I_1 \quad \text{--- (iv)}$$

Average Power deliver to $R_L \rightarrow$

$$P = I_2^2 R_L = \frac{V_2^2}{R_L} \quad \text{--- (v)}$$

Substitute V_1 from (iv) into (i)

$$2 - I_1 = I_1 Z_{11} + I_2 Z_{12}$$

$$2 - I_1 = 4I_1 + 6I_2$$

$$2 = 5I_1 + 6I_2 \quad \text{--- (v)}$$

Substitute V_2 from (iii) into (ii)

$$-I_2 R_L = I_1 Z_{21} + I_2 Z_{22}$$

$$-2I_2 = 8I_1 + 10I_2$$

$$0 = 8I_1 + 12I_2 \quad \text{--- (vi)}$$

By solving (v) and (vi) equation -

we get, $I_1 = 2 \text{ Amp}, I_2 = -\frac{4}{3} \text{ Amp}$

Therefore Power deliver to R_L


$$P = I_2^2 \times R_L = \frac{32}{9} \text{ Watts}$$

du

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0}; \quad h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}; \quad h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0}$$

if port b-b' is short circuited, $V_2=0$.

$$h_{11} = \left. \frac{V_1}{I_1} \right|_{V_2=0}; \quad V_1 = I_1 Z_{eq}$$

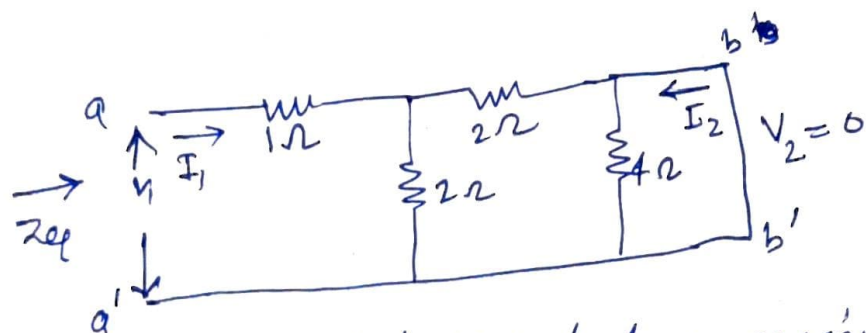

Z_{eq} the equivalent impedance as viewed from the port a-a' is 2Ω


$$V_1 = I_1 2V$$

$$h_{11} = \frac{V_1}{I_1} = 2\Omega$$

$$h_{21} = \left. \frac{I_2}{I_1} \right|_{V_2=0} \quad \text{when } V_2=0; \quad -I_2 = \frac{I_1}{2}$$

$$h_{21} = -\frac{1}{2}$$

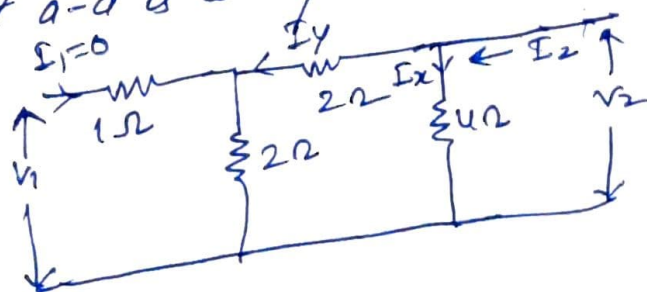if port a-a' is let open, $I_1=0$. ~~the circuit is the~~



$$h_{12} = \left. \frac{V_1}{V_2} \right|_{I_1=0}$$

$$V_1 = I_y 2; \quad I_y = \frac{I_2}{2}$$

$$V_2 = I_x 4; \quad I_x = \frac{I_2}{2}$$


$$h_{12} = \frac{V_1}{V_2} \bigg|_{I_1=0} = \frac{1}{2}$$

$$h_{22} = \left. \frac{I_2}{V_2} \right|_{I_1=0} = \frac{1}{2}\Omega$$


Soln: 08

Given parameters- $Z_{11} = 1\Omega$, $Z_{12} = 2\Omega$, $Z_{21} = 3\Omega$, $Z_{22} = 4\Omega$

Given Network-

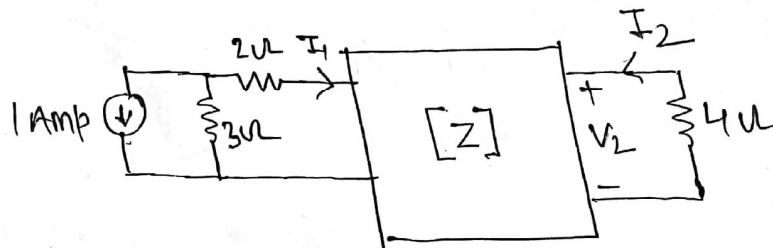

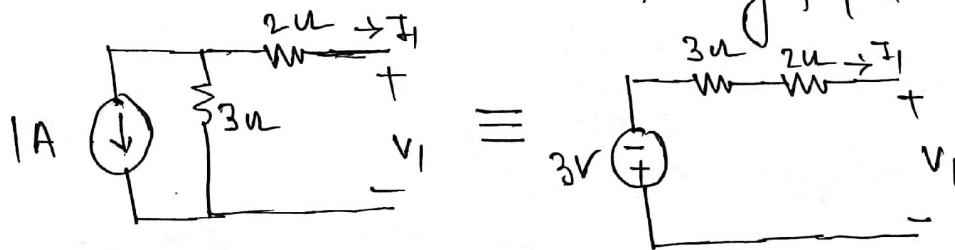The current source of 1Amp with 3Ω can be converted into equivalent voltage source as shown in the following figure



Apply KVL, we get, $V_1 = -3 - 5I_1 \rightarrow (i)$

From the given value of Z parameters-

$$V_1 = I_1 + 2I_2 \rightarrow \text{---} (ii)$$

$$V_2 = 3I_1 + 4I_2 \rightarrow \text{---} (iii)$$

From the Network- $V_2 = -4I_2 \rightarrow \text{---} (iv)$

Substitute the V_1 from (i) into (ii)

$$-3 - 5I_1 = I_1 + 2I_2$$

$$-3 = 6I_1 + 2I_2 \rightarrow (v)$$

Substitute the V_2 from (iv) into (iii)

$$-4I_2 = 3I_1 + 4I_2$$




$$I_2 = -\frac{3}{8}I_1 \rightarrow (vi)$$

Solving the equation (v) and (vi)
we get -

$$I_1 = -\frac{4}{7} \text{ Amp}$$

$$I_2 = \frac{3}{14} \text{ Amp}$$

Soln: 06

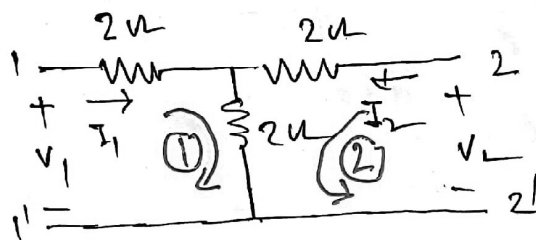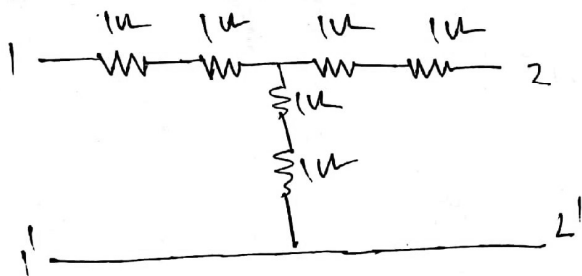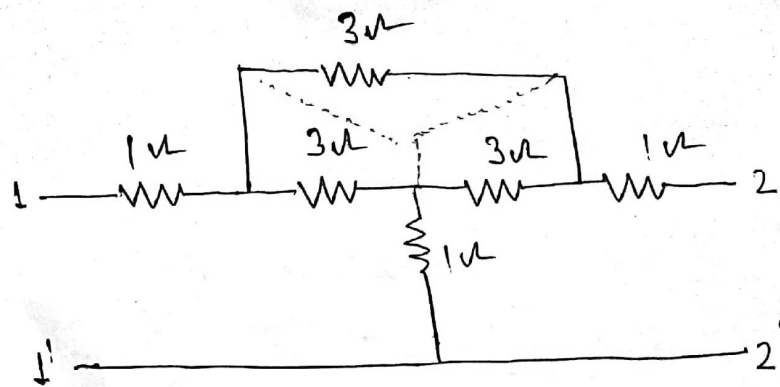

Apply KVL in mesh ①

$$V_1 = 2I_1 + 2(I_1 + I_2)$$

$$V_1 = 4I_1 + 2I_2 \quad \text{--- (i)}$$

Apply KVL in mesh ②

$$V_2 = 2I_2 + 2(I_1 + I_2)$$

$$V_2 = 2I_1 + 4I_2 \quad \text{--- (ii)}$$


In matrix form -

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 & 2 \\ 2 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Compare from standard z-matrix

Note:

Δ -Y

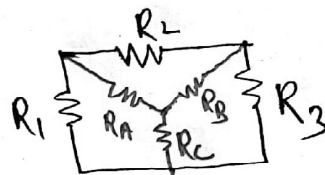

$$R_A = \frac{R_1 \times R_2}{R_1 + R_2 + R_3}$$

$$R_B = \frac{R_2 \times R_3}{R_1 + R_2 + R_3}$$

$$R_C = \frac{R_3 \times R_1}{R_1 + R_2 + R_3}$$

Note:

$$\begin{cases} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} \end{cases}$$

$$Z_{11} = 4 \text{ ohm}, Z_{12} = 2 \text{ ohm}$$

$$Z_{21} = 2 \text{ ohm}, Z_{22} = 4 \text{ ohm}$$