

Solutions to Tutorial Sheet-10

1. $V_2 = \frac{N_2}{N_1} \times V_1 = \frac{1}{12} \times 220 = 18.33 \text{ V}$; $V_m = V_2 \times \sqrt{2} = 18.33 \times \sqrt{2} = 25.93 \text{ V}$; $V_{dc} = \frac{V_m}{\pi} = \frac{25.92}{\pi} = 8.25 \text{ V}$;
 $PIV = V_m = 25.93 \text{ V}$

2. (a) $V_2 = \frac{N_2}{N_1} V_1 = \frac{1}{10} \times 220 = 22 \text{ V}$; $\therefore V_m = V_2 \times \sqrt{2} = 22 \times \sqrt{2} = 31.1 \text{ V}$; $I_m = \frac{V_m}{R_L + r_f} = \frac{31.1}{510} \approx 61 \text{ mA}$;
 $\therefore I_{dc} = \frac{I_m}{\pi} = 19.4 \text{ mA}$

(b) $\eta = \frac{40.6}{1 + r_f / R_L} \% = \frac{40.6}{1 + 10 / 500} \% = 39.8 \%$

(c) $PIV = V_m - V_T = 31.1 - 0.7 = 30.4 \text{ V}$

3. $N_1 : N_2 = 1000 : 50 = 20 : 1$, $V_{in} = 220 \text{ V}$, $R_L = 1 \text{ k}\Omega$

$V_2 = \frac{N_2}{N_1} V_1 = \frac{50}{1000} \times 220 = 11 \text{ V}$; $V_m = V_2 \times \sqrt{2} = 15.5 \text{ V}$

(a) $\therefore PIV = 2V_m = 31 \text{ V}$; (b) $V_{dc} = \frac{2V_m}{\pi} = \frac{2 \times 31}{\pi} = 9.9 \text{ V}$; (c) $I_{dc} = \frac{V_{dc}}{R_2} = \frac{9.9}{1000} = 9.9 \text{ mA}$

4. $V_{dc} = \frac{2(V_m - 2V_T)}{\pi}$; $\therefore V_m = \frac{\pi}{2} V_{dc} + 2V_T = \frac{\pi}{2} (15) + (0.7) = 24.95 \text{ V}$; $V_2 = \frac{V_m}{\sqrt{2}} = 17.64 \text{ V}$;

$\therefore \frac{N_1}{N_2} = \frac{V_1}{V_2} = \frac{220}{17.64} \approx 12.4$; $\therefore N_1 : N_2 \approx 12:1$

5. (a) $PIV = V_m - 2V_T = 20 - 0 = 20 \text{ V}$

(b) $I_m = (V_m - 2V_T) / (R_L + R_S + 2r_f) = \frac{20}{970 + 10 + 20} = 20 \text{ mA}$; $I_{dc} = \frac{2I_m}{\pi} = \frac{2 \times 20}{\pi} \text{ mA} = 12.7 \text{ mA}$

(c) $P_{dc} = I_{dc}^2 R_L = (12.7)^2 (970) \mu\text{W} = 156.5 \text{ mW}$

(d) $\eta = \frac{81.2}{1 + 2r_f / R_L} \% = \frac{81.2}{1 + 20 / 970} \% = 79.56 \%$


6. $V_m = 220 \times \sqrt{2} = 311 \text{ V}$; $V_{dc} = \frac{V_m}{\pi} = 105.4 \text{ V}$

7. (a) $I_{\max} = \frac{P_{\max}}{V_T} = \frac{14 \text{ mW}}{0.7 \text{ V}} = 20 \text{ mA}$

(b) $R_L = 5.6 \text{ k}\Omega \parallel 47 \text{ k}\Omega = 5 \text{ k}\Omega$; $I_{\max} = \frac{V_m - V_T}{R_L} = \frac{150 \text{ V} - 0.7 \text{ V}}{5 \text{ k}\Omega} = 29.86 \text{ mA}$

(c) $I_D = \frac{I_{\max}}{2} = 14.93 \text{ mA}$; (d) Yes; (e) $I_D = 29.86 \text{ mA} > I_{\max} = 20 \text{ mA}$

8.

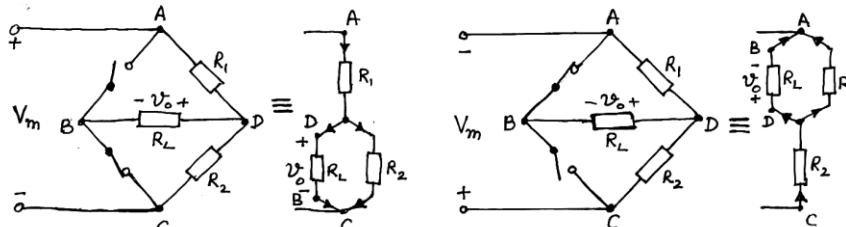


(a) For positive half-cycle.

(b) For negative half-cycle.


(a) $V_{o(\max)} = V_{DB(\max)} = V_m \frac{(R_L \parallel R_2)}{R_1 + (R_L \parallel R_2)} = (150 \text{ V}) \times \frac{1.1 \text{ k}\Omega}{2.2 \text{ k}\Omega + 1.1 \text{ k}\Omega} = 50 \text{ V}$

(b) $V_{o(\max)} = V_{DB(\max)} = V_m \frac{(R_L \parallel R_1)}{R_2 + (R_L \parallel R_1)} = (150 \text{ V}) \times \frac{1.1 \text{ k}\Omega}{2.2 \text{ k}\Omega + 1.1 \text{ k}\Omega} = 50 \text{ V}$; and $V_{dc} = \frac{2V_m}{\pi} = 31.8 \text{ V}$

9.

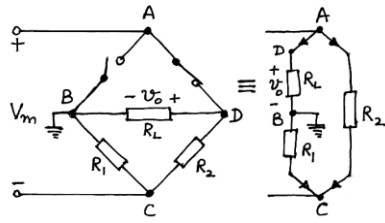

(a) For positive half-cycle.

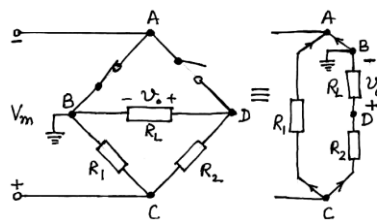


(b) For negative half-cycle.

$$V_m = \frac{V_{pp}}{2} = \frac{200 \text{ V}}{2} = 100 \text{ V}$$


$$(a) \quad V_{o(\max)} = V_{DB(\max)} = V_m \frac{R_L}{R_L + R_1} = (100 \text{ V}) \times \frac{2.2 \text{ k}\Omega}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 50 \text{ V}$$
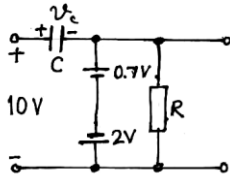
$$(b) \quad V_{o(\max)} = V_{DB(\max)} = V_m \frac{R_L}{R_L + R_2} = (100 \text{ V}) \times \frac{2.2 \text{ k}\Omega}{2.2 \text{ k}\Omega + 2.2 \text{ k}\Omega} = 50 \text{ V}; \text{ and } V_{dc} = \frac{2V_m}{\pi} = 31.8 \text{ V}$$



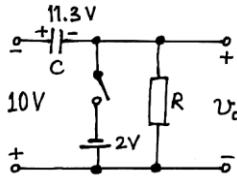
(a) Charging of capacitor during first positive half-cycle.

$$v_C = -0.7 \text{ V} + 2 \text{ V} + 10 \text{ V}$$



(b) Circuit during negative half-cycle.

$$v_o = -10 \text{ V} - 11.3 \text{ V}$$

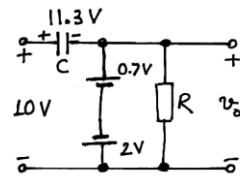

(c) Circuit during positive half-cycle.

$$v_o = -2 \text{ V} + 0.7 \text{ V}$$