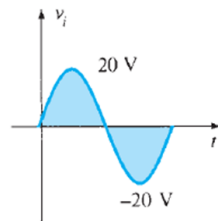


**JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY**  
**Electronics and Communication Engineering**  
**Electrical Science-II (15B11EC211)**  
**Tutorial Sheet: 11**

---

**Q.1[CO3]** Determine  $V_0$  for each network as shown in figure 1 and 2 for the input signal. Consider diode is a silicon diode.



Input signal

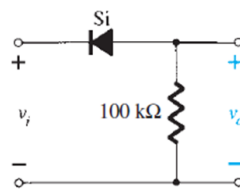


Fig. 1



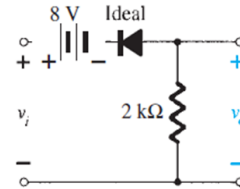


Fig. 2

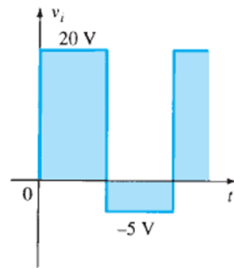**Q.2 [CO3]** Determine  $V_0$  for each network as shown in figure 3 and 4 for the input signal. Consider diode is a silicon diode.




Input signal

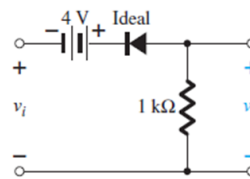

(a)


Fig. 3

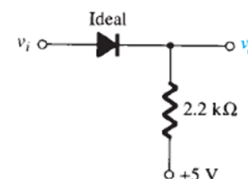


(b)

Fig. 4

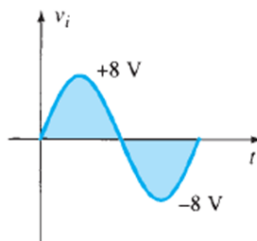**Q.3[CO3]** Determine  $V_0$  for each network as shown in figure 5 and 6 for the input signal. Consider diode is a silicon diode.




Input signal

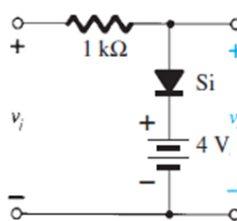

(a)


Fig. 5

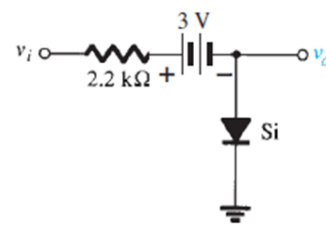

(b)

Fig. 6

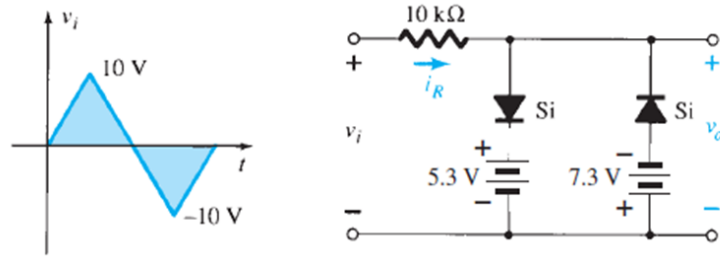
**Q.4[CO3]** Sketch  $I_R$  and  $V_o$  for the network is shown in figure 7 for the input signal. Consider diode is a silicon diode.



Input signal

Fig. 7

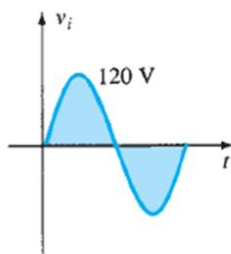**Q.5 [CO3]** Sketch  $V_o$  for the network is shown in figure 8 and 9 for the input signal.



Input signal

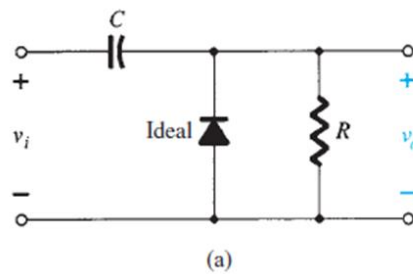


Fig. 8


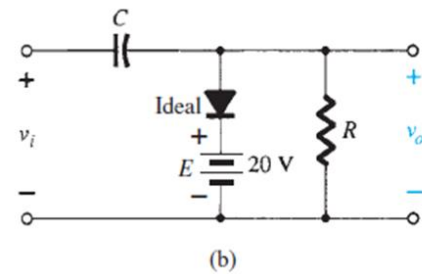


Fig. 9

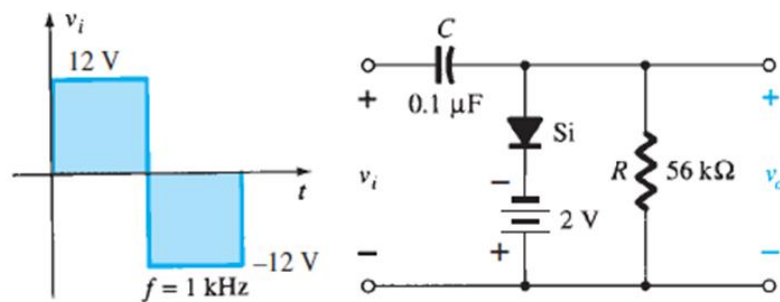**Q.6[CO3]** For the network of figure 10.

- Calculate 5 time constant ( $5\tau$ ).
- Compare  $5\tau$  to half the period of the applied signal.
- Sketch  $V_o$ .



Input signal

Fig. 10