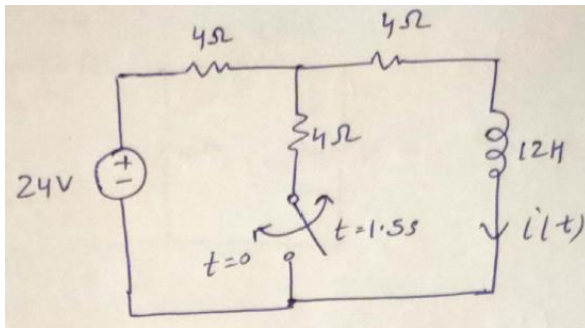


**JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY**  
**Electronics and Communication Engineering**  
**Electrical Science-II (15B11EC211)**  
**Tutorial Sheet: 2**

**Q1. [CO1]** The circuit shown in Fig. 1 is at steady state before the switch closes at time  $t=0$ . The switch remains closed for 1.5 s and then opens. Determine the inductor current  $i(t)$  for  $t>0$ .



$$i(t) = \begin{cases} 2 + e^{-0.5t} \text{ A} & 0 < t < 1.5 \text{ s} \\ 3 - 0.53e^{-0.667(t-1.5)} \text{ A} & t > 1.5 \end{cases}$$

Fig. 1

**Q2. [CO1]** For the circuit shown in Fig. 2, calculate the value of inductor current  $i_L(t)$  and  $i_{12\Omega}(t)$  for  $t>0$ .


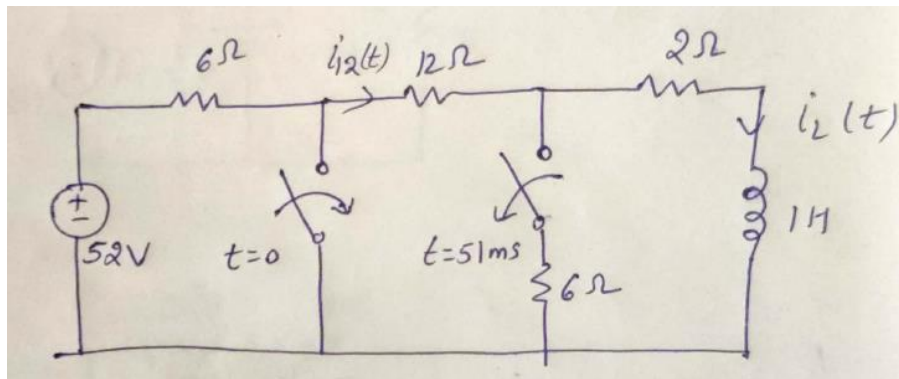


Fig. 2

$$i_L(t) = \begin{cases} 2 & t < 0 \\ 2e^{-6t} & 0 < t < 0.051 \\ 1.473e^{-14(t-0.051)} & t > 0.051 \end{cases} \quad i_{12}(t) = \begin{cases} 2.67 & t < 0 \\ \frac{2}{3}e^{-6t} & 0 < t < 0.051 \\ 1.473e^{-14(t-0.051)} & t > 0.051 \end{cases}$$

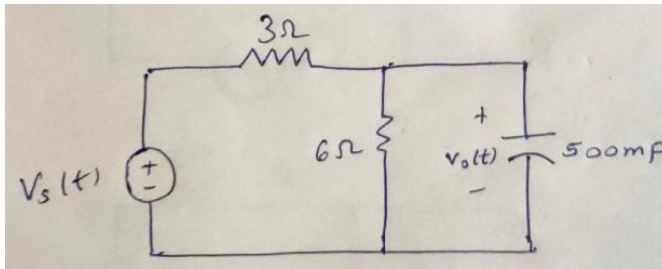
**Q3. [CO1]** The input to the circuit shown in Fig. 3 is the voltage  $V_s(t) = 3 + 3u(t)$  V. Determine the output voltage  $V_o(t)$  across capacitor for  $t > 0$ .



$$V_o(t) = \begin{cases} 2 & t < 0 \\ 4 - 2e^{-6t} & t > 0 \end{cases}$$

Fig. 3

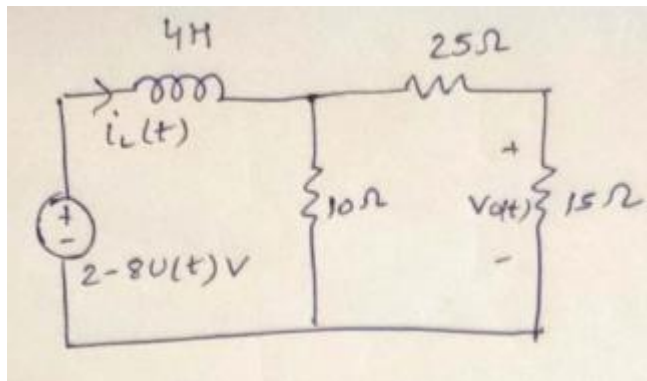
**Q4. [CO1]** Determine the voltage  $V_o(t)$  in the circuit shown in Fig. 4.



$$V_o(t) = -2.25 + 3e^{-2t} \text{ V}$$

Fig. 4

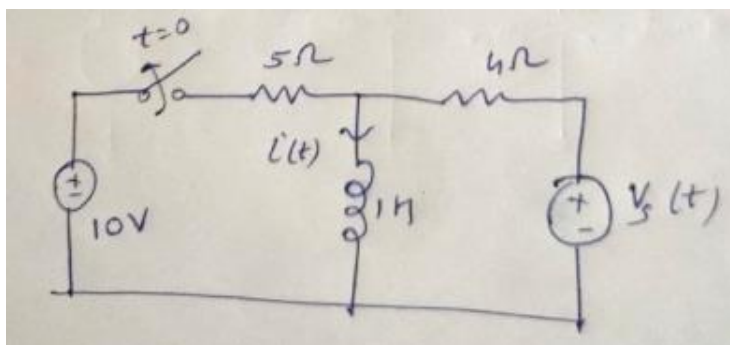
**Q5. [CO1]** For the circuit shown in Fig. 5, find the current  $i(t)$  for  $t > 0$ , when  $V_s(t) = 10e^{-2t}u(t)$  V. Assume the circuit is in steady state at  $t=0$ .



$$i(t) = -3e^{-4t} + 5e^{-2t} \text{ A for } t > 0$$

Fig. 5

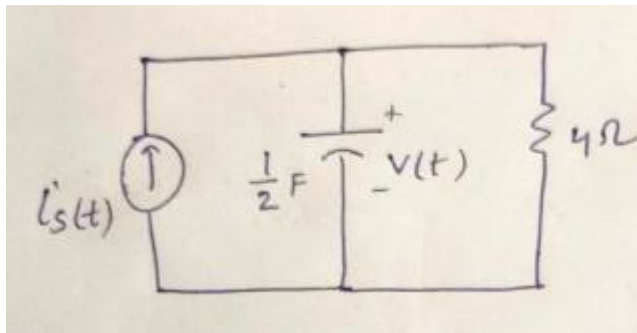**Q6. [CO1]** Find the response  $v(t)$  for  $t > 0$  for the circuit shown in Fig. 6. The initial voltage  $v(0) = 0$  and the current source is  $i_s(t) = (10\sin 2t)u(t)$  A.



$$V(t) = \frac{160}{17}e^{-1/2t} + \frac{40}{17}\sin 2t - \frac{160}{17}\cos 2t \text{ V}$$

Fig. 6

**Q7. [CO1]** For the given circuit shown in Fig. 7, determine the response of inductor current  $i_L(t)$  and voltage  $V_{24\Omega}(t)$  across  $24\Omega$  resistor for  $t > 0$ .

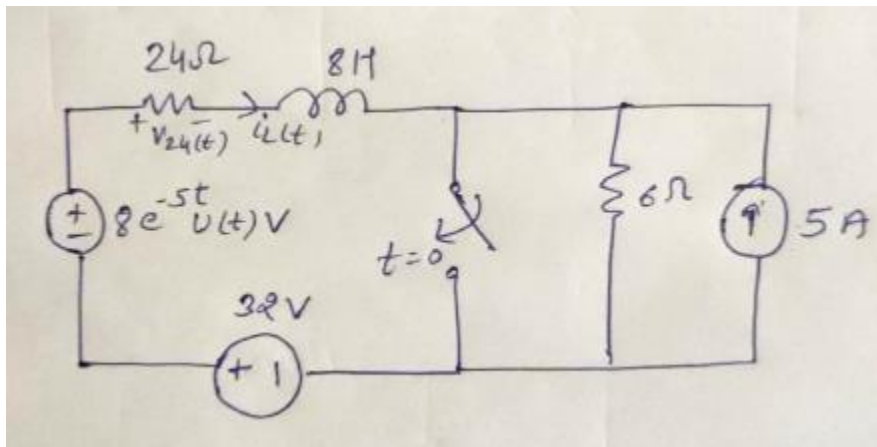


Fig. 7

$$i_L(t) = \frac{4}{3} - \frac{1}{2}e^{-5t} - \frac{23}{30}e^{-3t} \text{ A} \quad V_{24\Omega}(t) = 32 - 12e^{-5t} - \frac{92}{5}e^{-3t}$$