

Electrical Science-1 (15B11EC111)
TUTORIAL 2: Solution

Q1. Find the power supplied by the VCCS in Fig. 1.1.

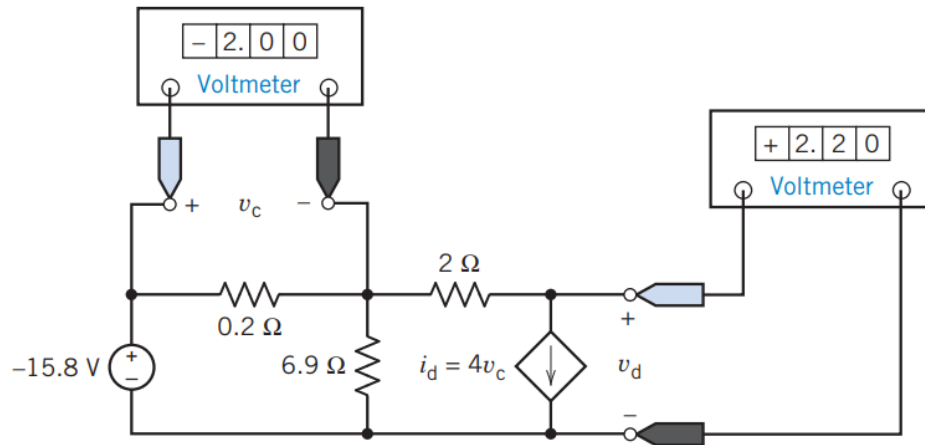


Fig. 1.1

Solution:

$$v_c = -2 \text{ V},$$

$$i_d = 4 v_c = -8 \text{ A and } v_d = 2.2 \text{ V}$$

i_d and v_d adhere to the passive convention so

$$P = v_d i_d = - (2.2) (8) = -17.6 \text{ W}$$

is the power received by the dependent source. The power supplied by the dependent source is 17.6 W.

Q.2 A current source and a voltage source are connected in parallel with a resistor as shown in Fig. 1.2. All of the elements connected in parallel have the same voltage v_s in this circuit. Suppose that $v_s = 15 \text{ V}$, $i_s = 3 \text{ A}$, and $R = 5 \Omega$.

(a) Calculate the current i in the resistor and the power absorbed by the resistor. (b) Change the current source current to $i_s = 5 \text{ A}$ and recalculate the current i in the resistor and the power absorbed by the resistor.

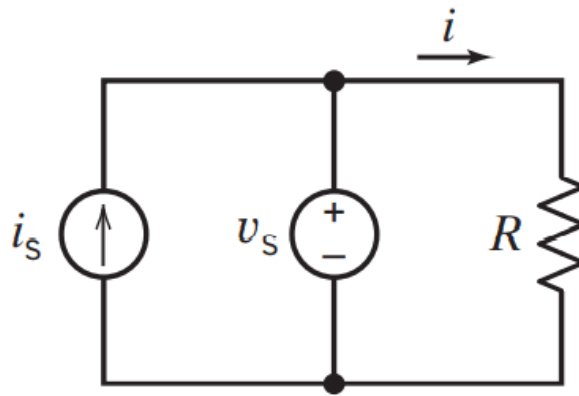


Fig. 1.2

Solution:

(a) $i = v_s / R = 15/5 = 3\text{ A}$
 $P = R i^2 = 45\text{ W}$

- (b) i and P do not depend on i_s .
 The values of i and P are 3 A and 45 W , both when $i_s = 3\text{ A}$ and when $i_s = 5\text{ A}$.

Q.3 Using Kirchhoff's laws, determine the values of i_2 , i_4 , v_2 , v_3 , and v_6 in Fig. 1.3.

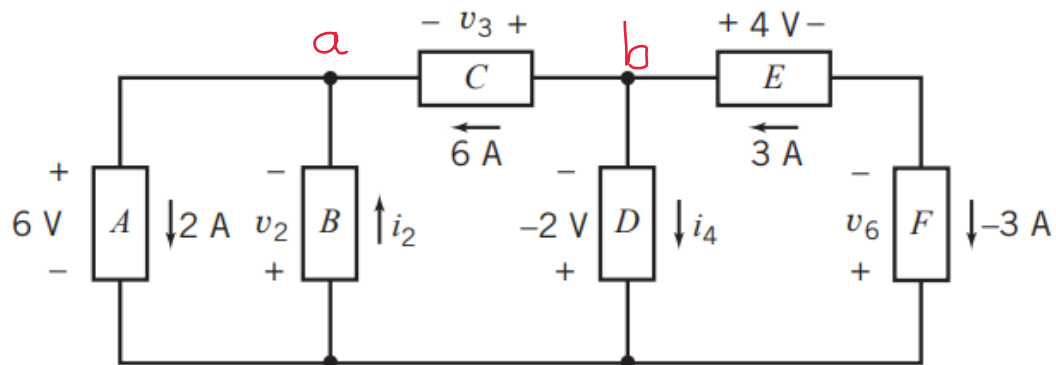


Fig. 1.3

Solution:

Apply KCL at node a to get $2 = i_2 + 6 = 0 \Rightarrow i_2 = -4 \text{ A}$

Apply KCL at node b to get $3 = i_4 + 6 \Rightarrow i_4 = -3 \text{ A}$

Apply KVL to the loop consisting of elements A and B to get

$$-v_2 - 6 = 0 \Rightarrow v_2 = -6 \text{ V}$$

Apply KVL to the loop consisting of elements C , D , and A to get

$$-v_3 - (-2) - 6 = 0 \Rightarrow v_4 = -4 \text{ V}$$

Apply KVL to the loop consisting of elements E , F and D to get

$$4 - v_6 + (-2) = 0 \Rightarrow v_6 = 2 \text{ V}$$

Check: The sum of the power supplied by all branches is

$$-(6)(2) - (-6)(-4) - (-4)(6) + (-2)(-3) + (4)(3) + (2)(-3) = -12 - 24 + 24 + 6 + 12 - 6 = 0$$

Q.4 Determine the voltage measured by the voltmeter in the circuit shown in Fig. 1.4.

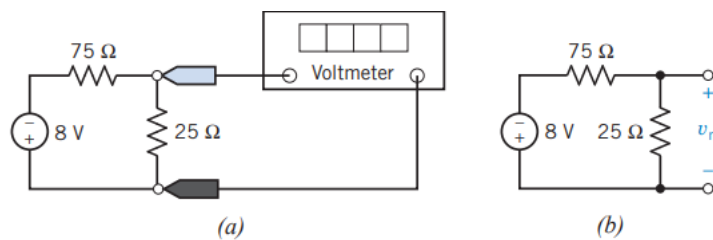


Fig. 1.4

Solution:

$$v_m = \frac{25}{25 + 75}(-8) = -2\text{V}$$

Q.5 Consider the two similar voltage divider circuits shown in Fig. 1.5. Use voltage division to determine the values of the voltage v_2 in Fig. 1.5(a) and the voltage v_b in Fig. 1.5(b).

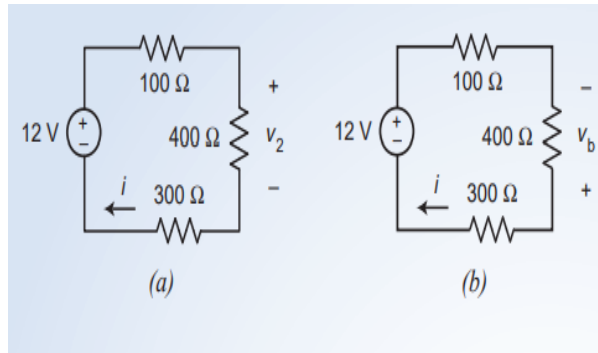


Fig. 1.5

Ans $v_2 = 6V$ and $v_b = -6V$

Solution:

- First, consider the circuit shown in Figure 1.5a. This circuit is an example of a single loop circuit like the circuit shown in Figure 1.5. The 100, 400, and 300Ω resistors are connected in series. The current in the loop is given by

$$i = \frac{12}{100+400+300} = 0.015 \text{ A} = 15\text{mA}$$

- We can calculate the value of v_2 using voltage division:

$$v_2 = \frac{400}{100+400+300} (12) = 6V$$

- As a check, notice that $6 = v_2 = 400(i) = 400(0.015)$
- Next, consider the circuit shown in Figure 1.5b. This circuit is also an example of a single loop circuit. Again, the current in the loop is given by

$$i = \frac{12}{100 + 400 + 300} = 0.015 \text{ A} = 15\text{mA}$$

- Notice that the voltage v_b in Figure 1.5b is the same voltage as the voltage v_2 in Figure 1.5a, except for polarity. Consequently

$$v_2 = -v_b$$

- Therefore

$$v_b = \frac{400}{100 + 400 + 300} (12) = -6V$$

Q.6 Use current division to determine the currents i_1 , i_2 , i_3 , and i_4 in the circuit shown in Fig. 1.6.

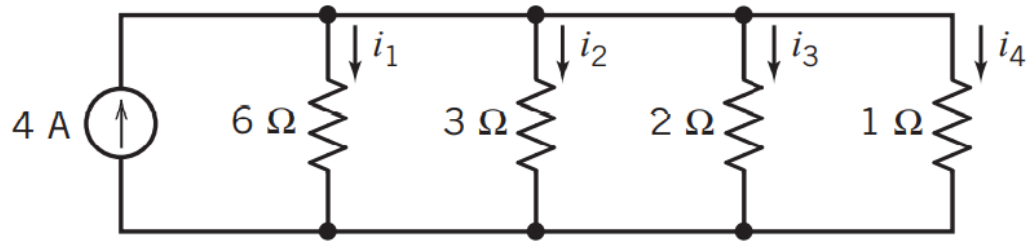


Fig. 1.6

Solution: Applying current divider rule:

$$i_1 = \frac{\frac{1}{6}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + \frac{1}{1}} 4 = \frac{1}{1+2+3+6} 4 = \underline{\underline{\frac{1}{3} \text{ A}}}$$

$$i_2 = \frac{\frac{1}{3}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + \frac{1}{1}} 4 = \underline{\underline{\frac{2}{3} \text{ A}}};$$

$$i_3 = \frac{\frac{1}{2}}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + \frac{1}{1}} 4 = \underline{\underline{1 \text{ A}}}$$

$$i_4 = \frac{1}{\frac{1}{6} + \frac{1}{3} + \frac{1}{2} + 1} 4 = \underline{\underline{2 \text{ A}}}$$