

Jaypee Institute of Information Technology, Noida
T-1 Examination, EVEN Semester-2017
B.Tech.II Semester

Course Title: Electrical Science-II/Basic Electronics Devices and Circuits
Course Code: 15B11EC211/10B11EC211
Max Marks: 20

Max Time: 1 Hour

All questions are compulsory.

- Q1. Find the current $i(t)$ after 0.2sec has elapsed for the circuit diagram shown in Fig.1. 2

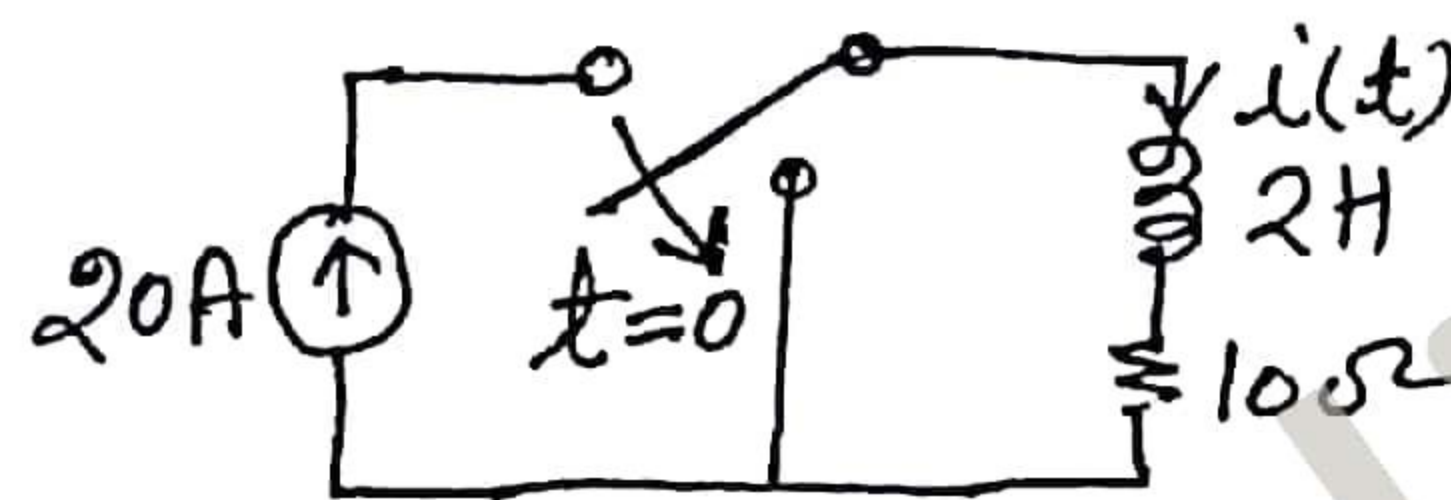


Fig. 1.

- Q2. Find the $v(t)$ for $t > 0$, for the circuit shown in Fig.2. Assuming $i(0)=0$ and $v(0)=0$. 5

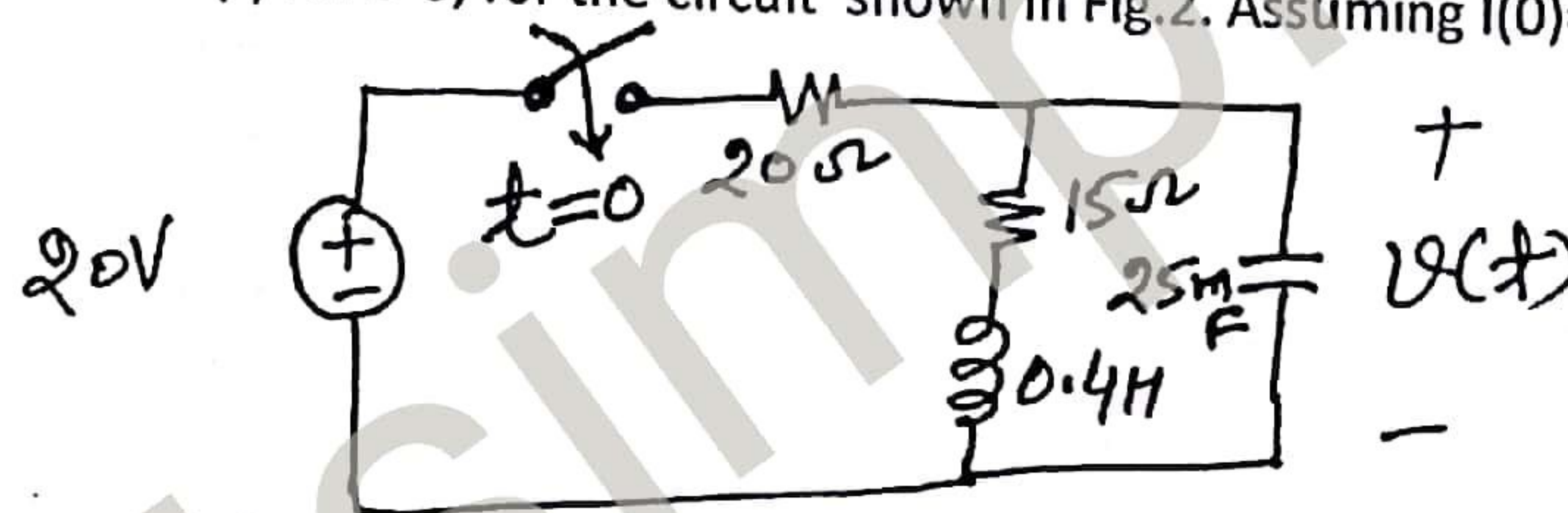


Fig. 2.

- Q3. Find the value of $i(t)$ for the circuit given in Fig.3. 4

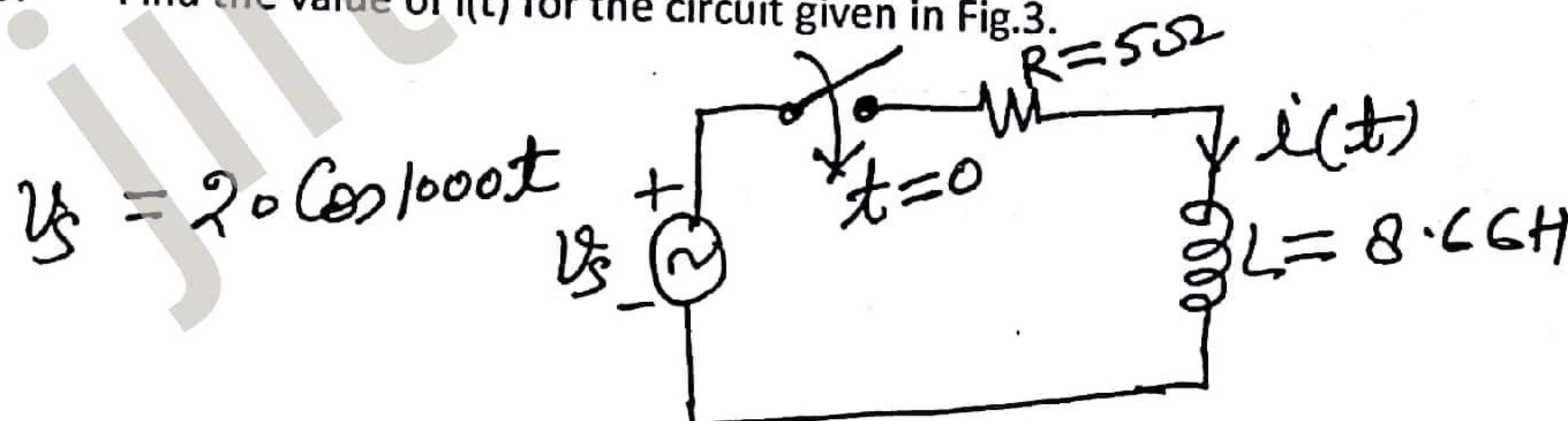


Fig. 3.

- Q4. Find the output voltage of the OPAMP circuit shown in Fig.4. 2


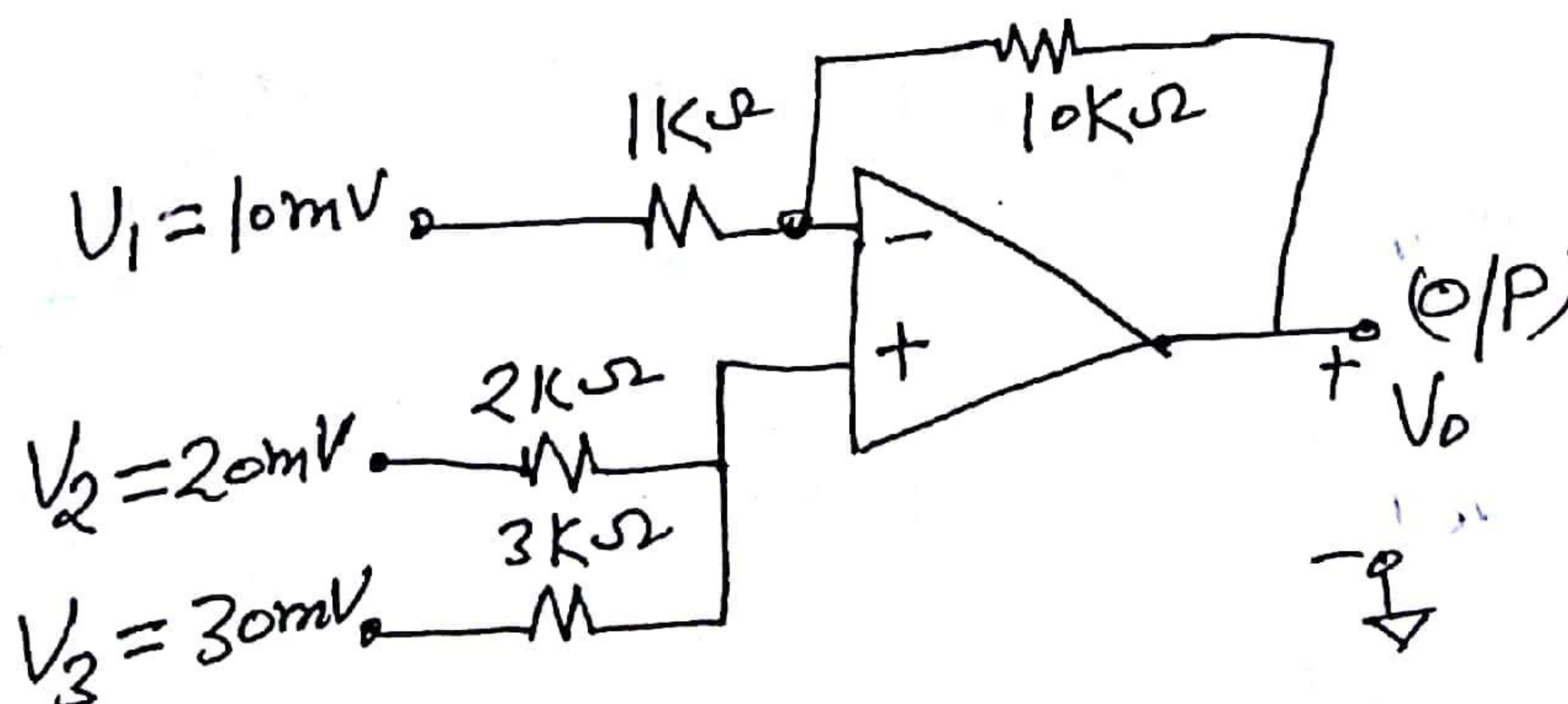


Fig. 4

✓ Q5. Draw the output waveform for the circuit shown in Fig.5.

2

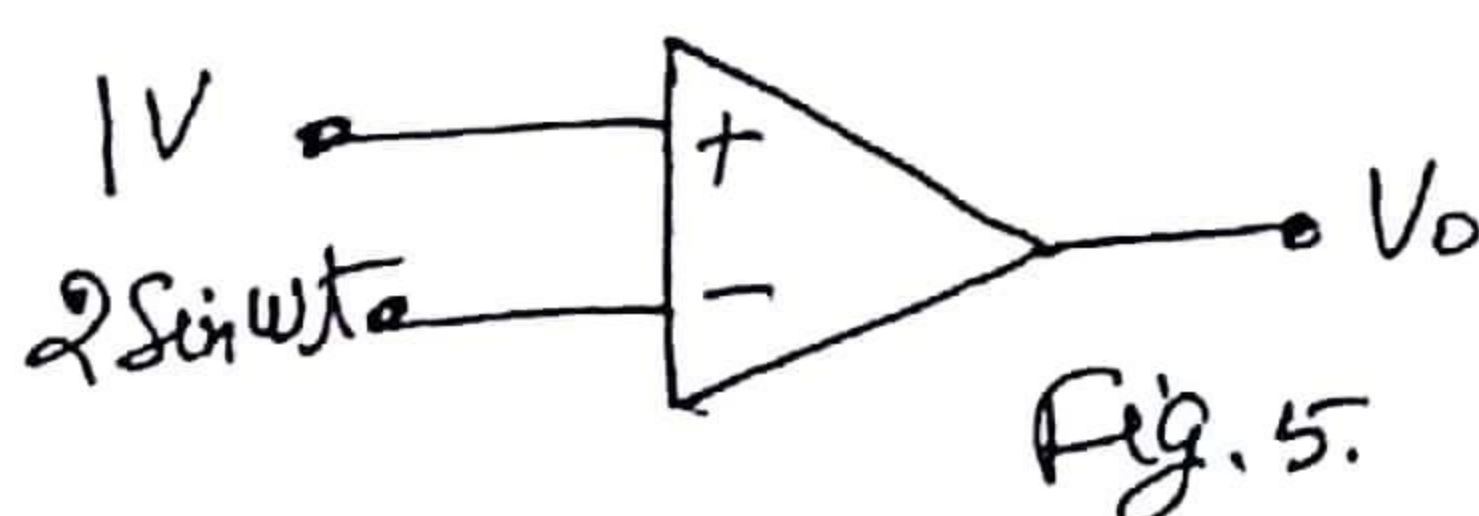

- ✓ Q6. (i) When a series RC circuit is connected to a voltage V at $t=0$, the current passing through the circuit at $t=0^+$ is 5*1
- a) 0 b) infinity c) 1 d) V/R
- (ii) Inductor does not allow sudden changes in
a) voltage b) power c) current d) all of the above
- (iii) In the common mode,
a) both inputs are grounded
b) the output is connected to ground.
c) an identical signal appears on both the inputs
d) the output signal is in-phase with input.
- (iv) If $A_{DM}=3500$ and $A_{CM}=0.35$, the CMRR is
a) 1225
b) 10,000
c) 90 dB
d) None of these
- (v) The ideal OPAMP has the following characteristics.
a) $R_i=\infty$, $A=\infty$, $R_o=0$
b) $R_i=0$, $A=\infty$, $R_o=0$
c) $R_i=\infty$, $A=\infty$, $R_o=\infty$
d) $R_i=0$, $A=\infty$, $R_o=\infty$

XXXXX ALL THE BEST XXXXX