



Digital Systems

18B11EC213

Module 1: Boolean Function Minimization Techniques and Combinational Circuits-12

Dr. Saurabh Chaturvedi


Combinational Logic Circuits

- Two classes of logic circuits:

- ❖ combinational

- ❖ sequential


- **Combinational Circuit:**

 

Each output depends entirely on the immediate (present) inputs.

Cont..


■ Sequential Circuit:

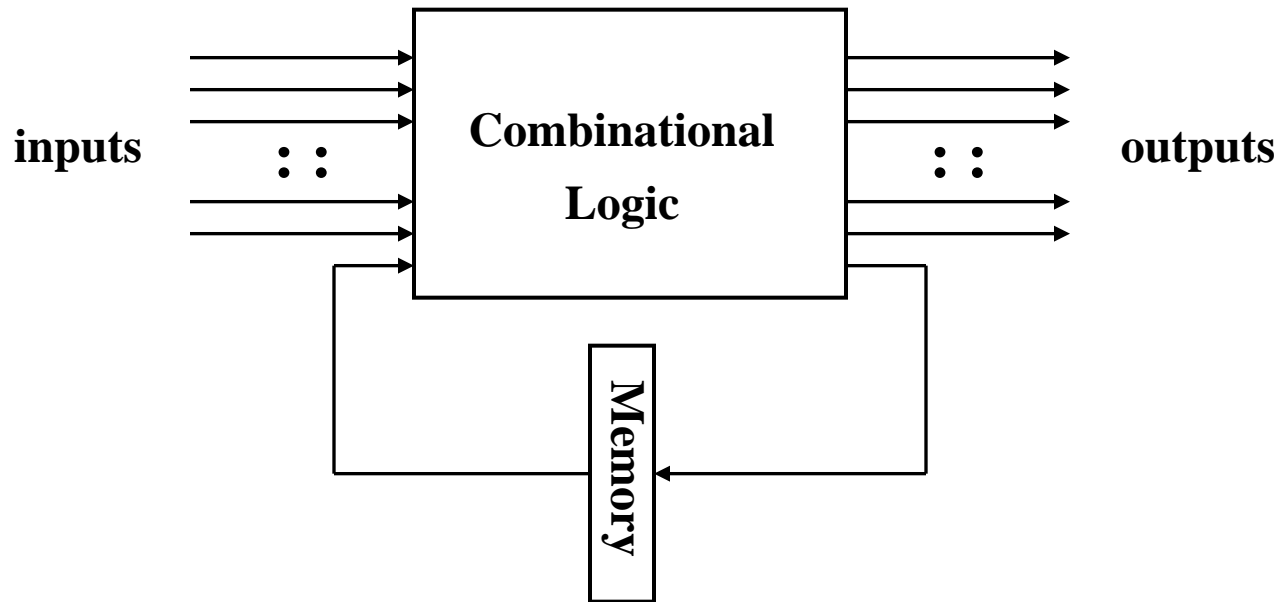

Output depends on both present and past inputs.
Memory (via feedback loop) contains past information.

Analysis Procedure

 - Analyze the function of the given combinational logic circuit:



Steps:

1. Label the inputs and outputs.
2. Obtain the functions of intermediate points and the outputs.
3. Draw the truth table.
4. Deduce the functionality of the circuit ➡ half adder

A	B	(A+B)	(A'+B')	F1	F2
0	0	0	1	0	0
0	1	1	1	1	0
1	0	1	1	1	0
1	1	1	0	0	1

Design Methods

- Different combinational circuit design methods:
 - ❖ Gate-level method (with logic gates)
 - ❖ Block-level design method
- Design methods make use of logic gates and useful functional blocks.
 - ❖ These are available as integrated circuit (IC) chips.

Gate-level Design: Half Adder


- Design procedure:

- 1) State Problem

Example: Build a **Half Adder** to add two bits

- 2) Determine and label the inputs and outputs of circuit.

 Example: Two inputs and two outputs labelled, as follows:



S: Sum

C: Carry

- 3) Draw truth table.

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Cont..


4) Obtain the simplified Boolean function from truth table:

$$C = X.Y$$

$$S = X'.Y + X.Y' = X \oplus Y$$

X	Y	C	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

5) Draw the logic diagram.

 

Half Adder

Gate-level Design: Full Adder


- Half adder adds up only two bits.
- To add two binary numbers, we need to add 3 bits (including the carry).

■ Example:

		1	1	1	carry	
		0	0	1	1	X
+		0	1	1	1	Y
		1	0	1	0	S

This addition operation requires a **Full Adder** circuit.

 A full adder can be made using two half adders.



Cont..

■ Truth table:

X	Y	Z	C	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Note:

Z: carry in (to the current position)

C: carry out (to the next position)

		C			
		YZ			
		00	01	11	10
X	0			1	
	1		1	1	1

Using K-map, the simplified SOP forms:

$$C = X.Y + X.Z + Y.Z$$

$$S = X'.Y'.Z + X'.Y.Z' + X.Y'.Z' + X.Y.Z$$

		S			
		YZ			
		00	01	11	10
X	0		1		1
	1	1		1	

Cont..

- Alternative formulae using algebraic manipulation:

$$\begin{aligned}C &= X.Y + X.Z + Y.Z \\&= X.Y + X.(Y+Y').Z + (X+X').YZ \\&= X.Y + XYZ + XY'Z + XYZ + X'YZ \\&= X.Y (1+Z) + (X\oplus Y).Z \\&= X.Y + (X\oplus Y).Z\end{aligned}$$


$$\begin{aligned}S &= X'.Y'.Z + X'.Y.Z' + X.Y'.Z' + X.Y.Z \\&= X'.(Y'.Z + Y.Z') + X.(Y'.Z' + Y.Z) \\&= X'.(Y\oplus Z) + X.(Y\oplus Z)' \\&= X\oplus(Y\oplus Z) \\&= X\oplus Y\oplus Z\end{aligned}$$

Cont..

- Full adder circuit using the following formulae:

$$C = X.Y + (X \oplus Y).Z$$

$$S = (X \oplus Y) \oplus Z$$

 


Full adder is made using two half adders and one OR gate.

Cont..

- Full adder circuit using the following formulae:

$$C = X.Y + (X \oplus Y).Z$$

$$S = (X \oplus Y) \oplus Z$$

 

Full adder is designed using two half adders and one OR gate.

Gate-level Design: Half Subtractor


1) Obtain the simplified Boolean functions from truth table:

$$B = X'.Y$$

$$D = X'.Y + X.Y' = X \oplus Y$$

X	Y	B	D
0	0	0	0
0	1	1	1
1	0	0	1
1	1	0	0

2) Draw the logic diagram.

 

D: Difference

B: Borrow

Gate-level Design: Full Subtractor

- Full subtractor has 3 inputs:
 - Two data inputs
 - One borrow input


$$B_{i+1} = X_i'Y_i + X_i'B_i + Y_iB_i$$

$$D_i = X_i \oplus Y_i \oplus B_i$$

D_i : Difference

B_i : Borrow in

B_{i+1} : Borrow out

 

(a)

X_i	Y_i	B_i	B_{i+1}	D_i
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	1	0
1	0	0	0	1
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1


(b)

Block-Level Design Method

- More complex circuits can be built using the block-level method.
- In general, block-level design method (as opposed to gate-level design) relies on algorithms or formulae of the circuit, which are obtained by decomposing the main problem to sub-problems recursively (until small enough to be directly solved by blocks of circuits).

Cont.. 4-bit Parallel Adder

 - Consider a circuit to add two 4-bit numbers together and a carry-in to produce a 5-bit result:




Black-box view of 4-bit parallel adder

5-bit result is sufficient because the largest result is:

$$(1111)_2 + (1111)_2 + (1)_2 = (11111)_2$$

Cont.. 4-bit Parallel Adder

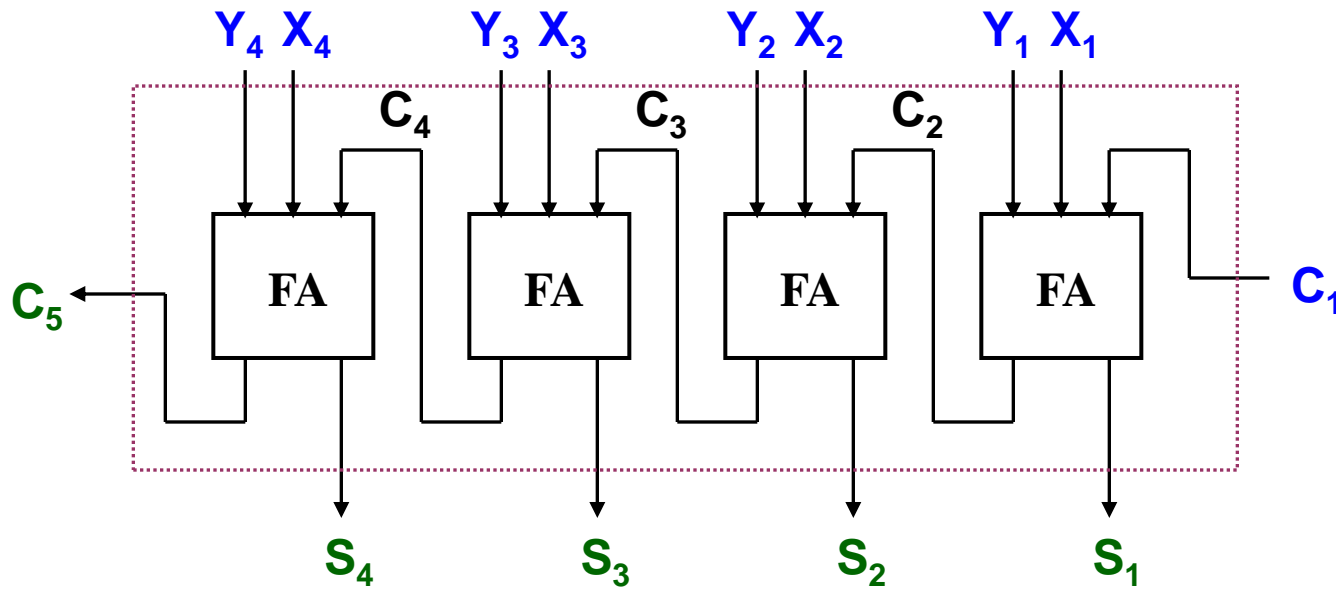
- Cascading four full adders via their carries:



■ Input
■ Output

Cont.. 16-bit Parallel Adder

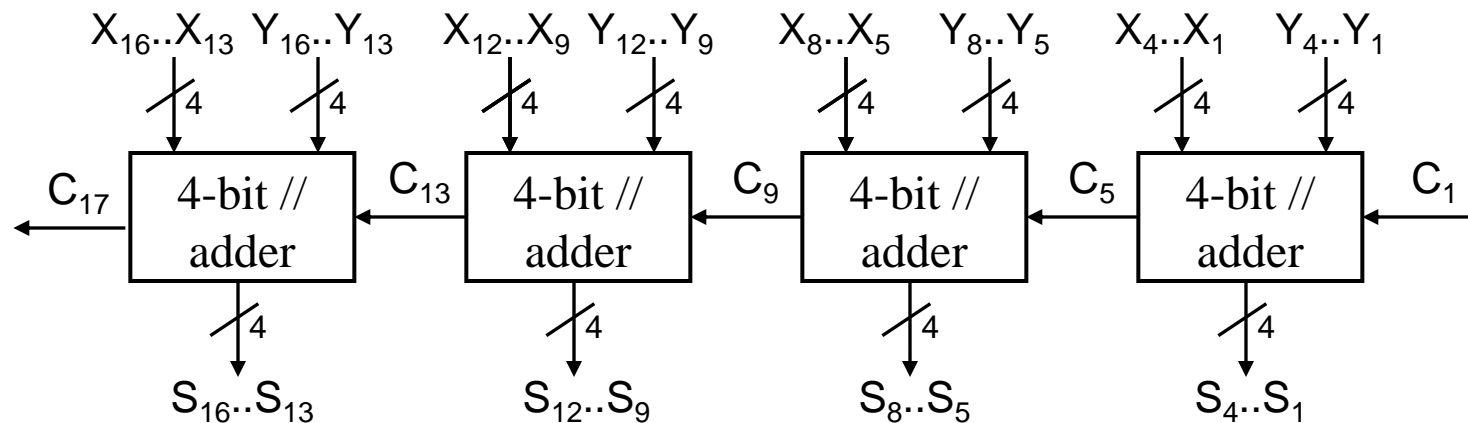
- Larger parallel adders can be built from smaller ones.
- Example: a **16-bit parallel adder** can be constructed from four 4-bit parallel adders:



Block diagram of 16-bit parallel adder

Cont.. 16-bit Parallel Adder

- Shortened notation for multiple lines:

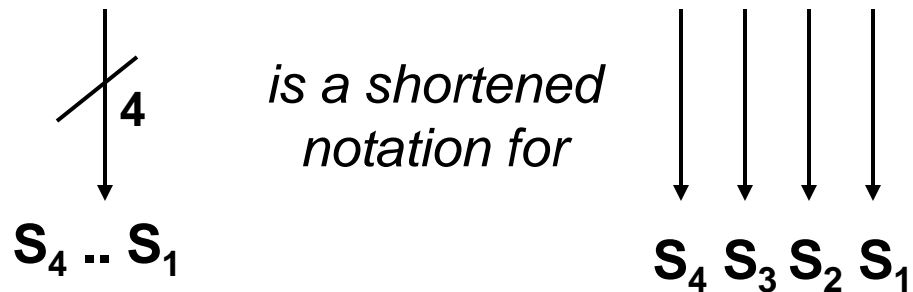

- 16-bit parallel adder ripples carry from one 4-bit block to the next.
- Such ripple-carry circuits are “slow” because of long delays needed to propagate the carries.

References

- M. M. Mano, *Digital Logic and Computer Design*, 5th ed., Pearson Prentice Hall, 2013.
- R. P. Jain, *Modern Digital Electronics*, 4th ed., Tata McGraw-Hill Education, 2009.