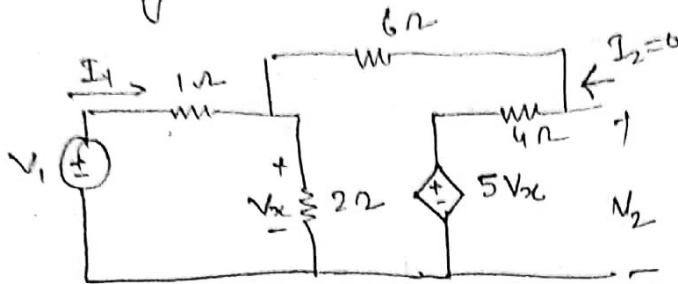


Solution, Tutorial-5

Q1

To get A and c




$$\frac{V_1 - V_x}{1} = \frac{V_x}{2} + \frac{V_x - 5V_x}{10}$$

$$V_1 = 1.1V_x$$

$$V_2 = 4(-0.4V_x) + 5V_x = 3.4V_x$$

$$A = \frac{V_1}{V_2} = \frac{1.1}{3.4} = 0.3235$$
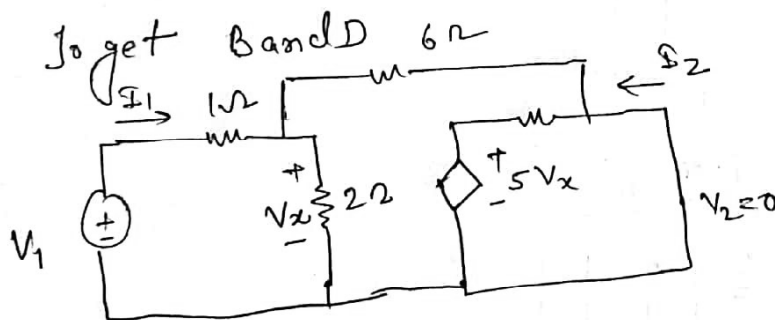
$$I_1 = \frac{V_1 - V_x}{1} = 1.1V_x - V_x = 0.1V_x \rightarrow c = \frac{I_1}{V_2} = \frac{0.1}{3.4} = 0.02941$$



$$\frac{V_1 - V_x}{1} = \frac{V_x}{6} + \frac{V_x}{2} \rightarrow V_1 = \frac{10}{6}V_x$$

$$I_2 = -\frac{5V_x}{4} - \frac{V_x}{6} = -\frac{17}{12}V_x \quad V_1 = I_1 + V_x$$

After solving
 $I_1 = V_1 - V_x = \frac{4}{6}V_x$


$$D = -\frac{I_1}{I_2} = \frac{4}{6} \left(\frac{12}{17} \right) = 0.4706$$

$$B = -\frac{V_1}{I_2} = \frac{10}{6} \times \frac{12}{17} = 1.176$$

$$[T] = \begin{bmatrix} 0.3235 & 1.176 \\ 0.02941 & 0.4706 \end{bmatrix}$$

Q₂

(a)

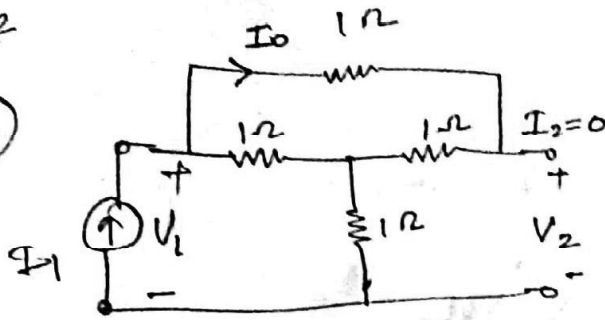

To obtain Z_{11} and Z_{21}

$$V_1 = I_1 \left[1 + 1 \parallel (1+1) \right] = I_1 \left(1 + \frac{2}{3} \right) = \frac{5}{3} I_1$$

$$Z_{11} = \frac{V_1}{I_1} = \frac{5}{3}$$

$$I_0 = \frac{1}{3} I_1$$

$$-V_2 + I_0 + I_1 = 0 \quad V_2 = \frac{1}{3} I_1 + I_1 = \frac{4}{3} I_1$$

$$Z_{21} = \frac{V_2}{I_1} = \frac{4}{3}$$

To obtain Z_{22} and Z_{12}



$$[Z] = \begin{bmatrix} \frac{5}{3} & \frac{4}{3} \\ \frac{4}{3} & \frac{5}{3} \end{bmatrix} \Omega$$


$$\left. \begin{aligned} Z_{22} &= Z_{11} = \frac{5}{3} \\ Z_{21} &= Z_{12} = \frac{4}{3} \end{aligned} \right\} \text{Due to symmetry.}$$

$$(b) [h] = \begin{bmatrix} \frac{\Delta_2}{Z_{22}} & \frac{Z_{12}}{Z_{22}} \\ -\frac{Z_{21}}{Z_{22}} & \frac{1}{Z_{22}} \end{bmatrix} = \begin{bmatrix} \frac{3}{5} & \frac{4}{5} \\ -\frac{4}{5} & \frac{3}{5} \end{bmatrix}$$

$$(c) [T] = \begin{bmatrix} \frac{Z_{11}}{Z_{21}} & \frac{\Delta_2}{Z_{21}} \\ \frac{1}{Z_{21}} & \frac{Z_{22}}{Z_{21}} \end{bmatrix} = \begin{bmatrix} \frac{5}{4} & \frac{3}{4} \\ \frac{3}{4} & \frac{5}{4} \end{bmatrix}$$

Q3

To get A and c

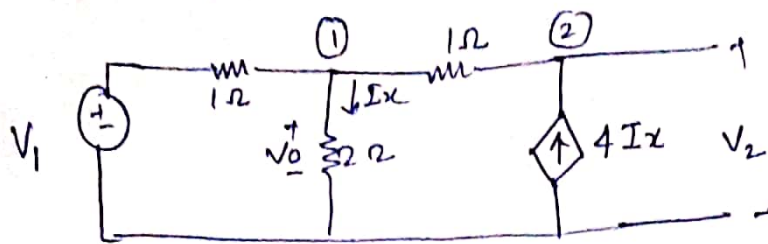

at node 1

$$I_1 = \frac{V_0}{2} + \frac{V_0 - V_2}{1} \rightarrow 2I_1 = 3V_0 - 2V_2$$

at node 2

$$\frac{V_0 - V_2}{1} = -4I_x = -4 \frac{V_0}{2} = -2V_0 \Rightarrow V_0 = \frac{V_2}{3}$$

after solving
 $2I_1 = -V_2$

$$c = \frac{I_1}{V_2} = \frac{-1}{2} = -0.5$$


But, $I_1 = \frac{V_1 - V_0}{1} = V_1 - \frac{V_2}{3} \Rightarrow -0.5V_2 = V_1 - \frac{V_2}{3} \Rightarrow V_1 = -\frac{0.5V_2}{3}$

$$A = \frac{V_1}{V_2} = -\frac{0.5}{3}$$

To get B and D

At node 1
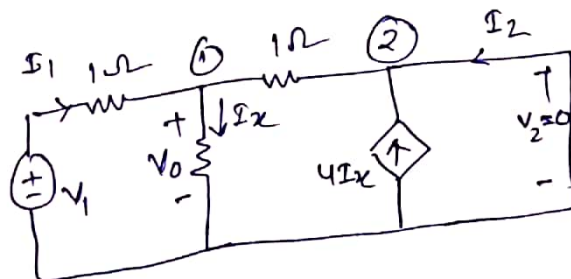
$$I_1 = \frac{V_0}{2} + \frac{V_0}{1} \rightarrow 2I_1 = 3V_0$$



at node 2

$$I_2 + 4I_x + \frac{V_0}{1} = 0$$

$$I_2 = -3V_0 \Rightarrow 2I_1 + I_2 = 0 \rightarrow I_1 = -0.5I_2 \rightarrow D = \frac{-I_1}{I_2} = 0.5$$

$$D = -0.5$$

$$I_1 = \frac{V_1 - V_0}{1} \Rightarrow V_1 = I_1 + V_0$$

$$V_1 = -\frac{1}{2}I_2 - \frac{1}{3}I_2 = -\frac{5}{6}I_2, \quad B = \frac{-V_1}{I_2} = \frac{5}{6}$$


$$[T] = \begin{bmatrix} -\frac{0.5}{3} & 5/6 \\ -0.5 & -0.5 \end{bmatrix}$$

Soln: 04


Given parameters-

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 3 & 4 \end{bmatrix} \begin{bmatrix} V_2 \\ -I_2 \end{bmatrix}$$

Two port network -

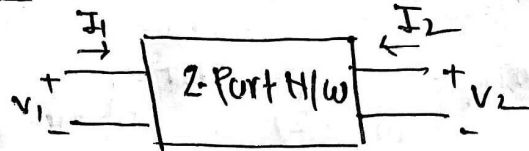

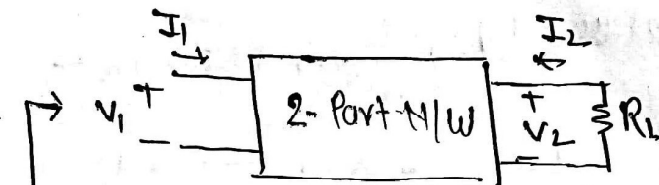According to given condition if port two is terminated by $R_L = 4\Omega$



Input Impedance $= \frac{V_1}{I_1}$

$$\begin{aligned} V_2 &= (-I_2)R_L \\ &= -4I_2 \quad \text{--- (i)} \end{aligned}$$

→ Input Impedance seen at port-1 $= \frac{V_1}{I_1} = \frac{V_2 - 2I_2}{3V_2 - 4I_2}$ --- (ii)

Substitute the value of (i) into (ii) -

$$\frac{V_1}{I_1} = \frac{V_2 - 2I_2}{3V_2 - 4I_2} = \frac{-4I_2 - 2I_2}{-12I_2 - 4I_2} = \frac{-6I_2}{-16I_2} = \frac{3}{8}$$

$$\boxed{\frac{V_1}{I_1} = \frac{3}{8} \text{ ohm}}$$

$$\text{ds} \quad [T] = \begin{bmatrix} 3 & 20 \\ 1 & 7 \end{bmatrix}$$


$$\Delta_T = (3)(7) - (20)(1) = 1$$

$$[\bar{A}] = \begin{bmatrix} \frac{A}{C} & \frac{\Delta_T}{C} \\ \frac{1}{C} & \frac{D}{C} \end{bmatrix} = \begin{bmatrix} 3 & 1 \\ 1 & 7 \end{bmatrix}$$

$$[Y] = \begin{bmatrix} \frac{D}{B} & -\frac{\Delta_T}{B} \\ -\frac{1}{B} & \frac{A}{B} \end{bmatrix} = \begin{bmatrix} \frac{7}{20} & -\frac{1}{20} \\ -\frac{1}{20} & \frac{3}{20} \end{bmatrix}$$

$$[Z] = \begin{bmatrix} \frac{B}{D} & \frac{\Delta_T}{D} \\ \frac{1}{D} & \frac{C}{D} \end{bmatrix} = \begin{bmatrix} \frac{20}{7} & \frac{1}{7} \\ -\frac{1}{7} & \frac{1}{7} \end{bmatrix}$$

Q6.

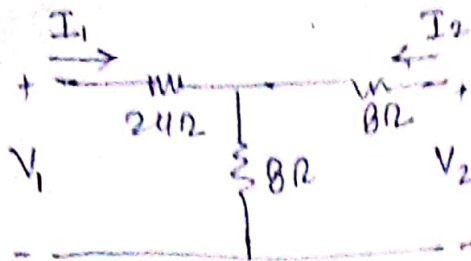

the admittance parameter use the output terminal shorted


$$Y_{11} = \frac{I_1}{V_1} \bigg|_{V_2=0}$$

Then, the two 8-ohm resistors are in parallel and $V_1 = 28I_1$

$$Y_{11} = \frac{1}{28} S$$

for Y_{12} , we have

$$Y_{12} = \frac{I_1}{V_2} \bigg|_{V_1=0}$$

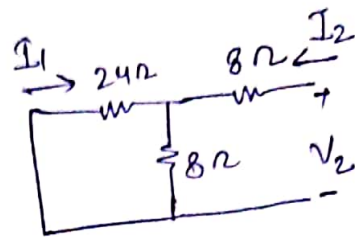

Employing current division, we have

$$-I_1 = I_2 \left(\frac{8}{8+24} \right)$$

$$\text{and } I_2 = \frac{V_2}{8 + \left[\frac{8(24)}{8+24} \right]} = \frac{V_2}{14}$$

$$Y_{12} = \frac{I_1}{V_2} = \frac{-(V_2/14)(1/4)}{V_2} = -\frac{1}{56} S$$

$$Y_{21} = Y_{12} = -\frac{1}{56} S$$

$$Y_{22} = \frac{I_2}{V_2} \bigg|_{V_1=0}, \quad I_2 = \frac{V_2}{8 + \left[\frac{8(24)}{8+24} \right]} = \frac{V_2}{14}$$

$$Y_{22} = \frac{1}{14} S$$

$$\text{Thus } I = YV \rightarrow \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} \frac{1}{28} & -\frac{1}{56} \\ -\frac{1}{56} & \frac{1}{14} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}$$