

JAYPEE INSTITUTE OF INFORMATION TECHNOLOGY
Electronics and Communication Engineering
Electrical Science-II (15B11EC211)
Tutorial Sheet: 4

Q.1 [CO2] In the circuit shown in Fig.1, the network is described by the following Y-parameter

$$\text{matrix } \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} 0.2 & 0.4 \\ 0.3 & 0.6 \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, \text{ Find the voltage gain } \left(\frac{V_2}{V_1}\right).$$

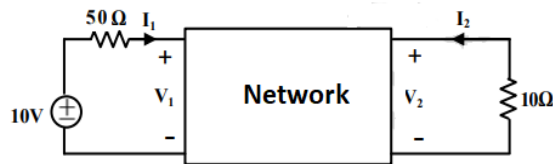


Fig.1

Q.2 [CO2] Find the impedance parameters Z_{11} , Z_{12} , Z_{21} and Z_{22} of the two port network as shown in Fig. 2.

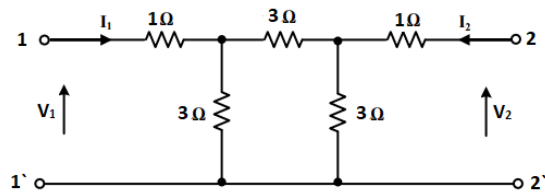


Fig.2

Q.3 [CO2] For the two port network shown in Fig.3, the impedance matrix is given as follows:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 4 & 6 \\ 8 & 10 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

Calculate the average power delivered to 2Ω resistor.

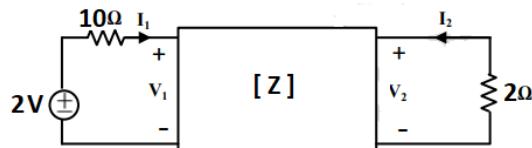


Fig.3

Q.4 [CO2] Find h-parameters for the network shown in figure 4.

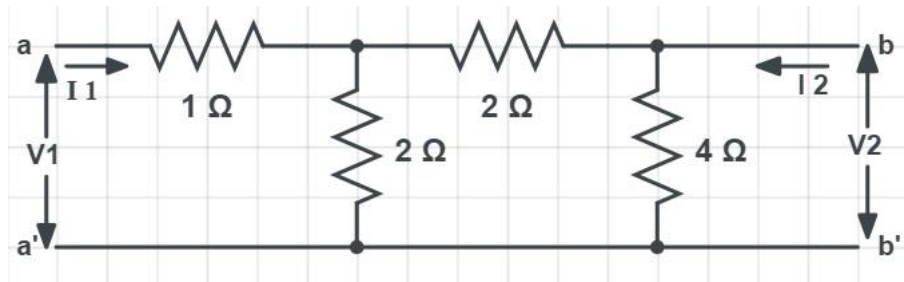


Fig.4

Q.5 [CO2] Find the value of current I_1 and I_2 for the circuit shown in Fig. 5, for this network Z-parameter matrix is given as follows:

$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} 1 & 2 \\ 3 & 4 \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}$$

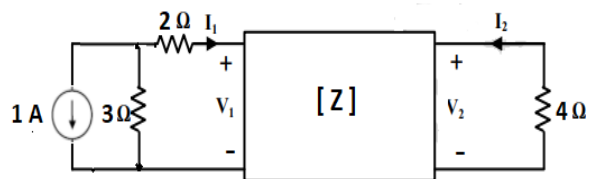


Fig.5

Q.6 [CO2] Find the impedance parameters Z_{11} , Z_{12} , Z_{21} and Z_{22} of the two port network shown in Fig.6.

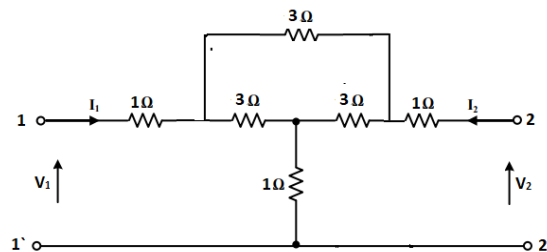


Fig.6